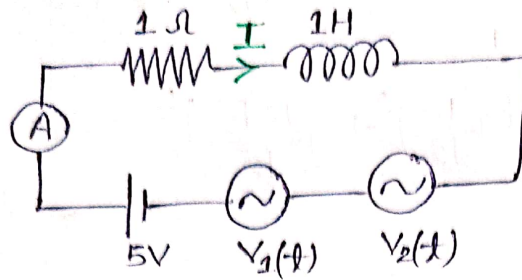


BE QUIZ-4 RUBRICS

SOL(1) :



$$V_1(t) = 10 \sin(t)$$

$$V_2(t) = 10\sqrt{5} \sin(2t)$$

NOTE: If nothing specified then RMS value considered of Ammeter in the question.

Here all sources having different frequencies, so by using Superposition theorem —

Case (I): According to 5V source

$$X_L = \omega L = (0)(1) = 0$$

$$|Z| = \sqrt{1^2 + 0^2} = 1 \Omega$$

$$I_0 = \frac{5}{|Z|} = \frac{5}{1} = 5A$$

— (1 Point)

Case (II): According to $V_1(t) = 10 \sin(t)$ source

$$X_L = \omega L = (1)(1) = 1 \Omega$$

$$|Z| = \sqrt{1^2 + 1^2} = \sqrt{2} \Omega$$

$$I_1 = \frac{(10/\sqrt{2})}{|Z|} = \frac{(10/\sqrt{2})}{\sqrt{2}} = 5A$$

— (1 Point)

Case (III): According to $V_2(t) = 10\sqrt{5} \sin(2t)$ source

$$X_L = \omega L = (2)(1) = 2 \Omega$$

$$|Z| = \sqrt{1^2 + 2^2} = \sqrt{5} \Omega$$

$$I_2 = \frac{(10\sqrt{5}/\sqrt{2})}{|Z|} = \frac{(10\sqrt{5}/\sqrt{2})}{\sqrt{5}} = 5\sqrt{2} A$$

— (1 Point)

$$\therefore \text{Ammeter reading, } I = \sqrt{I_0^2 + I_1^2 + I_2^2} = \sqrt{5^2 + 5^2 + (5\sqrt{2})^2} \\ = 10A$$

— (1 Point)

$$\begin{aligned} \text{Power Factor} &= \cos \theta = \frac{P}{S} = \frac{\text{Active Power}}{\text{Apparent Power}} = \frac{I^2 R}{VI} = \left(\frac{IR}{V} \right) \\ &= \frac{10 \times 1}{\sqrt{5^2 + \left(\frac{10}{\sqrt{2}} \right)^2 + \left(\frac{10\sqrt{5}}{\sqrt{2}} \right)^2}} = \frac{10}{\sqrt{325}} \\ &= 0.5 \end{aligned} \quad \text{--- (1 Point)}$$

SOL(2):

$$\begin{aligned} (a) \quad v(t) &= 9 \sin(t + 45^\circ) \\ i(t) &= 3 \sin(t - 45^\circ) \end{aligned}$$


Here voltage phasor lead to current phasor by 90° . Hence circuit contain a pure inductor with source.

$$X_L = \omega L$$

$$\frac{V}{I} = (1)(L)$$

$$\frac{(9/\sqrt{2})}{(3/\sqrt{2})} = (1)(L)$$

$$\therefore L = 3H$$

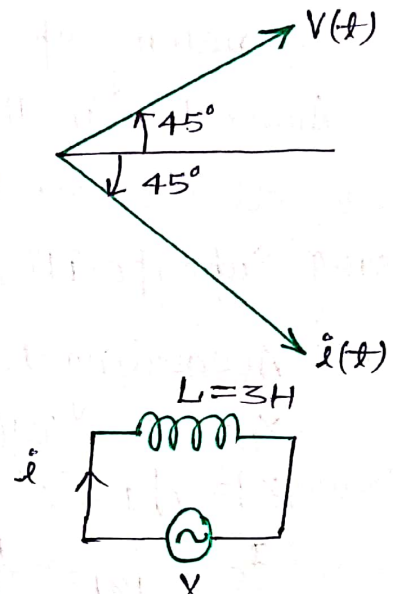


--- (2 Point)

$$\begin{aligned} (b) \quad v(t) &= 9 \sin(t + 30^\circ) \\ i(t) &= 3 \sin(2t + 60^\circ) \end{aligned}$$

NOTE: By using above equation, it is not possible to decide the Network. Since frequency of voltage & current are unequal.

--- (2 Point)

SOL(3):

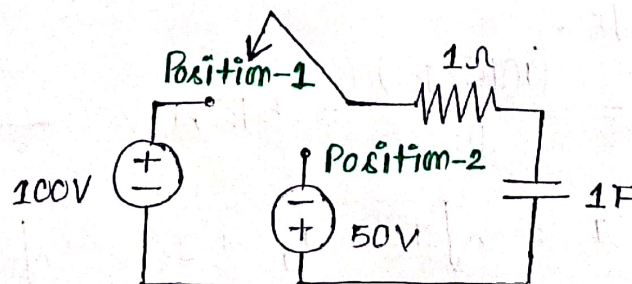

Case(I): at $t=0$ sec (Position-1)


$$V_c(t) = V_0 [1 - e^{-t/\tau}]$$

Here, $V_0 = 100$ Volt

$$\tau = RC = (1)(1) = 1 \text{ sec}$$

$$\therefore V_c(t) = 100 [1 - e^{-t/1}] = 100(1 - e^{-t}) \text{ Volt}$$
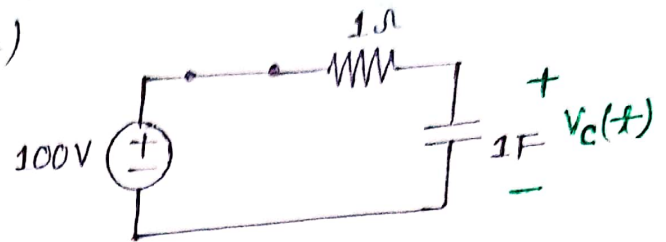
$$\therefore V_c(2\tau) = V_c(2) = 100(1 - e^{-2}) = 86.47 \text{ Volt} \quad \text{--- (2 Point)}$$




Case(II): at $t = 2\tau = 2$ sec (Position-2)

$$i(2) = \left(\frac{86.47 + 50}{1} \right) = 136.47 \text{ A}$$

--- (1)


--- (1 Point)

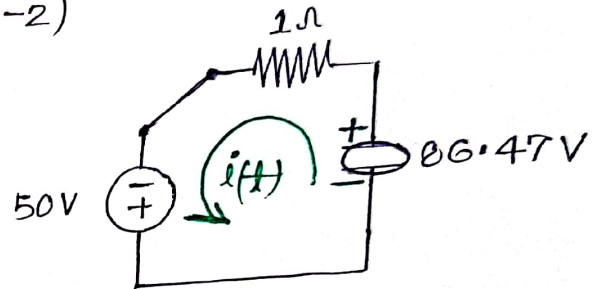

Case(III): at $t = \infty$ (Position-2)

$$i(\infty) = 0 \text{ A} \quad \text{--- (2)}$$

--- (1 Point)

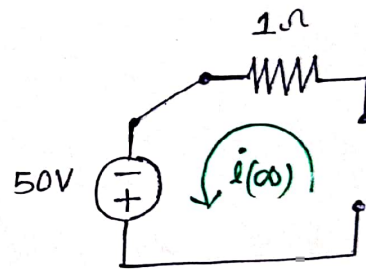

Now current response in Position-2 (by using eqn(1) & eqn(2)) ---

$$i(t) = [i(2) - i(\infty)] e^{-(t-2)/\tau} + i(\infty)$$

$$i(t) = [136.47 - 0] e^{-(t-2)/1} + 0$$

$$i(t) = (136.47) e^{-(t-2)}$$

--- (2 Point)