 


## DVD Quiz 6 Rubric

**Q1.** Draw the output waveform for the given input waveform for the given circuit and support your answer conceptually.




[2 Marks]

**Answer:**

Since NMOS cannot pass a strong 1 & PMOS cannot pass a strong 0 so we will have  $V_t$  drops across them and the swing will reduce accordingly.

[1 Mark]

 

[1 Mark]

**Q.2** Calculate the logical effort of input F (average) for the following skewed gates.

For simplicity, assume that any change in width will be done by a factor of 3, for making low or high skewed gates. Consider F as the inner input for making circuit of the below function.


High Skewed :  $Y = (A+B) \cdot (C+D) \cdot F$

[ 3 Marks]

# Answer


Q2) 
$$Y = (A+B) \cdot (C+D) \cdot F$$

 i) For high skewed case we have to downsize the NMOS. So instead of 3 we keep it 1 ( $\because$  width is decreased by a factor of 3). Also, F is critical output



For asymmetric gates, the reference inverter is taken accordingly to equal rise resistance & equal fall resistance

 For given design, the inverter with equal rise resistance is




Therefore 
$$g_m = \frac{2+1}{2+1} = 1$$

gate cap for the given circuit of F U/P

gate cap of the reference inverter

 Similarly reference inverter with equal fall resistance




$$g_d = \frac{2+1}{\frac{2}{3} + \frac{1}{2}} = \frac{3}{1} = 3$$

$$g_{avg} = \frac{g_u + g_d}{2} = \frac{3+1}{2} = \boxed{2}$$

**Q3.** In a 3 input NAND Gate the leakage power consumption drastically reduces on some input combinations (A=0, B=0, C=0). Explain the phenomenon with the help of a schematic diagram..

[2 Marks]


Answer:

 

This happens due to the stacking effect [0.5 Marks]. When A, B & C inputs are 0 then the Vb and Vc nodes are not pulled to the ground; they have certain potential depending on the resistance of the NMOS. Due to this Vsb increases and this leads to an increase of Vt of the device [0.5 Marks]. Leakage is inversely proportional to Vt so Leakage reduces [0.5 Marks]. Also, Vgs is negative for A & B NMOS and zero for C, this leads to a reduction in gate leakage. [0.5 Marks]

**Q4.** What function/ functionality does the circuit represent? What is the problem in the implementation below? How would you correct it? Draw the modified circuit diagram


[0.5 +0.5+1 marks]

 

 **Answer:**

The figure represents the MUX circuit. PMOS pass weak 0, so if the selected input is 0 then the output will be  $V_{th}$  of PMOS rather than 0.

We can improve the circuit by making a transmission gate implementation of the MUX circuit.



**Q5.** What is the challenge with transmission gate networks? How can we resolve it?

[0.5+0.5 marks]

**Answer:**

The long-chain transmission gate network has very high RC delays.

This can be resolved by adding buffers after a few stages.