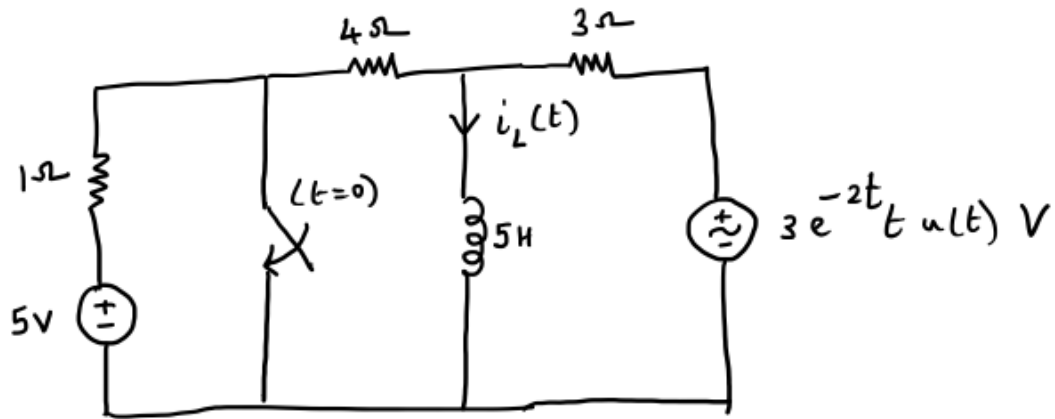



Ses-1

(10 marks) Consider the circuit shown below with voltage source excitation $v_s(t) = 3e^{-2t}u(t)V$. What is the current through the inductor, $i_L(t \geq 0)$?




Set-2

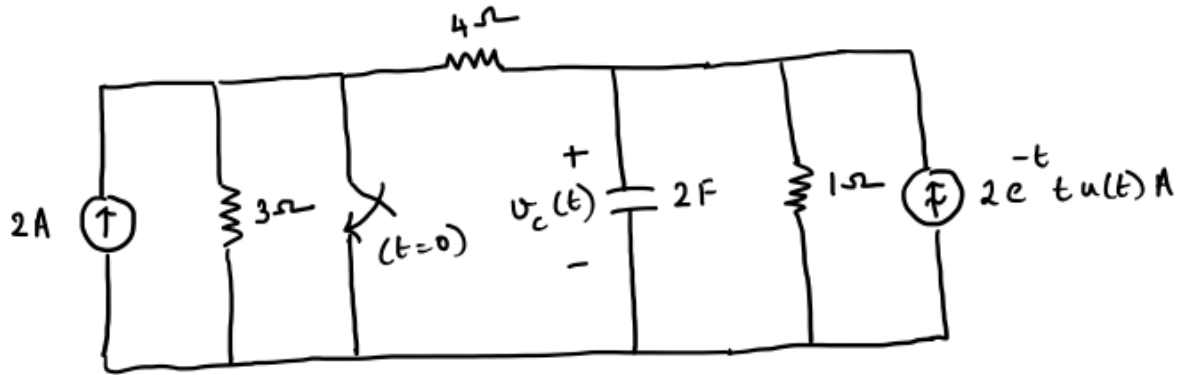(10 marks) Consider the circuit shown below with current source excitation $i_s(t) = 2e^{-t}u(t)$ A. What is the voltage across the capacitor, $v_C(t \geq 0)$?




Set - 3

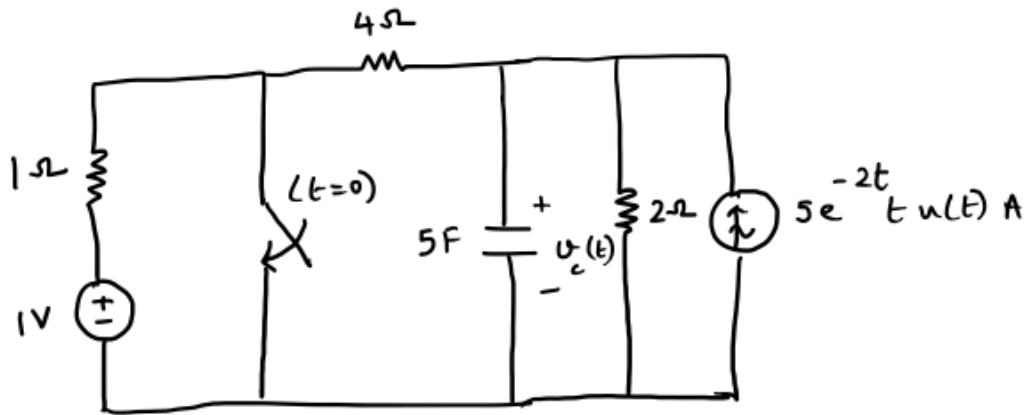
(10 marks) Consider the circuit shown below with current source excitation $i_s(t) = 5e^{-2t}u(t)$ A. What is the voltage across the capacitor, $v_C(t \geq 0)$?



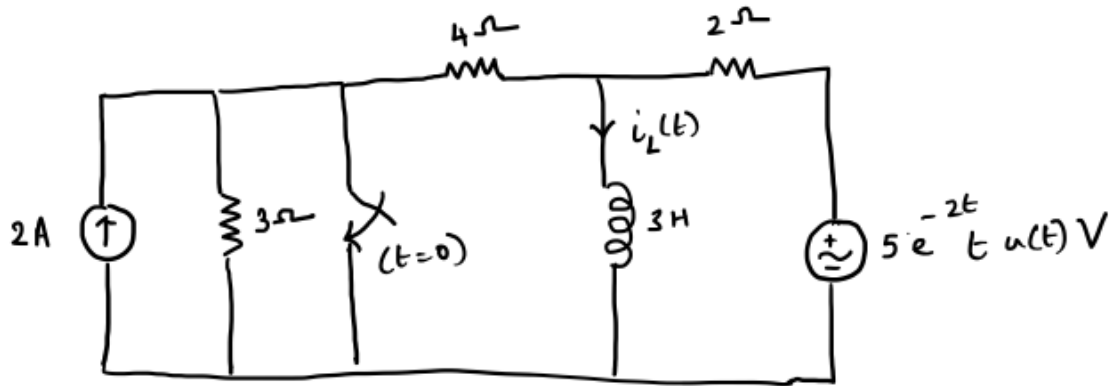
(10 marks) Consider the circuit shown below with voltage excitation $v_s(t) = 5e^{-2t}u(t)V$. What is the current through the inductor, $i_L(t \geq 0)$?




Q1

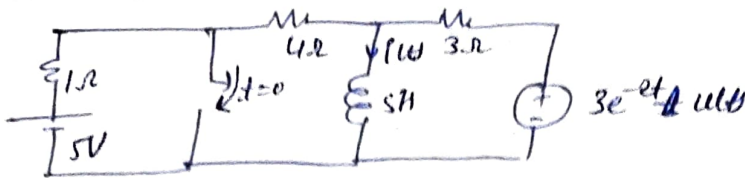Set-1given: $V_S(t) = 3e^{-2t} \text{ u(t)}$ 

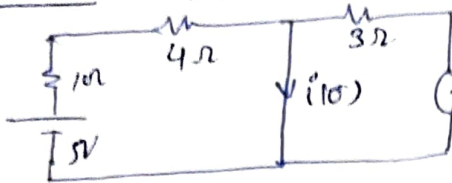Q1. finding $i(0^-)$ in the inductor
 at $t = 0^-$ (Inductor will be acting like short ckt as it attained Steady State)



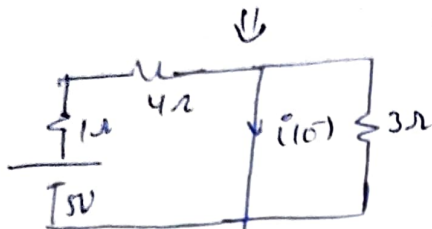Since if $t < 0$
 $\therefore V_S(t=0^-) = 0 \text{ V as } u(t) = 0$
 at $t = 0^-$




$$\therefore i(0^-) = \frac{5 \text{ V}}{(1+4) \Omega} = \frac{5}{5} = 1 \text{ A}$$

2 marks

$$\therefore i(0^-) = 1 \text{ A}$$

Now at $t \geq 0$ (case)

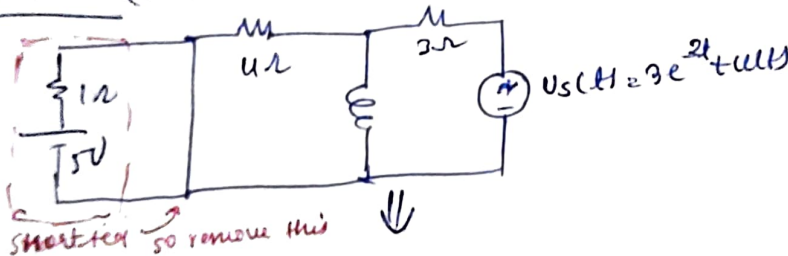


Shorted so remove this



2 marks

↓ use Laplace Transform

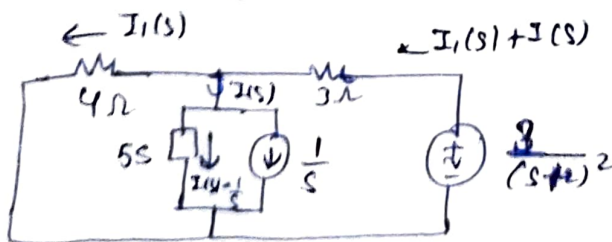

Replacing Inductor $s \rightarrow 1/s$
 by its Laplace domain equivalent.

2 marks

use KVL:

$$\frac{-3}{(s+2)^2} + 3(I_1(s) + I_2(s)) + 4I_1(s) = 0$$

→ 1 mark

$$\frac{3}{(s+2)^2} = 3I_1(s) + 3I_2(s) + 4I_1(s) = 7I_1(s) + 3I_2(s)$$

$$\frac{3}{(s+2)^2} = 3I_2(s) + 7I_1(s) \quad (+)$$

$$\text{Allo } \frac{-3}{(s+2)^2} + 3(I_1(s) + I_2(s)) + 5s \left[I_1(s) - \frac{1}{s} \right] = 0$$

$$= \frac{3}{(s+2)^2} + 3I_1(s) + 3I_2(s) + 5sI_1(s) - 5 = 0$$

$$5 + \frac{3}{(s+2)^2} = (3+5s)I_1(s) + 3I_2(s) \quad (2)$$

$$\begin{bmatrix} 3 & 7 \\ 3+5s & 3 \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} 3/(s+2)^2 \\ 5 + 3/(s+2)^2 \end{bmatrix}$$

$$\begin{pmatrix} I_1(s) \\ I_2(s) \end{pmatrix} = \frac{1}{-(12+35s)} \begin{bmatrix} 3 & -7 \\ -(3+5s) & 3 \end{bmatrix} \begin{bmatrix} 3/(s+2)^2 \\ 5 + 3/(s+2)^2 \end{bmatrix} \sim 1 \text{ mark}$$

$$I_1(s) = \frac{1}{-(12+35s)} \left(\frac{9}{(s+2)^2} - 35 \frac{21}{(s+2)^2} \right) = \frac{1}{(12+35s)} \left(35 + \frac{12}{(s+2)^2} \right)$$

$$I_1(s) = \frac{35}{35s+12} + \frac{12}{(12+35s)(s+2)^2}$$

$$= \frac{1}{s+12/35} + \frac{12/35}{(s+12/35)(s+2)^2} = \frac{1}{s+12/35} + \frac{0.125}{s+12/35} + \frac{0.126}{s+2} - \frac{0.207}{(s+2)^2}$$


Take inverse Laplace we get

$$i(t) = e^{-12/35t} u(t) + 0.125 e^{-12/35t} u(t) + 0.126 e^{-2t} u(t) - 0.207 t e^{-2t} u(t)$$

- 2 marks


Ques: $i_s(t) = 2e^{-t}u(t)$

Set -2

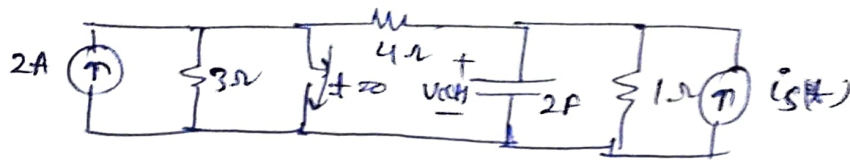

For $V(0^-)$ @

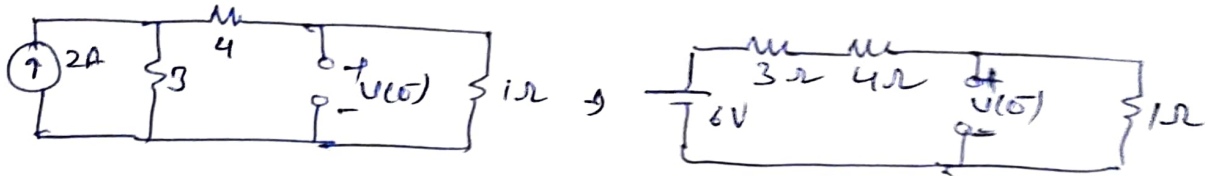at $t=0^-$ (Capacitor is at steady state and $i_s = 0A$ as $t=0^-$ $\therefore V(0^-) =$




$$V(0^-) = \frac{1}{\frac{1}{3} + \frac{1}{4}} \cdot \frac{1}{1} = \frac{3}{4} = 0.75V$$


$$V(0^-) = V(0^+) = 0.75V$$

→ 2 marks

@ $t > 0$

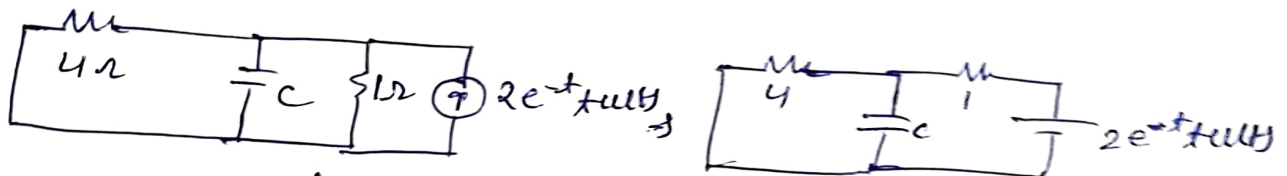

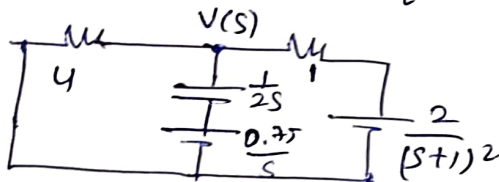use Laplace transform for capacitor and voltage source



(I need to find $V(s)$ only as it's volt on capacitor)

2 marks

use Nodal

2 marks

$$\frac{V(s)}{4} + \frac{V(s) - 0.75/s}{1/2s} + V(s) - \frac{2}{(s+1)^2} = 0 \rightarrow 1 \text{ mark}$$

$$\frac{V(s)}{4} + 2sV(s) - 1.5 + V(s) - \frac{2}{(s+1)^2} = 0$$

$$V(s) \left[1 + \frac{1}{4} + 2s \right] = 1.5 + \frac{2}{(s+1)^2}$$

$$V(s) \left[\frac{s}{4} + 2s \right] = 1.5 + \frac{2}{(s+1)^2} \Rightarrow V(s) = \frac{1.5}{2s + 5/4} + \frac{2}{(s+1)^2(2s + 5/4)}$$



$$V(s) = \frac{0.75}{s + 5/8} + \frac{1}{(s+1)^2(s + 5/8)} = \frac{0.75}{s + 5/8} + \frac{-2.107}{s+1} + \frac{-2.67}{(s+1)^2} + \frac{7.11}{(s + 5/8)} \quad 1 \text{ mark}$$

Taking inverse Laplace transform:

$$u(t) = 0.75e^{-518t} u(t) + 7.11e^{-518t} u(t) - 7.104e^{-t} u(t) - 2.67te^{-t} u(t).$$


— 2 marks

3-2

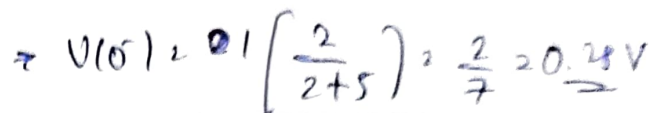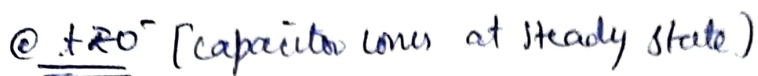

$$V(0^-) = V(0^+) = 0.28V$$
 - 2 marks


for $t > 0$

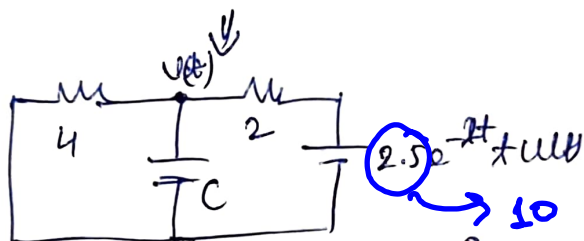

→ 2 marks

10 C 2 x 5 = 107

Take Laplace of circuit

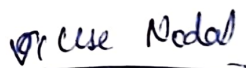

$$\frac{V(5)}{4} \leftarrow \frac{V(5) - 0.28/5}{1/55} + \frac{V(5) - 10}{2} \quad \text{but } 2 \rightarrow$$

- 5 1 mark

$$\frac{V(s)}{4} + 5sV(s) - 1.4 + \frac{V(s)}{2} - \frac{1.25}{(s+2)^2} = 0$$

$$V(s) \left[\frac{1}{4} + \frac{1}{2} + 5s \right] = 1.4 + \frac{225}{(s+2)^2} \Rightarrow V(s) [0.75 + 5s] = 1.4 + \frac{125}{(s+2)^2}$$

$$V(s) = \frac{1.4}{s+0.75} + \frac{1.25}{(s+0.75)(s+2)^2}$$

$$= \frac{0.28}{s+0.15} + \frac{0.25}{(s+2)^2(s+0.15)} = \frac{0.28}{s+0.15} + \frac{-0.073}{s+2} + \frac{-0.135}{(s+2)^2} + \frac{0.073}{s+0.15}$$

→ 1 mark

will change accordingly

→ 1 mark

2 marks


take new place will get

take inverse Laplace we get


$$i(t) = 0.28e^{-0.15t} u(t) - 0.073e^{-2t} u(t) - 0.135te^{-2t} u(t) + 0.073e^{-0.15t} u(t), \text{ or}$$

Ques: $v_s(t) = 5e^{-2t} \text{ mV}$

Sol-4

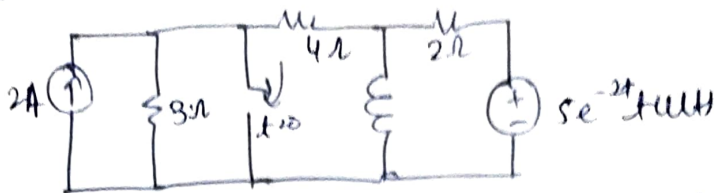

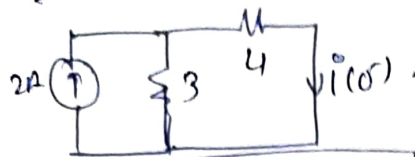① For $t=0^-$ capacitor inductor is at steady state




Using current division rule

$$i(0^-) = 2 \left[\frac{3}{3+4} \right] \cdot \frac{5}{7} = 0.85 \text{ A}$$


$$i(0^-) = i(0^+) = 0.85 \text{ A}$$

→ 2 marks


at $t > 0$

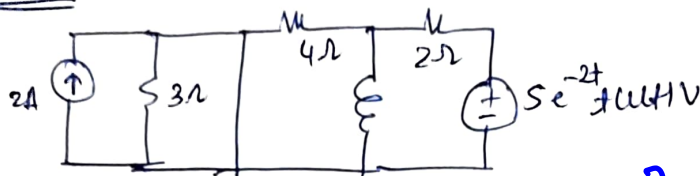

2 marks

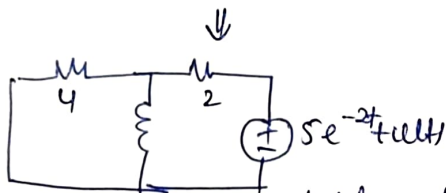

Use Laplace of the circuit

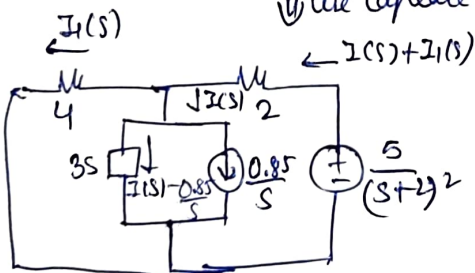

→ 2 marks

Use KVL

$$\frac{-5}{(s+2)^2} + 2[i(s) + i_1(s)] + 4i_1(s) = 0$$

$$\frac{5}{(s+2)^2} = 2i(s) + 2i_1(s) + 4i_1(s)$$

$$\frac{5}{(s+2)^2} = 2i(s) + 6i_1(s) \quad (1)$$

→ 1 mark.

$$\text{Also } \frac{-5}{(s+2)^2} + 2[i(s) + i_1(s)] + 3s[i_1(s) - 0.85/s] = 0$$

$$\frac{5}{(s+2)^2} = 2i(s) + 2i_1(s) + 3s i_1(s) - 2.55$$

$$2.55 + \frac{5}{(s+2)^2} = (2+3s)i(s) + 2i_1(s) \quad (2)$$

$$\begin{bmatrix} 2 & 6 \\ 2+3s & 2 \end{bmatrix} \begin{bmatrix} i(s) \\ i_1(s) \end{bmatrix} = \begin{bmatrix} 5/(s+2)^2 \\ 2.55 + 5/(s+2)^2 \end{bmatrix}$$

$$\begin{pmatrix} J(s) \\ I(s) \end{pmatrix} = \frac{1}{-(8+18s)} \begin{bmatrix} 2 & -6 \\ -(2+8s) & 2 \end{bmatrix} \begin{bmatrix} s(8+2)^2 \\ s(8+2)^2 + 0.185 \end{bmatrix}$$

→ 1 mark

$$J(s) = \frac{1}{-(8+18s)} \left[\frac{10}{(s+2)^2} - \frac{30}{(s+2)^2} - 1.53 \right] = \frac{20}{(s+2)^2(8+18s)} + \frac{1.53}{8+18s}$$

$$J(s) = \frac{0.085}{s+8/18} + \frac{1.11}{(s+8/18)(s+2)^2}$$

$$= \frac{0.085}{s+8/18} + \frac{-0.46}{s+2} - \frac{0.71}{(s+2)^2} + \frac{0.46}{s+8/18}$$

∴ Take inverse Laplace

$$i(t) = 0.085e^{-8/18t} u(t) - 0.46e^{-2t} u(t) - 0.71te^{-2t} u(t) + 0.46e^{-8/18t} u(t)$$

→ 2 marks