

DVD Quiz 3 Rubric

Q1. There are two wires with their dimensions shown in the Fig.1 below. The current direction is shown by the black arrow. If the ratio of their resistances $R_{\text{Wire1}} : R_{\text{Wire2}} = 3:2$. Find the ratio of their sheet resistances. [1 marks]

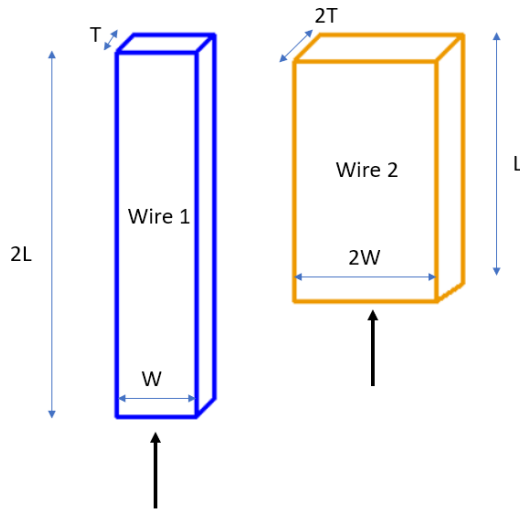


Fig. 1

Soln:

$$R_{\text{Wire1}} = R_{\text{sheet_Wire1}} * 2L/W$$

$$R_{\text{Wire2}} = R_{\text{sheet_Wire2}} * L/2W$$

$$R_{\text{Wire1}} : R_{\text{Wire2}} = 3 : 2$$

$$R_{\text{sheet_Wire1}} : R_{\text{sheet_Wire2}} = 3 : 8 \quad [\text{ binary marking 1 marks if answer is correct}]$$

Q2. What is the height of a standard cell in a 12 track library with the following specifications. : [2 marks]


Min metal1 width = $0.09u$

Min metal2 width = $0.1u$

Min spacing between two metal1 = $0.09u$

Min spacing between two metal2 = $0.1u$

Soln:

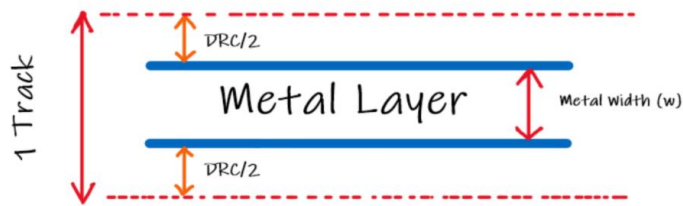

Track height is defined with respect to Metal2 layer so we have to use the Metal2 width and spacing(DRC). [0.5 marks]

Track pitch = 1 Track height = Metal track width + 2 * Half DRC [1 marks]

$$\text{Track pitch} = 0.1u + 2 * (0.1u/2) = 0.2u$$

$$12 \text{ track height} = 12 * \text{Track pitch} = 2.4u \quad [0.5 \text{ marks}]$$

Q3. Given below is the stick diagram(rough layout sketch) for a circuit.

Identify the circuit. How can you improve it?(Draw the modified stick diagram). List two advantages as compared to the given stick diagram? [1 + 1.5 +1]

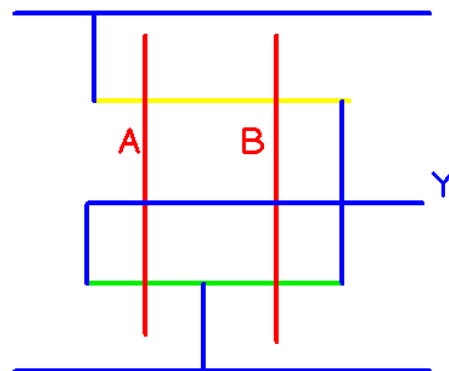


Fig.2

Soln:

The stick diagram represents the layout of a NOR gate [1 marks]

If the output Y is taken from the shared S/D region, then the diffusion capacitance at the output would reduce. [1.5 marks]

b) Where should you connect output Y in Fig 5 and Fig 6. [1 marks]

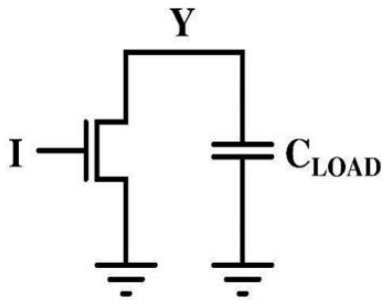


Fig. 4

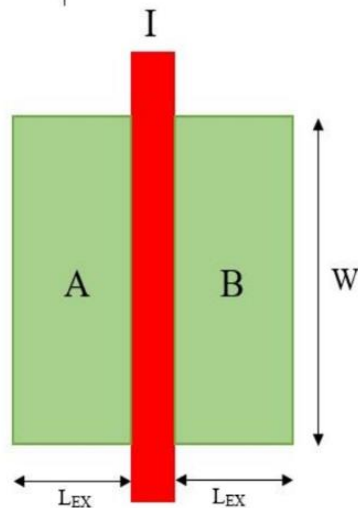


Fig. 5

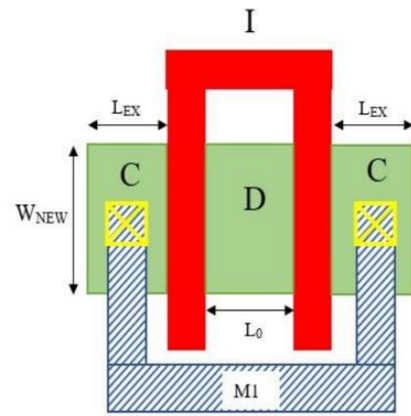


Fig. 6

Soln:

a) Diffusion capacitance = bottom capacitance + sidewall capacitance

For region A ,

$$\text{diffusion cap} = c_b * (W * L_{EX}) + c_s * (W + 2 * L_{EX})$$

$$\text{diffusion cap} = 0.5 * (W * W/4) + 0.4 * (W + 2 * W/4)$$

$$\Rightarrow 0.03125 + 0.3 = 0.33125 \text{ fF}$$

[0.5 marks]

Region A and B are symmetric so for B also 0.33125 fF

For region C,

Bottom capacitance is proportional to the bottom area

As, area of region A = $W * L_{EX}$

Area of region C = $2 * (W/2 * L_{EX}) = W * L_{EX}$ = Area of region A

So, bottom cap of region C = 0.03125 fF

[0.5 marks]

Sidewall capacitance is proportional to the perimeter of the sidewall

Perimeter of sidewall in region A = $W + 2 * L_{EX} = 0.5 + 2 * 0.125 = 0.75 \mu$

Perimeter of sidewall in region C = $2 * (W/2 + 2 * L_{EX}) = 2 * (0.25 + 2 * 0.125) = 1 \mu$

So, sidewall cap of region C = $(1/0.75) * \text{sidewall cap of A} = 0.4 \text{ fF}$ [0.5 marks]

So, diffusion capacitance of region C = $0.4 + 0.03125 = 0.43125 \text{ fF}$

For region D,

Bottom capacitance is proportional to the bottom area

As, area of region A = $W * L_{EX}$

Area of region D = $W/2 * L_0 = W/2 * 1.25 L_{EX}$

So, bottom cap of region D = $0.625 * \text{bottom cap of A} = 0.0195 \text{ fF}$

[0.5 marks]

Sidewall capacitance is proportional to the perimeter of the sidewall

*Perimeter of sidewall in region A = $W + 2 * L_{ex} = 0.5 + 2 * 0.125 = 0.75 \mu$*

*Perimeter of sidewall in region D = $2 * L_o = 2 * 1.25 L_{ex} = 0.3125 \mu$*

*So, sidewall cap of region D = $(0.3125/0.75) * \text{sidewall cap of A} = 0.125 \text{ fF}$ [0.5 marks]*

So, diffusion cap of region D = $0.0195 + 0.125 = 0.1445 \text{ fF}$

b) In Fig.5 as A and B region is symmetric we can connect Y in either of the region

In Fig.6 , output Y should be connected to the D region as it has less capacitance than C region. [0.5 + 0.5 marks]