

# Assignment -1

## Basic Electronics (BE): ECE113

### Winter-2023

Release: 22-Mar-2023 (4:00 PM)

Submission: 29-Mar-2023 (4:00 PM)

### Instructions

- **Institute Plagiarism Policy Applicable.** This will be subjected to strict plagiarism check.
- This assignment should be attempted individually.
- A maximum point for this assignment is 40. All questions are compulsory.
- **File Submission:** Only a *.pdf* file are acceptable, which you have to submit on Google Classroom. Use A4 size sheets only (ruled or blank) to solve your assignment and scan it to create a *.pdf* file. Attempt each question on a different sheet. Do not start a new question at the back of the previous one. Do not forget to mention Page Number (bottom center) clearly on each sheet of the assignment. Submit a *.pdf* file named *A1\_RollNo.pdf* (e.g., *A1\_PhD22100.pdf*), which containing the quality scan copy of your solved assignment.
- **Submission Policy:** Turn-in your submission as early as possible to avoid late submissions. In case of multiple submissions, the latest submission will be evaluated. Expect **No Extensions**. Late submissions will not be evaluated and hence will be awarded zero marks strictly.
- **Clarifications:** Symbols have their usual meaning. Assume the missing information & mention it in the report. Use Google Classroom for any queries. In order to keep it fair for all, no email queries will be entertained.
- There could be multiple ways to approach a question. Please justify your answers. Questions without justification will get zero marks.

**Question-1:** Find equivalent resistance between the points A & D, in the given below circuit- (4 Points)

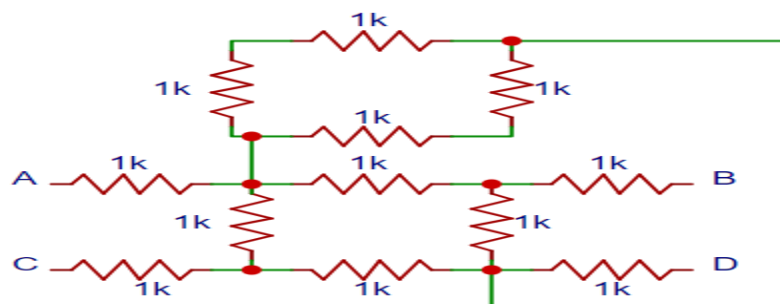


Figure 1

**Question -2:** In the given following circuit find the node voltage  $V_a$ ,  $V_b$ ,  $V_c$  and  $V_d$  with the help of nodal analysis. (6 Points)

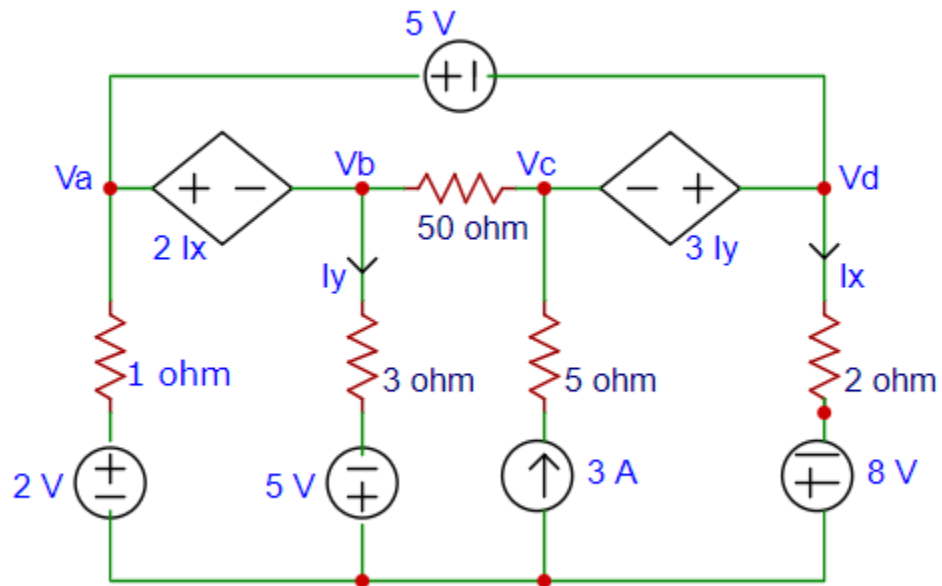


Figure 2

**Question -3:** In the given following circuit, find out the value of current 'I' by using mesh analysis.

(5 Points)

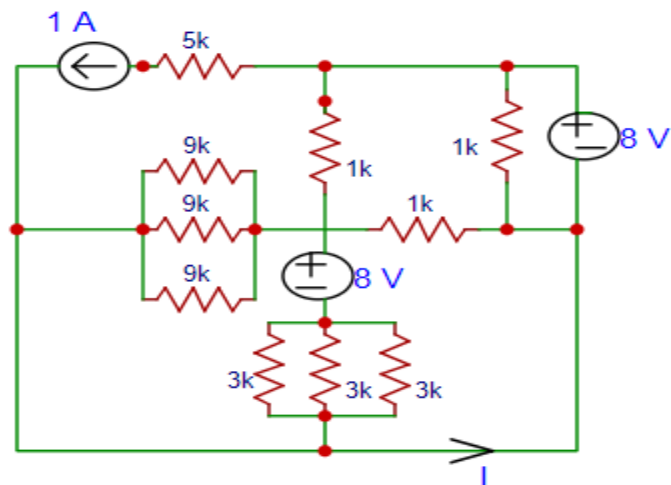


Figure 3

**Question -4:** Find the value of ' $V_x$ ' with the help of nodal analysis in the given below circuit- **(6 Points)**

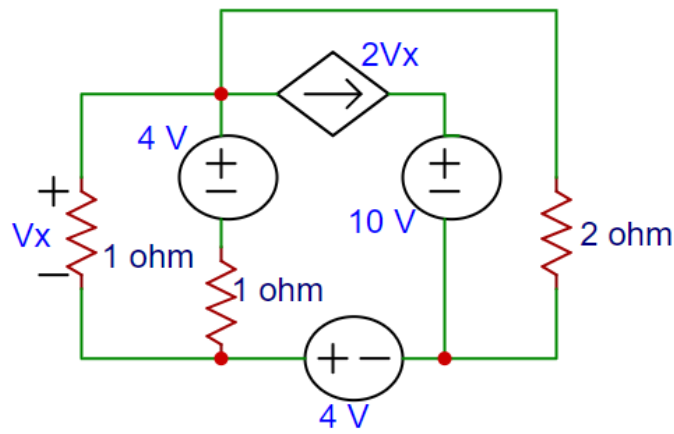


Figure 4

**Question -5:** In the given following circuit, find the value of currents  $I_1$ ,  $I_2$ ,  $I_3$  &  $I_4$  with the help of nodal analysis. **(7 Points)**

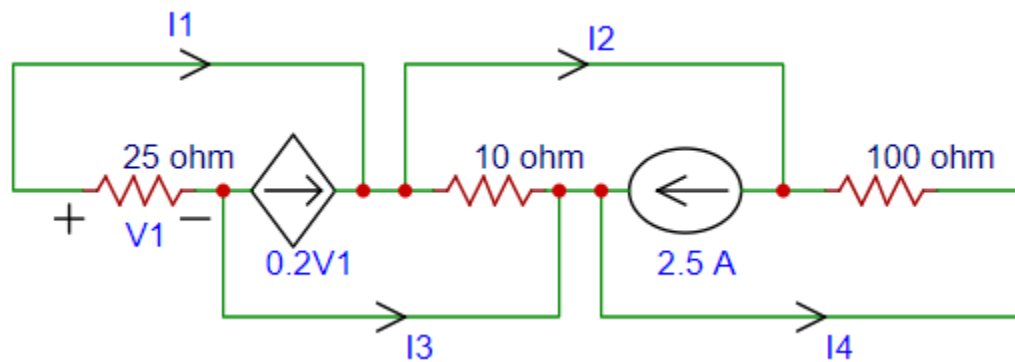


Figure 5

**Question -6:** In the given following circuit find the value of node voltages  $V_a$ ,  $V_b$  and  $V_c$  with the help of KVL, KCL & ohm's law. (6 Points)

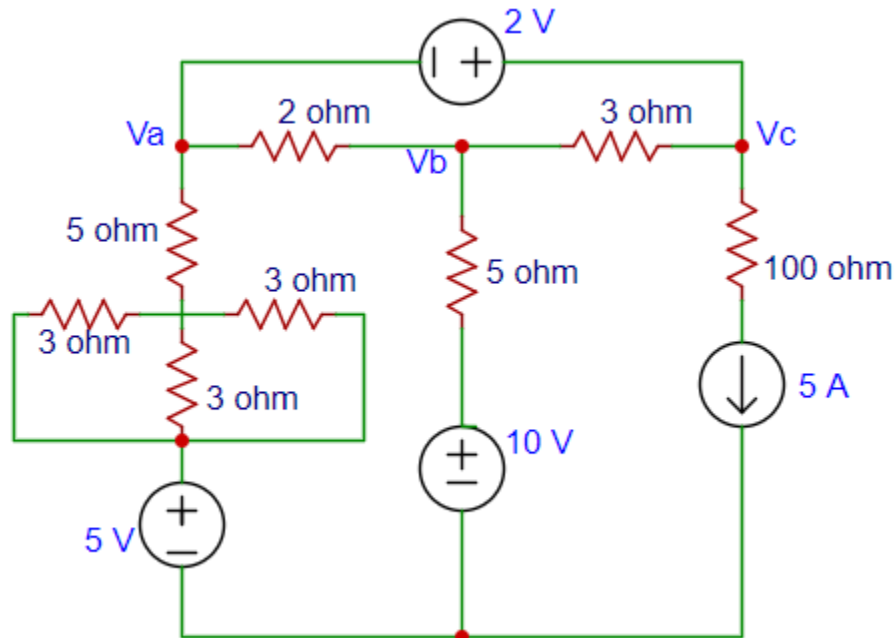


Figure 6

**Question -7:** The voltage  $V(t)$  & current  $I(t)$  through an electrical circuit element is given below. Draw the absorbed power in each and every cases (for all time period). (6 Points)

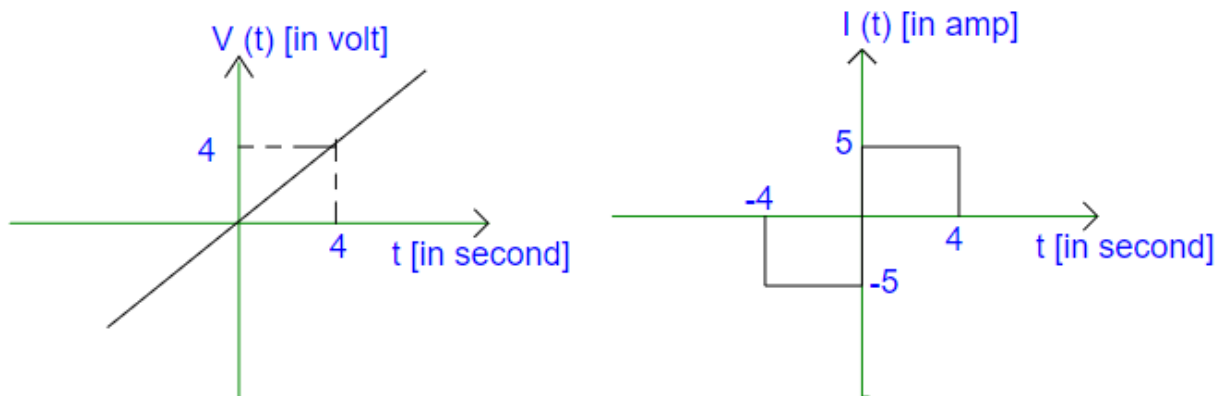


Figure 7

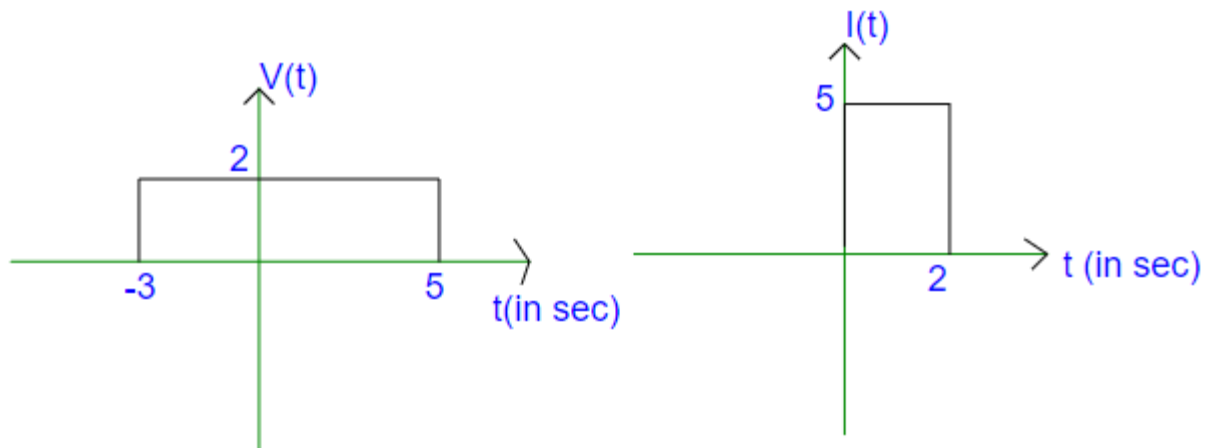


Figure 8

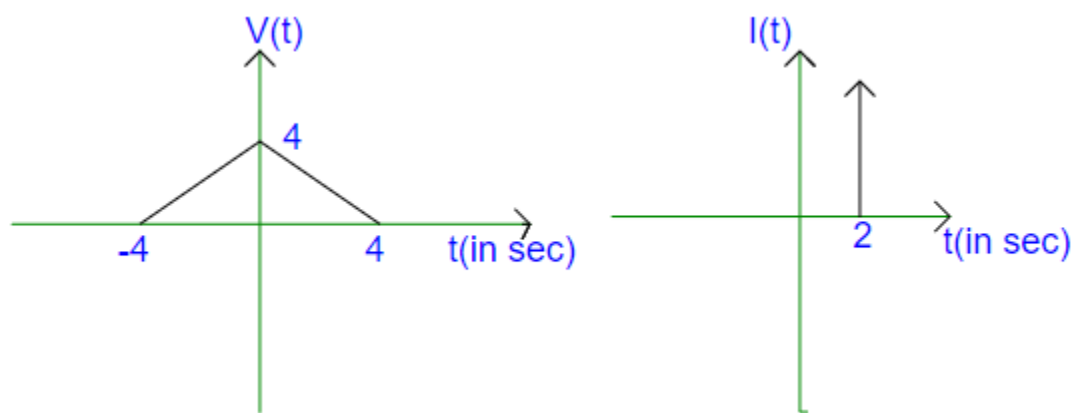


Figure 9