

# ECE113: Basic Electronics Re-Mid Semester Exam-2023

Date: **25/05/2023**

Duration: **1Hours**

Total Points: **40 Points**

**Q1:** In Fig.-1, Find the equivalent current across  $2\ \Omega$  resistor.

**[1 Points]**

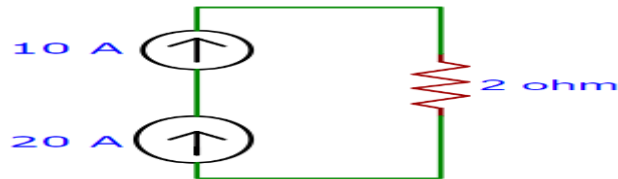


Figure 1

**Q2:** Define following terms with graphs- (a) Ideal & Practical Voltage Source (b) Ideal & Practical Current Source

**[3 Points]**

**Q3:** In Fig.-2, if  $V_1 = 5V$  &  $V_2 = 3V$ , then what is the input impedance of the CRO.

**[2 Points]**

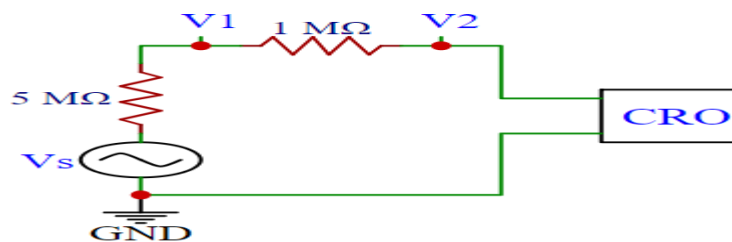


Figure 2

**Q4:** In Fig.-3, find the equivalent resistance between points A & B.

**[3 Points]**

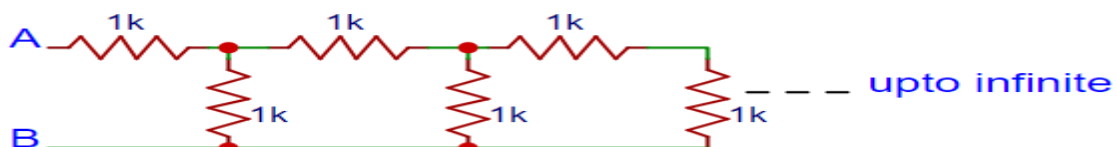


Figure 3

**Q5:** A practical voltage source of  $3V$  with internal resistance of  $2\ \Omega$  is connected to nonlinear resistor. The characteristic of nonlinear resistor is given by  $V_{NL} = I_{NL}^2$ . Find power dissipation of nonlinear resistor.

**[3 Points]**

**Q6:** In Fig.-4, find the equivalent resistance 'R' across the terminal A&B.

**[7 Points]**

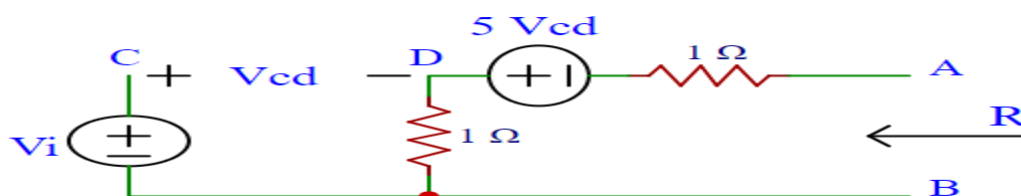


Figure 4

**Q7:** In Fig.-5, when switch  $S_1$  is closed, the ideal ammeter  $M_1$  reads 5 A. What will the ideal voltmeter  $M_2$  read when  $S_1$  is kept open? (The value of  $E$  is not specified). **[7 Points]**

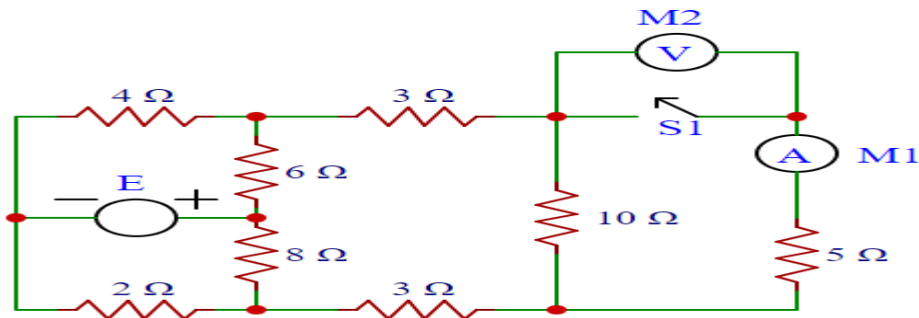


Figure 5

**Q8:** In Fig.-6, the switch  $S$  is open for a long time and it is closed at time  $t=0$  sec. What will be the current response  $i(t)$  for time  $t \geq 0^+$  sec. **[7 Points]**

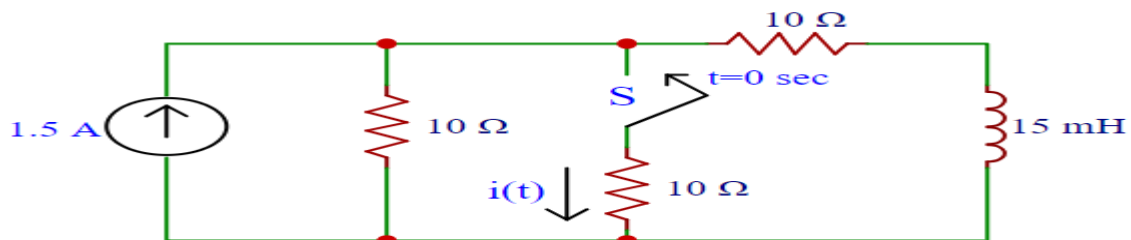


Figure 6

**Q9:** In Fig.-7, the switch has been in position-1 for long time and abruptly changes to position-2 at time  $t=0$  sec. Find out the response of the capacitor voltage  $V_C(t)$  for time  $t > 0$  sec. **[7 Points]**

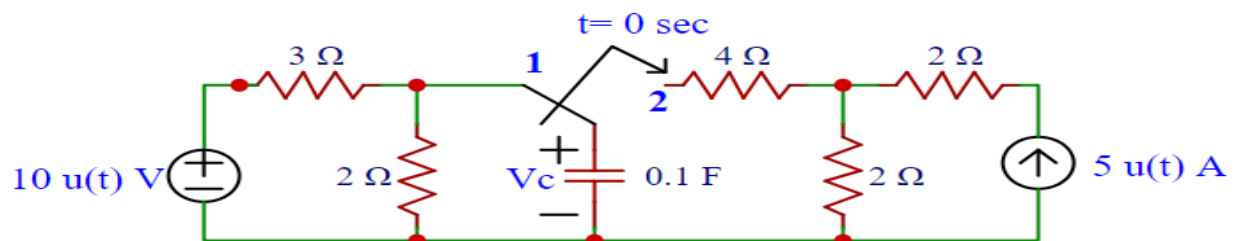


Figure 7