

# ASSIGNMENT-3 RUBRICS


SOL(1):

Step(I) ÷ at  $t = 0^- \text{ sec}$   
(steady state)

$$I_1(0^-) = 0 \text{ A}$$

$$I_2(0^-) = 0 \text{ A}$$

$$V_C(0^-) = 0 \text{ V}$$

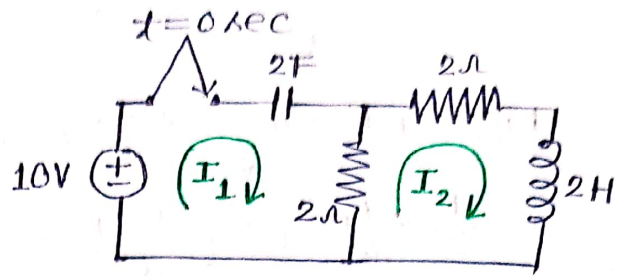

Step(II) ÷ at  $t = 0^+ \text{ sec}$  (Transient state)

$$I_1(0^+) = \left(\frac{10}{2}\right) = 5 \text{ A} \quad \text{--- (a)}$$

$$I_2(0^+) = I_2(0^-) = 0 \text{ A} \quad \text{--- (b)}$$

$$V_C(0^+) = V_C(0^-) = 0 \text{ V} \quad \text{--- (c)}$$

(3 x 0.2 Points)

$$4I_2 + 2 \frac{dI_2}{dt} - 2I_1 = 0 \quad \text{--- (1)}$$

$$4(0) + 2 \frac{dI_2(0^+)}{dt} - 2(5) = 0$$

$$\frac{dI_2(0^+)}{dt} = 5 \text{ (A/sec)} \quad \text{--- (d) --- (1 Points)}$$

Differentiating eq<sup>n</sup>(1), w.r.t. time 't'—

$$4 \frac{dI_2}{dt} + 2 \frac{d^2 I_2}{dt^2} - 2 \frac{dI_1}{dt} = 0 \quad \text{--- (2)}$$

$$-10 + \left(\frac{1}{2}\right) \int I_1 dt + 2(I_1 - I_2) = 0 \quad \text{--- (3)}$$

Differentiating eq<sup>n</sup>(3), w.r.t. time 't'—

$$-0 + \left(\frac{1}{2}\right) I_1 + 2 \left( \frac{dI_1}{dt} - \frac{dI_2}{dt} \right) = 0 \quad \text{--- (4)}$$

$$\left(\frac{1}{2}\right) 5 + 2 \left( \frac{dI_1(0^+)}{dt} - 5 \right) = 0$$

$$\frac{dI_1(0^+)}{dt} = 3.75 \text{ (A/sec)} \quad \text{--- (e) --- (1 Points)}$$

Put the value from eq<sup>n</sup>(e) to eq<sup>n</sup>(2) —

$$\frac{d^2 I_2(0^+)}{dt^2} = 2 \times 3.75 - 4 \times 5 = -6.25 \text{ A/sec}^2 \text{ — (f)}$$

— (1 Points)

Differentiating eq<sup>n</sup>(4) w.r.t. time 't' —

$$\left(\frac{1}{2}\right) \frac{dI_1}{dt} + 2 \left[ \frac{d^2 I_1}{dt^2} - \frac{d^2 I_2}{dt^2} \right] = 0$$

$$\frac{d^2 I_1(0^+)}{dt^2} = -7.10 \text{ A/sec}^2 \text{ — (g) — (1 Points)}$$

Step (III): at  $t = \infty$  sec (at steady state)

$$I_1(\infty) = 0 \text{ A}$$


— (h)

$$I_2(\infty) = 0 \text{ A}$$

— (i)

} (2x0.2 Points)

SOL(2) :-

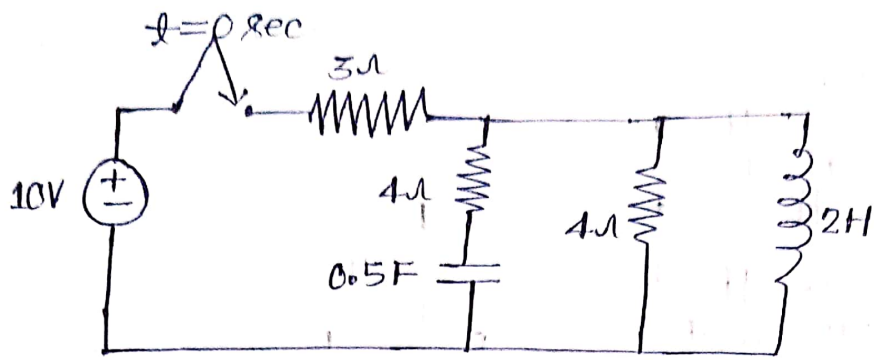


Step(I) : at  $t = 0^-$  sec (at steady state)

$$V_C(0^-) = 0V$$

$$I_L(0^-) = 0A$$

Step(II) : at  $t = 0^+$  sec (at Transient State)

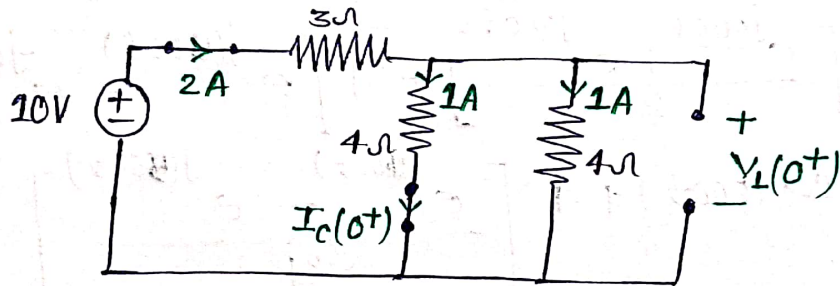Equivalent circuit at time  $t = 0^+$  sec



$$I_C(0^+) = 1A \quad \text{--- (a)}$$

$$I_C = C \cdot \frac{dV_C}{dt}$$

$$\frac{dV_C(0^+)}{dt} = \left(\frac{1}{0.5}\right) = 2 \text{ (V/sec)} \quad \text{--- (b)}$$

$$V_L(0^+) = 1 \times 4 = 4V \quad \text{--- (c)}$$


$$V_L = L \cdot \frac{dI_L}{dt}$$

$$\frac{dI_L(0^+)}{dt} = \left(\frac{4}{2}\right) = 2 \text{ (A/sec)} \quad \text{--- (d)}$$

(4x1.25 Points)



SOL(3) :-

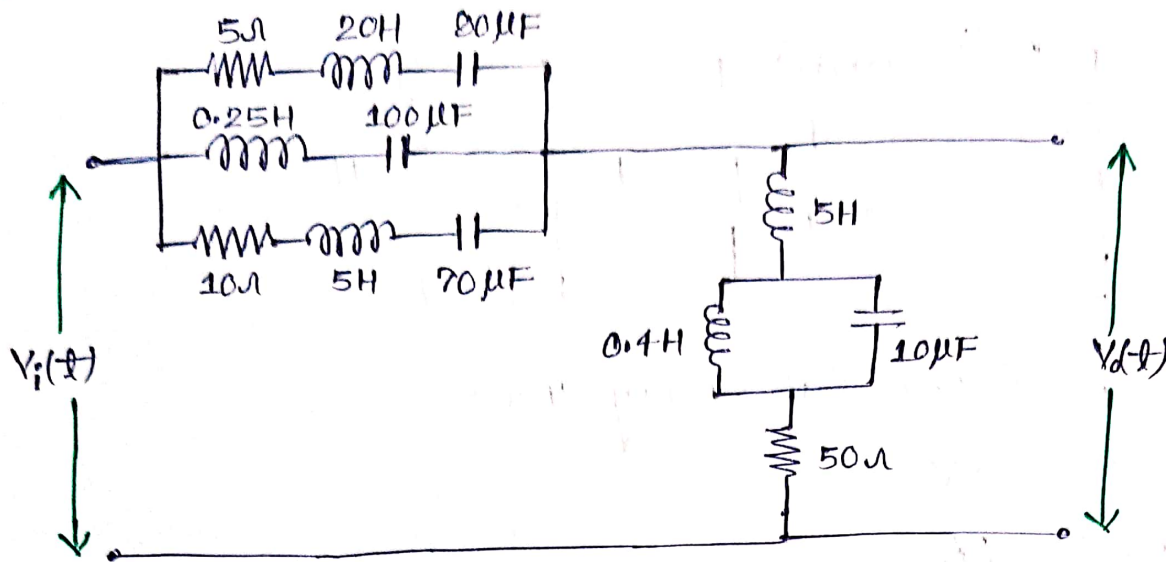

$$\begin{aligned}
 \text{where } V_i(t) &= e^{-j200t} + 2e^{-j(500t - \pi/2)} + e^{j200t} - 2e^{j(500t + \pi/2)} \\
 &= (e^{j200t} + e^{-j200t}) + 2j e^{-j(500t)} - 2j e^{j(500t)} \\
 &= 2 \left[ \frac{e^{j200t} + e^{-j200t}}{2} \right] + 2j \left[ \frac{e^{-j(500t)} - e^{j(500t)}}{2j} \right] \\
 &= 2 \cos(200t) + 4 \left[ \frac{e^{j(500t)} - e^{-j(500t)}}{2j} \right] \\
 &= 2 \cos(200t) + 4 \sin(500t)
 \end{aligned}$$


As different frequencies are operating, using superposition theorem, we get —

for  $\omega = 200 \text{ rad/sec}$

$$X_L = \omega L = (200)(0.25) = 50\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(200)(100 \times 10^{-6})} = 50\Omega$$

$$\therefore X_L = X_C$$

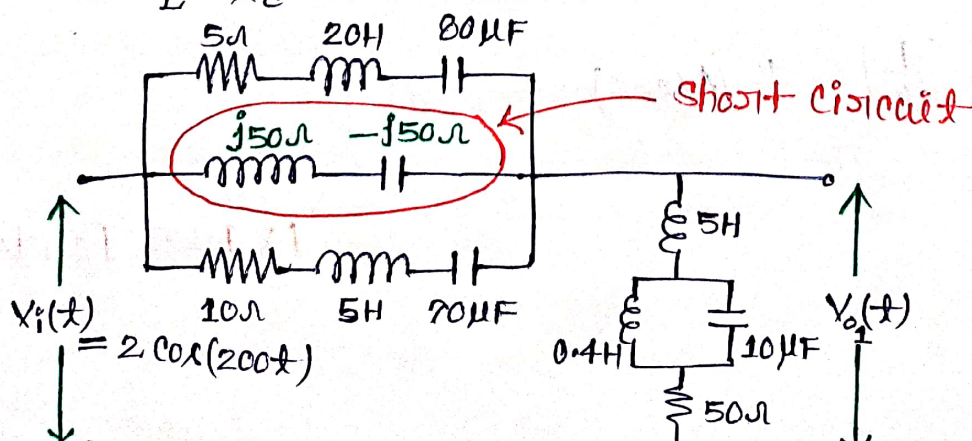


$$\therefore V_o(t) = V_i(t) = 2 \cos(200t) \quad \text{--- (1) --- (2 Points)}$$

for  $\omega = 500 \text{ rad/sec}$

$$X_L = 500 \times 0.4 = 200 \Omega$$

$$X_C = \left( \frac{1}{500 \times 10 \times 10^{-6}} \right) = 200 \Omega$$

$$\therefore X_L = X_C$$

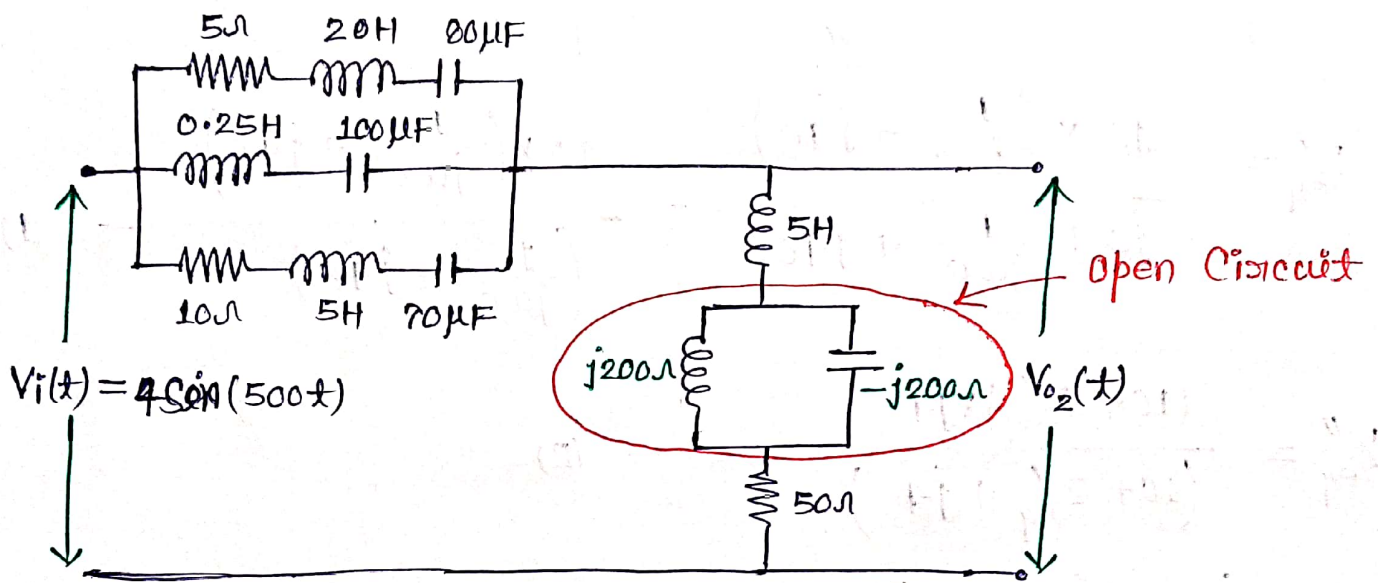


$$\therefore V_o(t) = V_i(t) = 4 \sin(500t) \quad \text{--- (2) --- (2 Points)}$$

By eq<sup>n</sup>(1) & eq<sup>n</sup>(2) — [By Superposition Theorem]

$$V_o(t) = V_{o1}(t) + V_{o2}(t)$$

$$V_o(t) = 2 \cos(200t) + 4 \sin(500t) \quad \text{--- (1 Points)}$$

SOL (4) :-

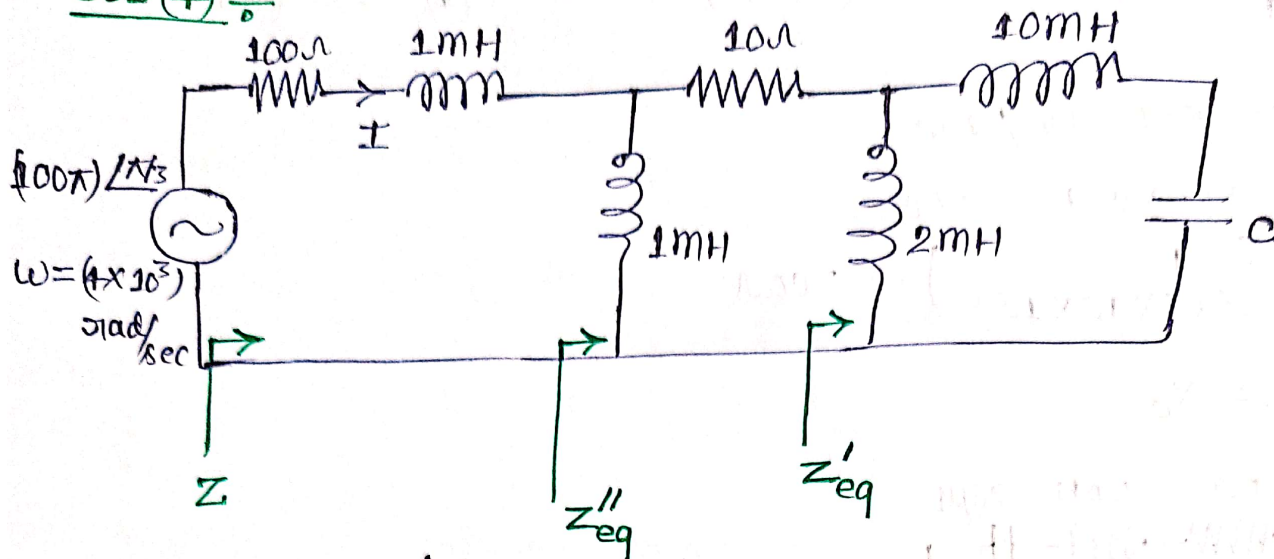

$$Z'_{eq} = \frac{j8 \times \left( \frac{1}{j\omega C} + j40 \right)}{j8 + \frac{1}{j\omega C} + j40} = \frac{j8 \times \left( \frac{1}{j\omega C} + j40 \right)}{\left( \frac{1}{j\omega C} + j40 \right)} \quad (1)$$

$$Z''_{eq} = \frac{(10 + Z'_{eq}) \times j4}{(10 + Z'_{eq} + j4)} \quad (2)$$

$$Z = (100 + j4 + Z''_{eq}) \quad (3)$$

$\therefore I = 0$  (Given)

$\therefore Z$  should be infinite ( $\infty$ ).

Hence  $Z''_{eq} = \infty$  (By eq<sup>n</sup> (3))

$\therefore 10 + Z'_{eq} + j4 = 0$  (By eq<sup>n</sup> (2))

$$-(10 + j4) = \frac{j8 \times \left( \frac{1}{j\omega C} + j40 \right)}{\left( \frac{1}{j\omega C} + j40 \right)}$$

$$-(10 + j4) \left( \frac{1}{j\omega C} + j40 \right) = \frac{8}{\omega C} - 320$$

After solving —  $C = 5.21 \mu F$  (Imaginary Part)

AND


$C = 5.86 \mu F$  (Real Part) (5 Points)

NOTE: In Practical, complex value of 'C' is not possible.



### SOL(5) :-

Step(I): To find the  $V_{th}$  —

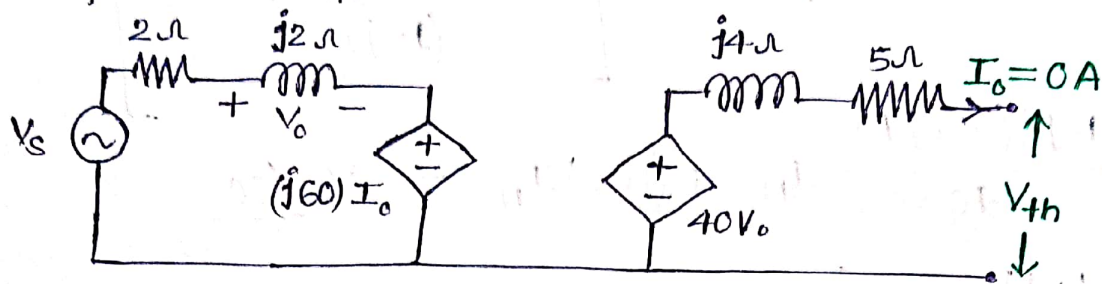

$$\therefore I_0 = 0$$


$$\therefore (j60)I_0 = 0 \quad (\text{Short circuit})$$

$$V_s = 80 \angle 60^\circ \quad (\text{Given})$$

$$\begin{aligned} \therefore V_0 &= \left( \frac{j2}{2+j2} \right) (80 \angle 60^\circ) \\ &= \left( \frac{1 \angle 90^\circ}{\sqrt{2} \angle 45^\circ} \right) (80 \angle 60^\circ) = 56.57 \angle 105^\circ \text{ Volt} \end{aligned}$$

$$\therefore V_{th} = 40V_0 = (2262.8) \angle 105^\circ \text{ Volt} \quad \text{--- (2 Points)}$$

Step(II): To find the  $I_N$  —

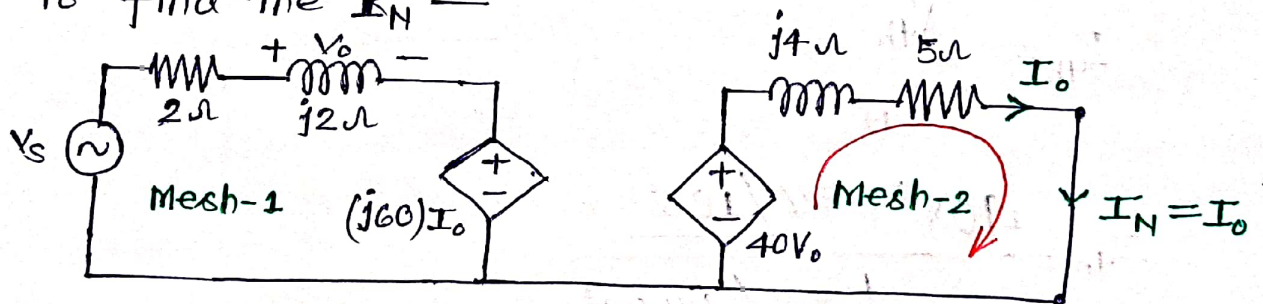

In Mesh-2 —

$$-40V_0 + (5+j4)I_N = 0 \quad \text{--- (1)}$$

In Mesh-1 —

$$\frac{V_s - (j60)I_N}{(2+j2)} = \frac{V_0}{j2}$$

$$V_s - (j60)I_N = -j(1+j)V_0 = (1-j)V_0$$

$$V_0 = \frac{80 \angle 60^\circ - (j60)I_N}{(1-j)} \quad \text{--- (2)}$$

By eq<sup>n</sup> (1) & (2) —

$$(5+j4)I_N = 40 \left[ \frac{80 \angle 60^\circ - (j60)I_N}{(1-j)} \right]$$

$$\frac{(1-j)(5+j4)}{40} I_N + (j60)I_N = 80 \angle 60^\circ$$

$$\left[ \frac{(9-j)}{40} + j60 \right] I_N = 80 \angle 60^\circ$$

$$(0.23 + j59.98) I_N = 80 \angle 60^\circ$$

$$[59.98 \angle 89.78^\circ] I_N = 80 \angle 60^\circ$$

$$I_N = 1.33 \angle -29.78^\circ \text{ A} \quad \text{--- (2 Points)}$$

Step (III): To find  $R_{th}/Z_{th}$

$$Z_{th} = \frac{V_{th}}{I_N}$$

$$Z_{th} = \frac{40 \times 56.57 \angle 105^\circ}{1.33 \angle -29.78^\circ}$$


$$Z_{th} = 40 \times (42.53) \angle 134.78^\circ \Omega$$

$$Z_{th} = (1701.35) \angle 134.78^\circ \Omega \quad \text{--- (1 Points)}$$



SOL(6) :-

Step (i) :-

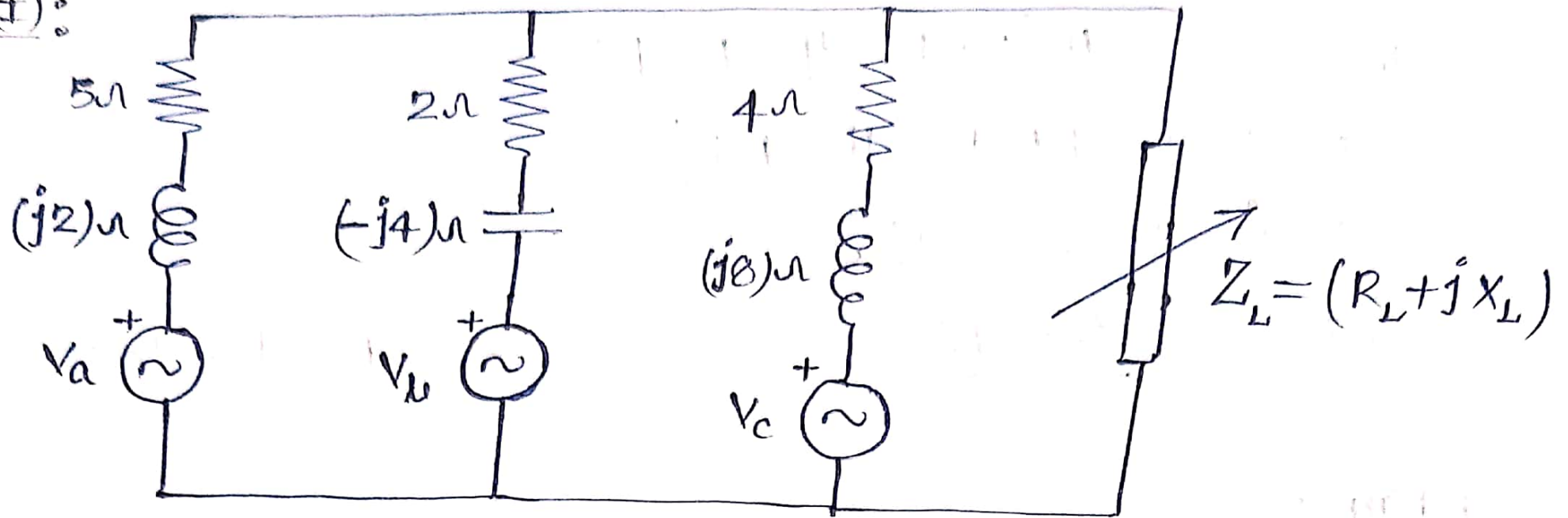

where,  $V_a = 100 \angle 60^\circ \text{ V}$

$$V_b = 80 \angle 40^\circ \text{ V}$$

$$V_c = 40 \angle 20^\circ \text{ V}$$


To find out the  $V_{ab}$

Step (II): To find  $Z_{th}$

$$\begin{aligned} Z_{th} &= (5+j2) \parallel (2-j4) \parallel (4+j0) \\ &= (2.98-j1.43) \parallel (4+j0) \\ &= (3.07-j0.29) \Omega \\ &= 3.08 \angle -5.40^\circ \Omega \end{aligned}$$

— (1.5 points)

Step (III):

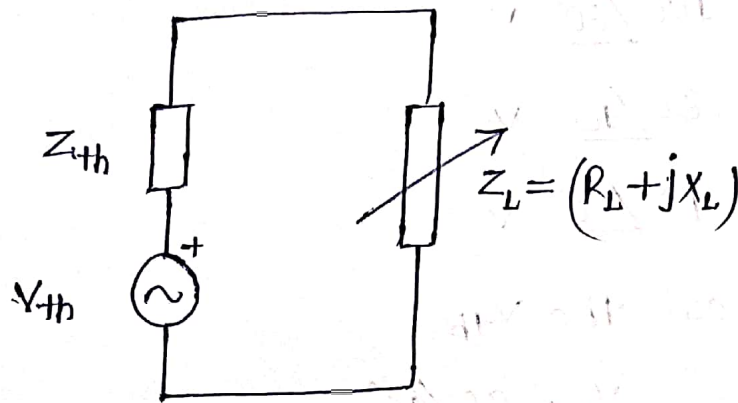

For maximum power transfer in the load impedance —


$$Z_L = Z_{th}^* \quad (R_L \text{ \& } X_L \text{ both are variable})$$

$$\therefore Z_L = (3.07 + j0.29) \Omega$$

$$= 3.08 \angle 5.40^\circ \Omega$$

— (1 points)

SOL (7) ÷

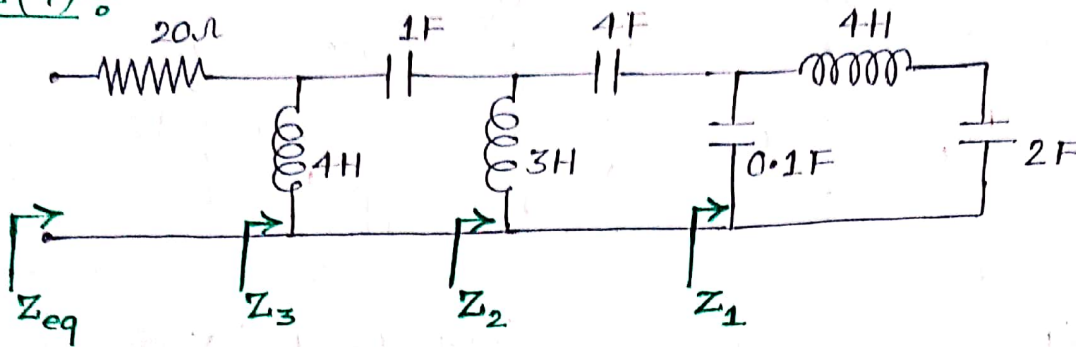

$$Z_1 = \left( -\frac{10j}{\omega} \right) \parallel \left[ j(4\omega - \frac{1}{2\omega}) \right]$$

$$Z_1 = \frac{(-10j)(8\omega^2 - 1)}{\omega(8\omega^2 - 21)} \quad \text{--- (1 Point)}$$

$$Z_2 = (j3\omega) \parallel \left[ \left( \frac{-j}{4\omega} \right) + Z_1 \right]$$

$$Z_2 = \frac{j3\omega(-328\omega^2 + 61)}{(96\omega^4 - 500\omega^2 + 61)} \quad \text{--- (1 Point)}$$

$$Z_3 = (j4\omega) \parallel \left[ \frac{-j}{\omega} + Z_2 \right]$$

$$Z_3 = \frac{j4\omega[-1000\omega^4 + 763\omega^2 - 61]}{[-1000\omega^4 + 763\omega^2 - 61] + 4\omega^2[96\omega^4 - 500\omega^2 + 61]}$$

--- (1 Point)

$$Z_{eq} = 20 + Z_3$$

For resonance frequency of the circuit —

$$\text{Im}(Z_{eq}) = 0$$

$$4\omega(-1000\omega^4 + 763\omega^2 - 61) = 0$$


$$\omega = 0, 0.78, 0.3 \text{ rad/sec}$$

$$f = 0 \text{ Hz}, 0.12 \text{ Hz}, 0.05 \text{ Hz}$$

--- (1 Point)



SOL(8) :-

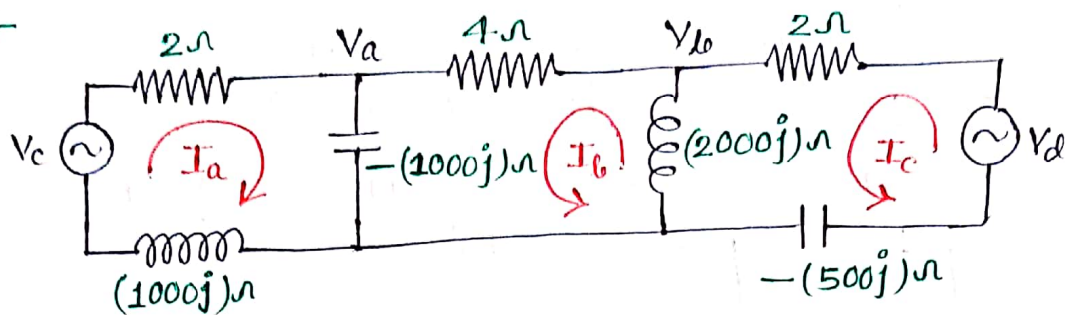

$$V_c = 40 \sin(1000t + 60^\circ) = 40 \angle 60^\circ = (20 + 34.64j) \text{ Volt}$$

$$V_d = 60 \sin(1000t - 40^\circ) = 60 \angle -40^\circ = (45.96 - 38.57j) \text{ Volt}$$

(a) Using Nodal analysis —

$$\frac{V_a - V_c}{(2 + 1000j)} + \frac{V_a}{(-1000j)} + \frac{V_a - V_b}{4} = 0$$

$$0.25 V_a - 0.25 V_b = (0.03 - 0.02j) \quad \text{--- (1)}$$

$$\frac{V_b - V_a}{4} + \frac{V_b - V_d}{(2 - 500j)} + \frac{V_b}{(2000j)} = 0$$

$$-0.25 V_a + (0.25 + 1.5 \times 10^{-3}j) V_b = (0.08 + 0.09j) \quad \text{--- (2)}$$

By eq<sup>n</sup> (1) & (2), we get —

$$\therefore V_a = (46.8 - 73.4j) \text{ Volt}$$

$$= 87.05 \angle (-57.48^\circ) \text{ Volt}$$

$$= 87.05 \sin(1000t - 57.48^\circ) \text{ Volt}$$

$$\therefore V_b = (46.67 - 73.33j) \text{ Volt}$$

$$= 86.92 \angle (-57.53^\circ) \text{ Volt}$$

$$= 86.92 \sin(1000t - 57.53^\circ) \text{ Volt}$$

} (3 x 0.5 Points)

} (3 x 0.5 Points)

(b) Using Mesh Analysis —

$$-(20 + 34.64j) + (2 + 1000j)I_a + (-1000j)(I_a + I_b) = 0 \quad \text{--- (3)}$$

$$(-1000j)(I_b + I_a) + 4I_b + (2000j)(I_b - I_c) = 0 \quad \text{--- (4)}$$

$$-(45.96 - 38.57j) + (2 - 500j)I_c + (2000j)(I_c - I_b) = 0 \quad \text{--- (5)}$$

By solving eq<sup>n</sup> (3), (4) & (5), we get —

$$\therefore I_a = (0.1 + 0.03j) \text{ A} = 0.1 \angle 16.7^\circ = 0.1 \sin(1000t - 16.7^\circ) \text{ A}$$

--- (3 x 0.5 Points)



$$\therefore I_b = (-0.03 + 0.02j) A$$

$$= 0.04 \angle 151.7^\circ A$$

$$= 0.04 \sin(1000t + 151.7^\circ) A$$

} (3x0.5 Points)

$$\therefore I_c = (-0.07 + 0.1j) A$$

$$= 0.07 \angle 180^\circ A$$

$$= 0.07 \sin(1000t + 180^\circ) A$$

} (3x0.5 Points)