

## MTH 204: Worksheet 6 solutions

Q1.

$$I = \frac{dQ}{dt}$$

$$\Rightarrow Q(t) = \int I(t) dt$$

Voltage drop across circuit = External voltage

$$V.d. \text{ across } R + V.d. \text{ across } L + V.d. \text{ across } C = \cancel{Q(t)} V(t)$$

$$RI + LI' + \frac{Q}{C} = \cancel{Q(t)} V(t)$$

$$\Rightarrow LI' + RI + \frac{1}{C} \int I(t) dt = V(t) = V_0 \sin(\omega t)$$

Differentiate once to get rid of integral

$$\Rightarrow \boxed{LI'' + RI' + \frac{I}{C} = V_0 \omega \cos(\omega t)} \quad \text{--- (1)}$$

Q2.

$$\text{Homogeneous part is } LI'' + RI' + \frac{1}{C} I = 0$$

$$\text{char. eqn is } Lm^2 + Rm + \frac{1}{C} = 0$$

$$\Rightarrow m = \frac{-R \pm \sqrt{R^2 - \frac{4L}{C}}}{2L}$$

$$\boxed{m = \frac{-R}{2L} \pm \frac{1}{2L} \sqrt{R^2 - \frac{4L}{C}}}$$

Q3.

$$I_p = a \cos(\omega t) + b \sin(\omega t)$$

$$I_p' = -a\omega \sin(\omega t) + b\omega \cos(\omega t)$$

$$I_p'' = -a\omega^2 \cos(\omega t) - b\omega^2 \sin(\omega t)$$

Substitute it in ODE in eqn (1) and collect  $\cos(\omega t)$  &  $\sin(\omega t)$  terms, we get

$$\left((-L\omega^2 + \frac{1}{C})a + R\omega b\right) \cos(\omega t) + \left(-R\omega a + (-L\omega^2 + \frac{1}{C})b\right) \sin \omega t = V_0 \omega \cos(\omega t)$$

$$\Rightarrow \left(-L\omega^2 + \frac{1}{C}\right)a + R\omega b = V_0 \omega$$

$$\& -R\omega a + \left(-L\omega^2 + \frac{1}{C}\right)b = 0$$

Let  $S := L\omega - \frac{1}{C\omega}$  (it is known as Impedance)

$$\Rightarrow -Sa + Rb = V_0 \quad \& -Ra - Sb = 0$$

$$\Rightarrow a = \frac{-V_0 S}{R^2 + S^2} \quad \& \quad b = \frac{V_0 R}{R^2 + S^2}$$

Q4.

If  $I_p = a \cos(\omega t) + b \sin(\omega t)$

We want  $I_p = C \sin(\omega t - \delta)$

$$\Rightarrow I_p = C (\sin(\omega t) \cos \delta - \cos(\omega t) \sin \delta)$$

$$\Rightarrow -C \sin \delta = a \quad \& \quad C \cos \delta = b$$

$$\Rightarrow C = \sqrt{a^2 + b^2} \quad \& \quad \delta = \tan^{-1} \frac{a}{b}$$

$$\Rightarrow \boxed{C = \frac{V_0}{\sqrt{R^2 + S^2}} \quad \& \quad \delta = \tan^{-1} \frac{S}{R}}$$

Q5.

From Q2.

$$m = -\frac{R}{2L} \pm \frac{1}{2L} \sqrt{R^2 - \frac{4L}{C}}$$

$$= -\frac{13}{0.6} \pm \frac{1}{0.6} \sqrt{169 - \frac{1.2}{10^{-2}}}$$

$$= \frac{-13 \pm \sqrt{49}}{0.6} = \frac{-13 \pm 7}{0.6}$$

$$\Rightarrow m_1 = -10 \quad \& \quad m_2 = -\frac{100}{3}$$

$$\text{So, } I_h = c_1 e^{-10t} + c_2 e^{-\frac{100}{3}t}$$

For  $I_p$ ,

$$S = L\omega - \frac{1}{C\omega} = 0.3 \times 100\pi - \frac{1}{10^{-2} \times 100\pi} \approx 93.93$$

Then

$$I_p = \frac{110}{\sqrt{13^2 + (93.93)^2}} \sin\left(100\pi t - \tan^{-1} \frac{93.93}{13}\right)$$

$$I_p \approx 1.16 \sin(100\pi t - 82.13^\circ)$$

So, general solution is

$$I(t) = c_1 e^{-10t} + c_2 e^{-\frac{100}{3}t} + 1.16 \sin(100\pi t - 82.13^\circ) \quad \text{--- } (*)$$

We know,  $I(0) = 0$  &  $Q(0) = 0$

$$\text{Since, } LI'(t) + RI(t) + \frac{Q(t)}{C} = V_0 \sin(\omega t)$$

$$I(0) = 0 \quad \& \quad Q(0) = 0 \quad \Rightarrow \quad I'(0) = 0$$

Substituting  $I(0) = 0$  &  $I'(0) = 0$  in  $(*)$ , we obtain

$$c_1 = 0.54 \quad \& \quad c_2 = -1.69$$

Hence,

$$I(t) = 0.54 e^{-10t} - 1.69 e^{-\frac{100}{3}t} + 1.16 \sin(100\pi t - 82.13^\circ)$$