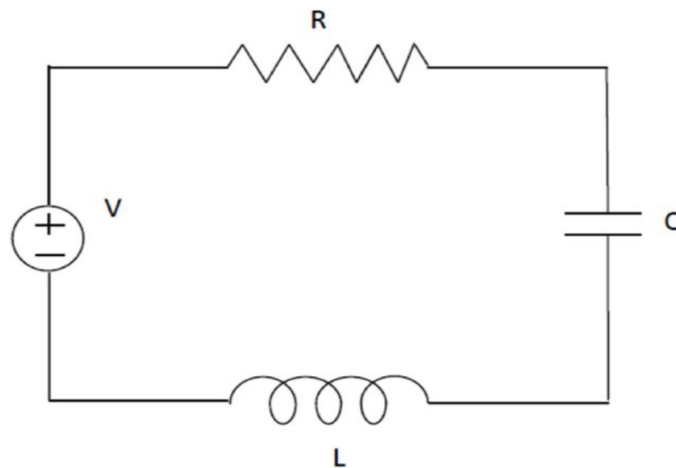


MTH204: Worksheet 6

March 15, 2023

Consider a RLC-circuit



$R \rightarrow$ Resistance (ohm, Ω): Voltage drop $= RI$, $L \rightarrow$ Inductance (Henry, H): Voltage drop $= L \frac{dI}{dt}$,
 $C \rightarrow$ Capacitance (Farad, F): Voltage drop $= \frac{Q}{C}$,
where $I(t)$ is the current in the circuit at any time t , $Q(t)$ is the amount of charge in capacitor at any time t and $V(t)$ is the external voltage provided to circuit. Here, $V(t) = V_0 \sin(\omega t)$.
Relationship in the capacitor between charge and current is $I = \frac{dQ}{dt}$.

1. Write a second order ODE model for the current $I(t)$ in this RLC circuit. (2)
2. Solve the characteristic equation of homogeneous part (find roots in terms of R , L and C). (2)
3. Start with a particular solution

$$I_p = a \cos(\omega t) + b \sin(\omega t),$$

and find a and b .

(2)

4. Write your particular solution found in the previous question as

$$I_p = C \sin(\omega t - \delta).$$

Find C and δ explicitly in terms of V_0 , R , L , C and ω .

(2)

5. Find the current in an RLC circuit with $R = 13\Omega$, $L = 0.3H$, $C = 10^{-2}F$ which is connected to a source of EMF, $V(t) = 110 \sin(100\pi t)$. Assume that current and capacitor charge are 0 at $t = 0$. (2)