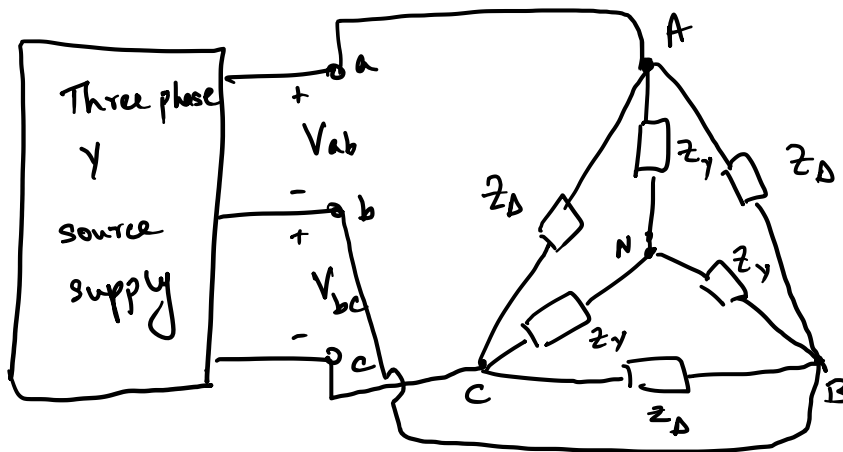


# Set 1

## Quiz 2 (12 marks)

The figure shows a balanced Y-connected load having  $Z_Y = (5 + j5)\Omega$  in parallel with a  $\Delta$ -connected load having  $Z_\Delta = (15 - j9)\Omega$ . The combined load is then connected to a 50Hz three-phase balanced Y- power supply having a line voltage  $V_{ab} = 230\angle 15^\circ$  V. The wire impedance (of each wire) is  $0\Omega$ . Find the following –

- (a) Phase voltages in time-domain
- (b) Line currents in time-domain
- (c) Complex power supplied by the source
- (d) Power factor of the source
- (e) Total time-averaged power consumed by the Y load
- (f) Total time-averaged power consumed by the  $\Delta$  load




## Set 2

### Quiz 2 (12 marks)

The figure shows a 60Hz three-phase balanced Y- power supply having a phase voltage  $V_{an} = 110\angle -15^\circ$  V connected to a balanced Y-connected load having  $Z_Y = (15 - j9)\Omega$  in parallel with a  $\Delta$ -connected load having  $Z_\Delta = (5 + j5)\Omega$ . The wire impedance (of each wire) to the combined load is  $0\Omega$ . Find the following –

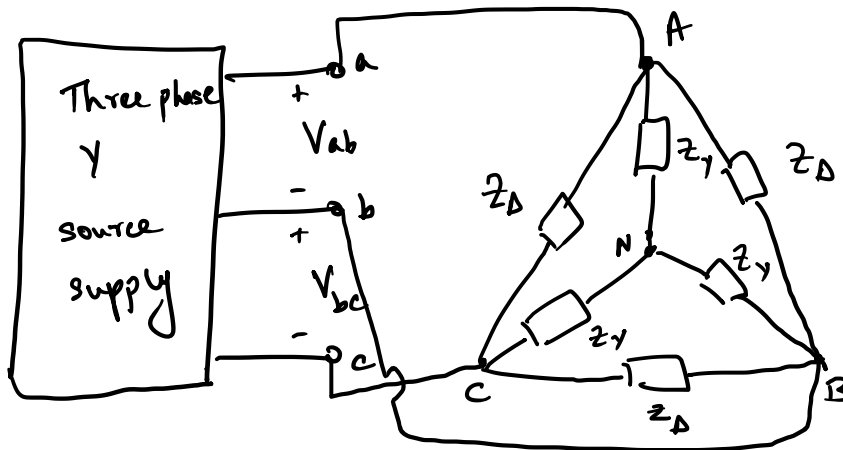- (a) Line voltages in time-domain
- (b) Line currents in time-domain
- (c) Complex power supplied by the source
- (d) Power factor of the source
- (e) Total time-averaged power consumed by the Y load
- (f) Total time-averaged power consumed by the  $\Delta$  load




## Set 3

### Quiz 2 (12 marks)

The figure shows a 60Hz three-phase balanced Y- power supply that provides a time-averaged power 5KW that supplies a line current of  $1\angle+30^\circ$  A connected to a balanced Y-connected load having  $Z_Y = (5 + j5)\Omega$  in parallel with a  $\Delta$ -connected load having  $Z_\Delta = (5 + j5)\Omega$ . The wire impedance (of each wire) to the combined load is  $0\Omega$ . Find the following –

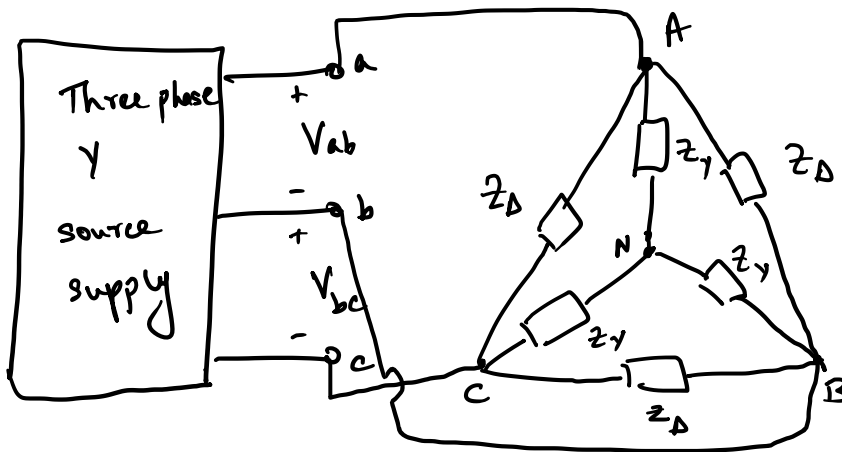- (a) Phase voltages in time-domain
- (b) Line voltages in time-domain
- (c) Power factor of the source
- (d) Reactive power supplied by the source
- (e) Total time-averaged power consumed by the Y load
- (f) Total time-averaged power consumed by the  $\Delta$  load



# Solutions of Set 1

Ques-

$$Z_Y = 5 + j5 \Omega$$

$$Z_\Delta = 15 - j9 \Omega$$

$$V_L = 230 \angle 15^\circ \text{ V}$$

$$V_{AB} = V_L = 230 \angle 15^\circ \text{ V}$$

$$V_{AB} = \sqrt{3} V_{an} \angle 30^\circ \text{ (the phase sequence) i.e (abc sequence)}$$

$$230 \angle 15^\circ = \sqrt{3} V_{an} \angle 30^\circ$$

$$V_{an} = \frac{230}{\sqrt{3}} \angle (15^\circ - 30^\circ) = 132.79 \angle -15^\circ \text{ V}$$

$$V_{bn} = \frac{230}{\sqrt{3}} V_{an} \angle -120^\circ = [132.79 \angle -15^\circ] \angle -120^\circ = 132.79 \angle -135^\circ \text{ V}$$

$$V_{cn} = V_{an} \angle -240^\circ = [132.79 \angle -15^\circ] \angle -240^\circ = 132.79 \angle -255^\circ \text{ V}$$

(a)  $f = 50 \text{ Hz}$   
 $2\pi f = 314$

Phase voltages in time domain,


$$\begin{aligned} V_{an}(t) &= 132.79 \cdot \cos(314t - 15^\circ) \text{ V} \\ V_{bn}(t) &= 132.79 \cdot \cos(314t - 135^\circ) \text{ V} \\ V_{cn}(t) &= 132.79 \cdot \cos(314t - 255^\circ) \text{ V} \end{aligned}$$

(b) Line currents in time-domain

Convert ' $\Delta$ ' load to 'Y' equivalent




$\equiv$

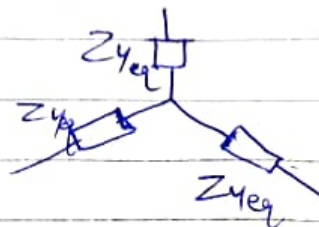

$$Z_{Yeq} = \frac{Z_\Delta}{3}$$

$$Z_{Yeq} = \frac{(15 - j9)}{3} = 5.83 \angle -30.96^\circ$$

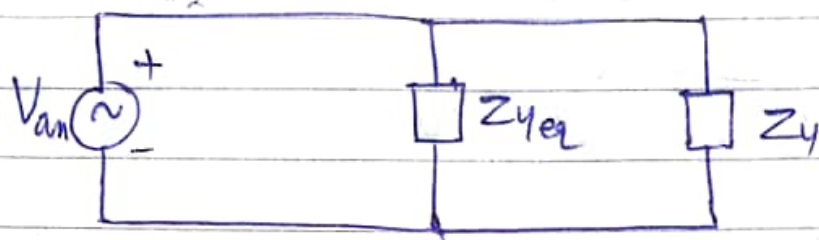using per phase equivalent circuit of an,



$$Z_{Yeq} = 5.83 \angle -30.96^\circ$$


$$Z_Y = 5 + j5 = 7.07 \angle 45^\circ$$

from above ckt,

$$Z_{net} = \frac{(Z_{Yeq})(Z_Y)}{Z_Y + Z_{Yeq}}$$

$$= \frac{(7.07 \angle 45^\circ)(5.83 \angle -30.96^\circ)}{(7.07 \angle 45^\circ) + (5.83 \angle -30.96^\circ)}$$

$$Z_{net} = 4.04 \angle 2.73^\circ$$

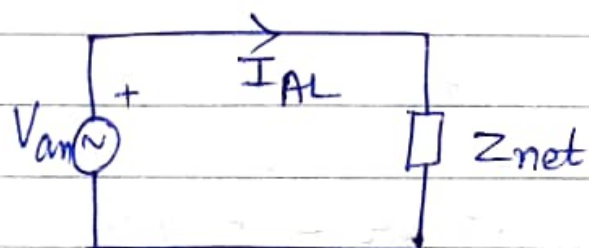

$$\Rightarrow \begin{aligned} V_{an} &= 132.79 \angle -15^\circ \\ Z_{net} &= 4.04 \angle 2.73^\circ \end{aligned}$$

$$\text{So, } I_{AL} = \frac{V_{an}}{Z_{net}} = \frac{132.79 \angle -15^\circ}{4.04 \angle 2.73^\circ}$$

$$I_{AL} = 32.87 \angle -17.73^\circ \text{ A}$$

Now,

$$I_{BL} = I_{AL} \angle -120^\circ = 32.87 \angle -137.73^\circ \text{ A}$$

$$I_{CL} = I_{AL} \angle -240^\circ = 32.87 \angle -257.73^\circ \text{ A}$$



Line currents in time-domain are,

$$\begin{aligned} I_{AL} &= 32.87 \cdot \cos(314t - 17.73^\circ) \text{ A} \\ I_{BL} &= 32.87 \cdot \cos(314t - 137.73^\circ) \text{ A} \\ I_{CL} &= 32.87 \cdot \cos(314t - 257.73^\circ) \text{ A} \end{aligned}$$

$$\begin{aligned} (c) \quad S_{3\phi} &= \sqrt{3} V_L I_L^* \\ &= \sqrt{3} \times (230 \angle 15^\circ) \times (32.87 \angle -17.73^\circ)^* \\ &= \sqrt{3} \times (230 \angle 15^\circ) \times (32.87 \angle 17.73^\circ) \end{aligned}$$

$$S_{3\phi} = 13094.47 \angle 32.73^\circ$$

→ complex power supplied by the source.


(d) Power factor of the source,

$$\begin{aligned} \text{Power factor} &= \cos(32.73^\circ) \text{ lag.} \\ \boxed{\text{P.F} &= 0.841 \text{ lag}} \end{aligned}$$

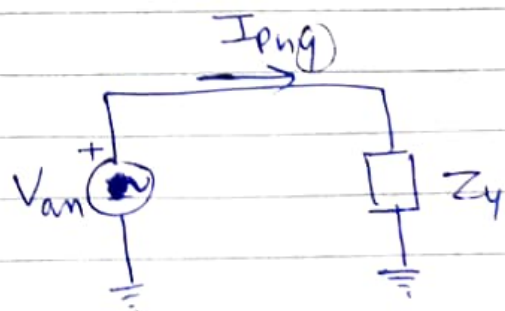(e) Total time-averaged power consumed by the Y-load,  
for Y-load.

$$V_{an} = 132.79 \angle -15^\circ \text{ V}$$

$$\begin{aligned} I_{ph(Y)} &= \frac{V_{an}}{Z_Y} \\ &= \frac{132.79 \angle -15^\circ}{7.07 \angle 45^\circ} \\ &= 18.78 \angle -60^\circ \end{aligned}$$



$$\begin{aligned} Z_Y &= 5 + j5 \\ &= 7.07 \angle 45^\circ \end{aligned}$$

$$S_{1\phi} (Y \text{ load}) = \overline{V_{an}} \cdot \overline{I_{an}}^* \\ = (132.79 \angle -15^\circ) (18.78 \angle -60^\circ)$$


$$S_{1\phi} = 2493.79 \angle -75^\circ \text{ KVA}$$

$$P_{1\phi} = 2493.79 \cos(75^\circ) = 645.44 \text{ W}$$

$$P_{3\phi} = 3 \times P_{1\phi} = 3 \times 645.44 \text{ W}$$

$$P_{3\phi} = 1936.32 \text{ W}$$

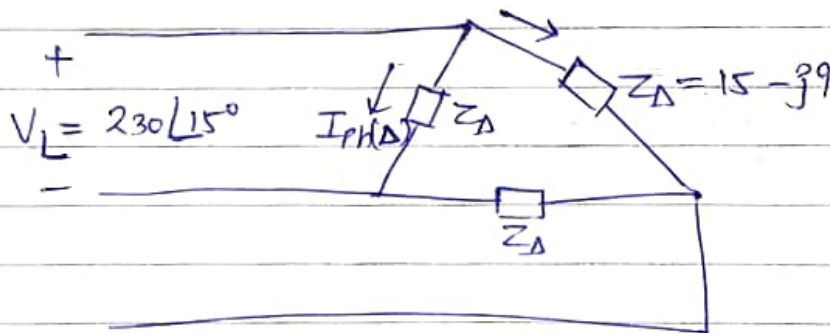(7) Total time-averaged power consumed by the  $\Delta$ -load,



$$I_{ph(\Delta)} = \frac{230 \angle 15^\circ}{Z_{\Delta}} = \frac{230 \angle 15^\circ}{15 - j9} = 13.14 \angle 45.96^\circ \text{ A}$$

$$S_{1\phi} = V_{ph} \cdot I_{ph}^* = (230 \angle 15^\circ) (13.14 \angle 45.96^\circ)^* \\ = (230 \angle 15^\circ) (13.14 \angle -45.96^\circ) \\ = 3022.2 \angle -30.96^\circ$$

$$P_{1\phi} = 3022.2 \cdot \cos(30.96^\circ)$$

$$P_{3\phi} = 3 \times P_{1\phi} = 3 \times 3022.2 \cdot \cos(30.96^\circ)$$

$$P_{3\phi} = 7774.85 \text{ W}$$

## SET 2 SOLUTIONS

Given,

$$\text{Phase voltage } V_{an} = 110 \angle -15^\circ \text{ V}$$

$$Z_Y = (15 - j9) \Omega$$

$$Z_\Delta = (5 + j5) \Omega$$

a) line voltages in time domain:

We know,

$$V_{ab} = \sqrt{3} V_{an} \angle 30^\circ \text{ (the phase sequence } \rightarrow abc)$$

$$\begin{aligned} \Rightarrow V_{ab} &= \sqrt{3} \times (110 \angle -15^\circ) \text{ V} \\ &= \boxed{190.52 \angle -45^\circ \text{ V}} \end{aligned}$$

$$V_{bc} = V_{ab} \angle -120^\circ$$

$$= \boxed{190.52 \angle -165^\circ \text{ V}}$$

$$V_{ca} = V_{ab} \angle -240^\circ$$

$$= \boxed{190.52 \angle -285^\circ \text{ V}}$$

$$f = 50 \text{ Hz}$$

$$\omega = 2\pi f = 314 \text{ rad/s}$$



∴ line voltage in time domain are-

$$V_{ab}(t) = 190.52 \cos(314t - 45^\circ) \text{ V}$$

$$V_{bc}(t) = 190.52 \cos(314t - 165^\circ) \text{ V}$$

$$V_{ca}(t) = 190.52 \cos(314t - 285^\circ) \text{ V}$$

b) line currents in time domain:

$$Z_{Yeq} = \frac{Z_\Delta}{3}$$

$$Z_{Yeq} = \frac{5 + j5}{3} = 2.35 \angle 45^\circ \Omega$$

$$Z_Y = 15 - j9 = 17.49 \angle -30.96^\circ \Omega$$

$$\therefore Z_{net} = (Z_{Yeq} \parallel Z_Y)$$

$$= \frac{Z_{Yeq} (Z_Y)}{(Z_Y) + (Z_{Yeq})}$$

$$= \frac{(2.35 \angle 45^\circ)(17.49 \angle -30.96^\circ)}{(2.35 \angle 45^\circ) + (17.49 \angle -30.96^\circ)}$$

$$Z_{net} = 2.25 \angle -9.72^\circ \Omega$$

$$\text{Now, } I_{aL} = \frac{V_{an}}{Z_{eq}}$$

$$= \frac{160 \angle -15^\circ}{2.25 \angle -9.72^\circ}$$

$$= 48.8 \angle -5.28^\circ \text{ A.}$$

$$I_{bL} = I_{aL} \angle -120^\circ$$

$$= 48.8 \angle -5.28 - 120^\circ$$

$$= 48.8 \angle -125.28^\circ \text{ A.}$$

$$I_{cL} = I_{aL} \angle -240^\circ$$

$$= 48.8 \angle -245.28^\circ \text{ A}$$

In time domain,

$$I_{aL} = 48.8 \cos(314t - 5.28^\circ) \text{ A}$$

$$I_{bL} = 48.8 \cos(314t - 125.28^\circ) \text{ A}$$

$$I_{cL} = 48.8 \cos(314t - 245.28^\circ) \text{ A.}$$

c) Complex power supplied by source

$$= S_{3\phi} = \sqrt{3} V_L I_L^*$$

$$= \sqrt{3} \times (190.52 \angle 45^\circ) \times 82 \angle (-48.8 \angle +5.28^\circ)$$

$$S_{3\phi} = 16103.5 \angle -39.72^\circ \text{ VA.}$$

d) Power factor of source -

$$PF = \cos(-39.72^\circ)$$

$$= 0.769$$

e) Total time averaged power consumed by  
Y load

$$V_{cn} = 110 \angle -15^\circ \text{ V}$$

$$I_{ph_Y} = \frac{V_{cn}}{Z_Y} = \frac{110 \angle -15^\circ}{17.49 \angle -30.96^\circ} = 6.28 \angle 15.96^\circ$$

$$\text{Now, } S_{1\phi} = V_{cn} \cdot I_{cn}^*$$

$$= (110 \angle -15^\circ) (6.28 \angle 15.96^\circ)$$

$$= 690.8 \angle 30.96^\circ \text{ VA}$$

$$\therefore P_{1\phi} = 690.8 \times \cos(30.96^\circ) = 592.3 \text{ W}$$

$$P_{3\phi} = 3 \times P_{1\phi} = 1776.9 \text{ W}$$

f) Power by  $\Delta$ -load.

c Total time averaged power consumed by  $\Delta$

$$I_{Ph \Delta} = \frac{190.52 \angle -45^\circ}{85 + j35} = \frac{190.52 \angle -45^\circ}{7.07 \angle 45^\circ}$$

$$\therefore S_{1q} = (190.52 \angle -45^\circ) \times (\cancel{4} 26.94 \angle +90^\circ)$$

$$= 5132.6 \text{ L} \text{ } \cancel{\text{kg}} \text{ } \frac{\text{m}^3}{\text{kg}} \text{ } \frac{\text{VA}}{\text{m}^3}$$

$$\therefore P_{\text{eq}} = 5132.6 \text{ W} (45^\circ)$$

$$= 3628.8 \text{ W}$$

$$P_{30} = 3 \times 3628.8 \text{ W}$$

$$= 10806.4 \text{ W}$$

\_\_\_\_\_

# SET-3 Solutions


(1.)

given:  $f = 60 \text{ Hz}$   
 $P = 5 \text{ kW}$   
 $I_L = 1 \angle 30^\circ \text{ A}$

$$Z_Y = 5 + j5 \Omega = 7.07 \angle 45^\circ \Omega$$

$$Z_A = 5 + j5 \Omega = 7.07 \angle 45^\circ \Omega$$

$$Z_{\text{wire}} = 0 \Omega$$

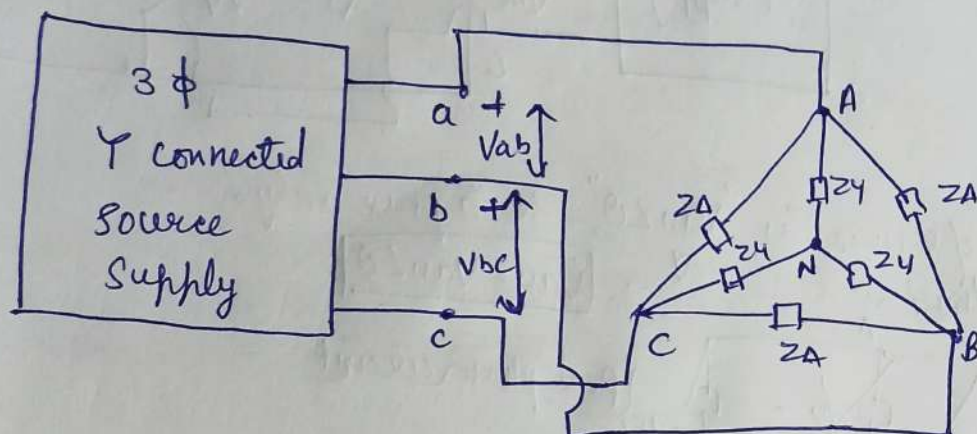


(a) For phase voltages [We can find the phase voltages via 2 ways]

Method-①


Here since all  $Z_Y$  and  $Z_A$  are equal so they are in balanced state. Also source is also balanced. In this configuration we can perform per phase analysis to find phase voltages.

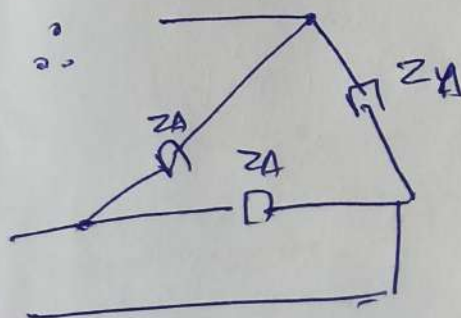Problem is ~~only~~ this in doing per phase analysis is that it can be done when both loads are connected in Y configuration only. But in question one load is  $\Delta$  and other is Y.

So convert  $\Delta$  load to Y equivalent so that per phase analysis can be performed.





equivalent  
Y conn.

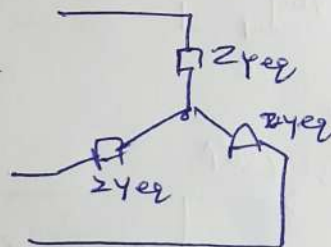

(Here  $Z_{Yeq}$  is equivalent Y of  $\Delta$  load)

$$\therefore Z_{Yeq} = \frac{Z_A \times Z_A}{Z_A + Z_A + Z_A}$$

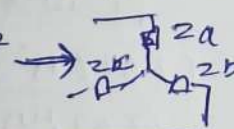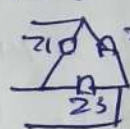Using  $\Delta \rightarrow Y$  conversion formula



$$Z_A = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$$



$$\text{As } Z_1 = Z_2 = Z_3 = Z_A$$

$$\text{So } Z_A = Z_b = Z_c$$



$$Z_{Yeq} = \frac{Z_Y}{3} = \frac{5 + j5}{3} = 2.35 \angle 45^\circ \Omega$$




$\therefore$  

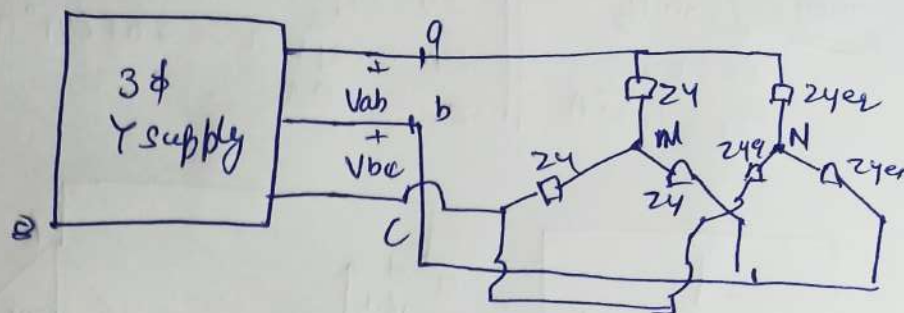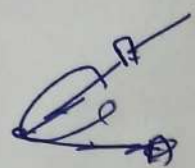

Let phase supply of source is " $V_{an} \angle 0^\circ$ " for 'a' phase only.


$\therefore$  For 'b' phase  ~~$V_{bn} \angle -120^\circ$~~

$$V_{an} = V_{an} \angle 0^\circ$$

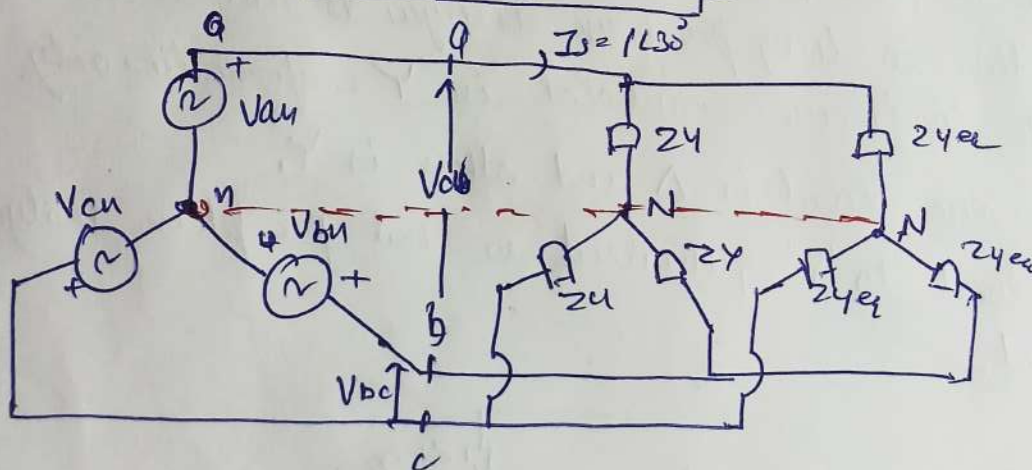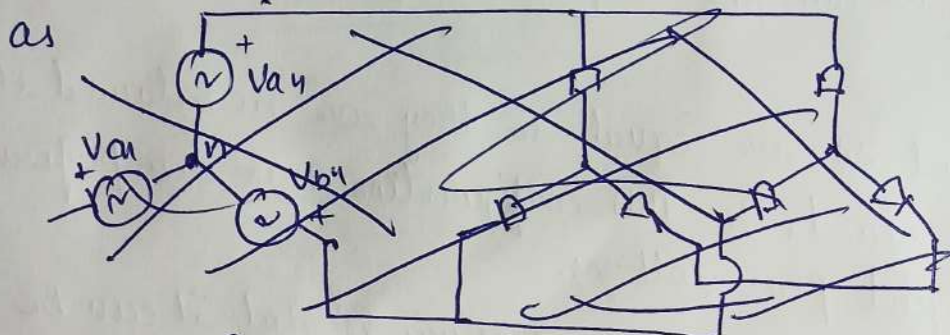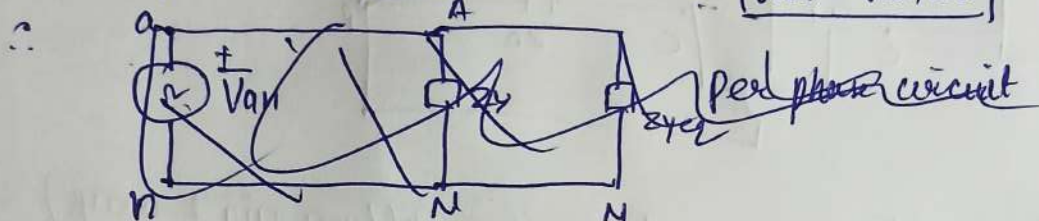


Now (n, N) can be connected for per phase analysis

$\Rightarrow$  Per phase ckt is

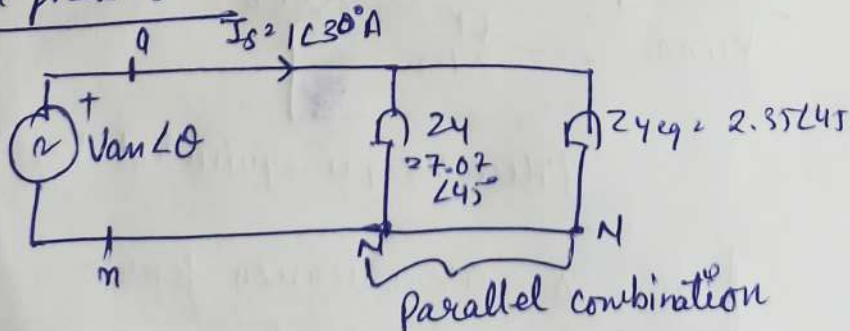

$$Z = \frac{Z_Y \cdot Z_{Yeq}}{Z_Y + Z_{Yeq}} = \frac{(7.07 \angle 45^\circ)(2.35 \angle 45^\circ)}{(7.07 \angle 45^\circ) + (2.35 \angle 45^\circ)} = 1.76 \angle 45^\circ$$

>

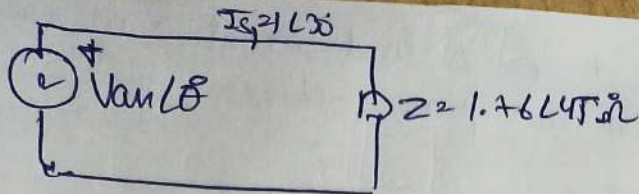

$$\therefore V_{anL0} = \vec{I}_S Z = (1\angle30^\circ)(1.76\angle45^\circ) = 1.76\angle75^\circ \text{ V}$$


$$\therefore V_{bn} = V_{an} \angle -120^\circ = (1.76\angle75^\circ) \angle -120^\circ = 1.76\angle-45^\circ \text{ V}$$

$$V_{cn} = V_{an} \angle -240^\circ = 1.76\angle75^\circ \angle -240^\circ = 1.76\angle-165^\circ \text{ V}$$


$$\text{As } f = 60 \text{ Hz} \therefore \omega = 2\pi f = 120\pi \text{ rad/sec}$$

$$\therefore \left. \begin{aligned} V_{an}(t) &= 1.76 \cos(120\pi t + 75^\circ) \text{ V} \\ V_{bn}(t) &= 1.76 \cos(120\pi t - 45^\circ) \text{ V} \\ V_{cn}(t) &= 1.76 \cos(120\pi t - 165^\circ) \text{ V} \end{aligned} \right\} \text{ are Required phase voltages in Time Domain}$$

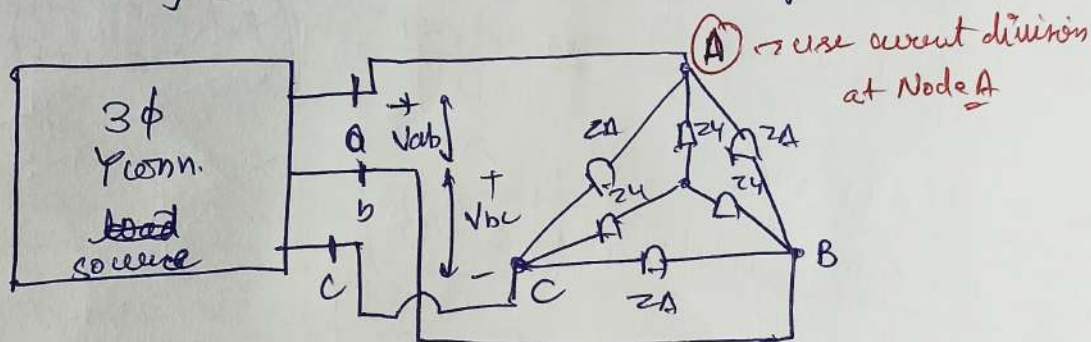Method 2 : Using current division at Node A of the load.



Make full ckt of source + loads

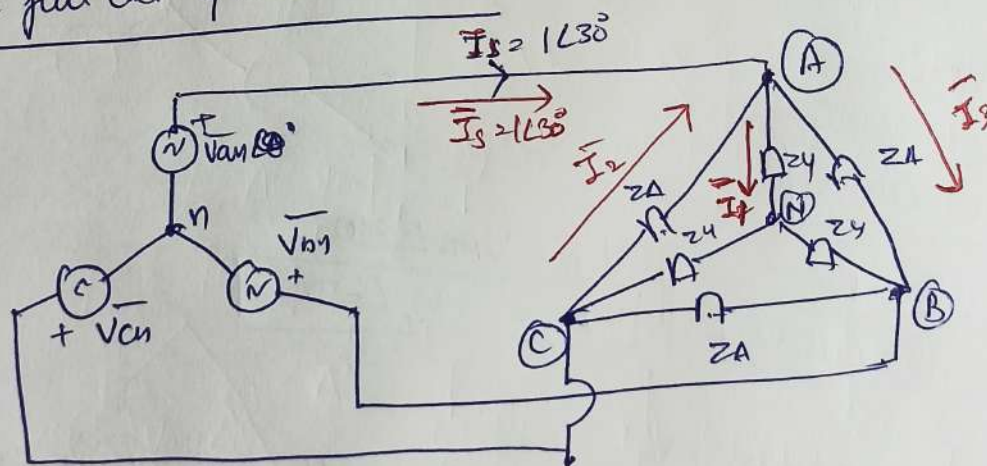

Using KCL:  $\vec{I}_S + \vec{I}_2 = \vec{I}_1 + \vec{I}_3$

$$\vec{I}_S = \vec{I}_1 + \vec{I}_3 - \vec{I}_2$$

Now for  $\vec{I}_1$   $\Rightarrow \vec{I}_1 = \frac{\vec{V}_{an}}{Z_Y}$

(as  $\vec{I}_1$  is phase current in (AN) : Use phase voltage only as its Y connection)



For  $\underline{I_2}$  :  $\underline{I_2} = \frac{\underline{V_{CA}}}{Z_A}$  || Here it's  $\Delta$  load current  $\therefore$  We use line voltage  
 $\underline{V_{CA}}$  not phase voltage.

Also we know :  $\underline{V_{AB}} = \sqrt{3} \underline{V_{an}} \angle 30^\circ$

and  $\underline{V_{CA}} = \underline{V_{AB}} \angle -240^\circ = \sqrt{3} \underline{V_{an}} \angle -240^\circ + 30^\circ$

$\underline{V_{CA}} = \sqrt{3} \underline{V_{an}} \angle -210^\circ \text{ V}$

$\therefore \underline{I_2} = \frac{\sqrt{3} \underline{V_{an}} \angle -210^\circ}{Z_A}$

For  $\underline{I_3}$  :  $\underline{I_3} = \frac{\underline{V_{AB}}}{Z_A} = \frac{\sqrt{3} \underline{V_{an}} \angle 30^\circ}{Z_A}$  (as  $\underline{V_{AB}} = \sqrt{3} \underline{V_{an}} \angle 30^\circ$ )

Now use  $\underline{I_1}, \underline{I_2}, \underline{I_3}$  values in KCL eqn:

$\underline{I_S} = \underline{I_1} + \underline{I_3} - \underline{I_2}$

$1 \angle 30^\circ = \frac{\underline{V_{an}}}{5+j5} + \frac{\sqrt{3} \underline{V_{an}} \angle 30^\circ}{5+j5} - \frac{\sqrt{3} \underline{V_{an}} \angle -210^\circ}{5+j5}$  (Put  $Z_Y = 5+j5$   
 $Z_A = 5+j5$ )

$\underline{V_{an}} = 1.76 \angle 75^\circ \text{ V}$  as

$\therefore \underline{V_{bn}} = 1.76 \angle -45^\circ$  and  $\underline{V_{cn}} = 1.76 \angle -165^\circ$

b. For line voltages

$\underline{V_{AB}} = \sqrt{3} \underline{V_{an}} \angle 30^\circ$   
 $= \sqrt{3} [1.76 \angle 75^\circ] \angle 30^\circ$

$\underline{V_{AB}} = 3.05 \angle 105^\circ \text{ V}$

and  $\underline{V_{BC}} = \underline{V_{AB}} \angle -120^\circ$   
 $\underline{V_{BC}} = 3.05 \angle -15^\circ \text{ V}$

$\underline{V_{CA}} = \underline{V_{AB}} \angle -240^\circ$   
 $\underline{V_{CA}} = 3.05 \angle -135^\circ$

$\therefore \underline{V_{AB}} = 3.05 \cos(120\pi t + 105^\circ) \text{ V}$   
 $\underline{V_{BC}} = 3.05 \cos(120\pi t - 15^\circ) \text{ V}$   
 $\underline{V_{CA}} = 3.05 \cos(120\pi t - 135^\circ) \text{ V}$

} Line voltages in Time Domain

c. For power factor of source

$\text{P.f.} = \cos(\theta - \phi) = \cos(75^\circ - 30^\circ)$   
 $= \cos 45^\circ = \frac{1}{\sqrt{2}} = 0.707 \text{ lag.}$

Here  $\theta = 75^\circ$  (angle of  $\underline{V_{an}}$ )  
 $\phi = 30^\circ$  (angle of  $\underline{I_S}$ )

d. for reactive power


$$Q = P \tan(\theta - \phi) \quad \text{[and } P = 5 \text{ kW and } \theta - \phi = 75^\circ - 30^\circ = 45^\circ]$$

$$= 5 \tan 45^\circ$$

$$\boxed{Q = 5 \text{ KVARs}} \quad \text{Q}$$

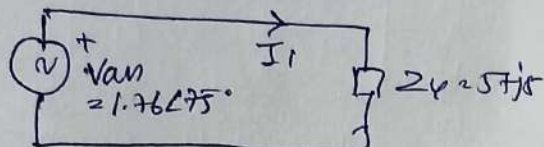e. for average power consumed by Y load

using per phase ckt for (Y) load only (not Δ load)



$$I_1 = \frac{V_{ph}}{Z_Y} = \frac{1.76 \angle 75^\circ}{5 + j5} = 0.25 \angle 30^\circ \text{ A}$$

$$\therefore P_{3\phi} = \frac{3}{2} V_m I_m \cos(\theta - \phi)$$

$$\left\| \begin{array}{l} I_m = I_1 \\ V_m = V_{ph} \end{array} \right. \quad \text{(and they are phase voltage and current)}$$


$$= \frac{3}{2} \times 1.76 \times 0.25 \cos(75^\circ - 30^\circ) = 0.466 \text{ W}$$

$$\boxed{P_{3\phi} = 0.466 \text{ W}}$$

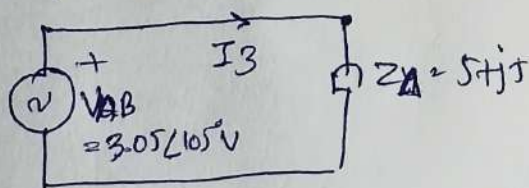f. for Average power consumed in Δ load

use per phase ckt for (Δ) load only

Here as it's Δ load so we take line voltage of source as  $V_m$  as line and phase voltage of Δ connection are equal.



$$I_3 = \frac{V_{AB}}{Z_{\Delta}} = \frac{3.05 \angle 105^\circ}{5 + j5} = 0.43 \angle 60^\circ$$

$$\therefore P_{3\phi} = \frac{3}{2} V_m I_m \cos(\theta - \phi)$$

$$= \frac{3}{2} \times 0.43 \times 3.05 \cos(105^\circ - 60^\circ)$$

$$\left\| \begin{array}{l} V_m = V_{AB} = 3.05 \text{ V} \\ I_m = 0.43 \text{ A} \\ \theta = 105^\circ \\ \phi = 60^\circ \end{array} \right.$$

$$\boxed{P_{3\phi} = 1.39 \text{ W}} \quad \text{a.c.}$$