


DVD Quiz 7

Total marks =10

Instructions


1. This is a take-home quiz, with no compulsion to join the meeting, but please ask your doubts in the meeting itself.
 2. The quiz duration is **25 mins and 10 mins** extra given to upload your scanned PDFs (high quality) on the google classroom. Upload answer PDF on classroom
 3. The quiz starts at **8:00 PM** sharp and ends at 8:20 PM. 10 minutes are reserved for scanning and uploading the quiz to Google Classroom, any submission after **8:35 PM** will attract a penalty
 4. Meeting link for doubts: <https://meet.google.com/gyd-cecr-tez>
-

 Q1. Explain back gate coupling using the below circuit (2 marks) with waveform (1 mark), and how it can be avoided (1 mark)? (4 marks)



ANS.

In the above circuit, a dynamic NAND gate drives a static NAND gate. The gate-to-source capacitance C_{gs1} of N1 is shown explicitly. Suppose that the dynamic gate is in the evaluation and its output X is floating high. The other input B to the static NAND gate is initially low. Therefore, the NAND output Y is high and the internal node W is charged up to $V_{DD} - V_{tn}$. At some time B rises, discharging Y and W through transistor N2. The source of N1 falls. This tends to bring the gate along for the ride because of the C_{gs1} capacitance, resulting in a drop on the dynamic node X. As with charge sharing, the magnitude of the drop depends on the ratio of C_{gs1} to the total capacitance on node X. (2 marks)

 

(1 mark)



Back-gate coupling is eliminated by driving the input closer to the rail. For example, if X drove N2 instead of N1, the problem would be avoided. Otherwise, the back-gate coupling noise must be included in the dynamic noise budget. (1 mark)

Q2. One of the partitions on SoC is operating at high frequency (>Mhz) while another partition is working on very low frequency, you have to design a circuit for the same. Explain briefly where you use dynamic logic style and why? (2 mark)

ANS- we use dynamic logic for high-frequency partition because...


During the evaluation phase, when the pull-down network is not ON, then leakage current exists in the form of the reverse-biased diode and subthreshold leakage, if the frequency is high then the output node discharges less compared to when the frequency is low if the change in V_{out} is larger than the $|V_{tp}|$ of static inverter following the dynamic gate, there exists a short circuit current in the static inverter which further increases the power consumption. That's why we avoid using dynamic gates in low-frequency operations.

Q3. If $V_{tn}=|V_{tp}|=0.5\text{V}$ and V_{DD} is 2.5 V then complete the waveform of the X, Y and Z node for the below circuit (2 marks) and verify it mathematically (2 marks) {overall 4 marks}

  

ANS:

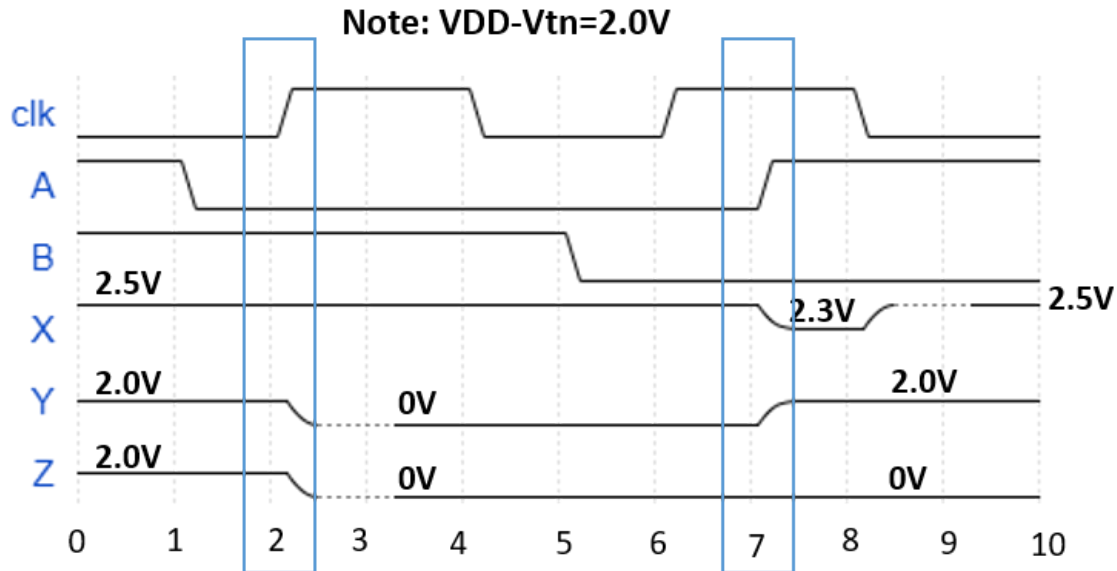The waveform of the desired node is shown below. (2 marks)



Mathematical explanation (2 marks)

At time $t=0$

$$A=B=2.5V$$

Along with node X, internal nodes Y and Z will be precharged to $(V_{DD}-V_{tn})$

At time $t=2$

$$A=0V \quad B=2.5V$$

VY remains at 2.5V while internal nodes discharge to 0V.

At time $t=7$

For the case when V_x is at V_{DD} while V_y is at zero and input A is “2.5V” and $B=0V$, there are two possibilities.

1) When $\Delta V_{out} < V_{tn}$

$$V_y = (V_{DD}-V_{tn})$$

$$\Delta V_{out} = - (C_a/C_L) * \{V_{DD}-V_{tn}\} \text{ -----(1)}$$

2) When $\Delta V_{out} > V_{tn}$

$$\Delta V_{out} = - \{C_a/(C_a + C_L)\} * V_{DD} \text{ -----(2)}$$

Which of the above scenario is valid is determined by the capacitance ratio, boundary condition between two cases can be determined by setting ΔV_{out} equals to V_{tn} , putting $\Delta V_{out} = V_{tn}$ in any of the above equations gives you.

$$C_a/C_L = V_{tn}/(V_{DD}-V_{tn}) \text{ -----(3)}$$

If $C_a/C_L < V_{tn}/(V_{DD}-V_{tn})$ then equation 1 holds while if $C_a/C_L > V_{tn}/(V_{DD}-V_{tn})$ then equation 2 holds.

Now,

$$C_a/C_L = 0.1$$

$$V_{tn}/(V_{DD}-V_{tn}) = 0.5/2 = 0.25$$

Since $C_a/C_L < V_{tn}/(V_{DD}-V_{tn})$, Therefore equation 1 hold true.

$$V_Y = V_{DD} - V_{tn} = 2.0V$$

While

$$\Delta V_{out} = - (C_a/C_L) * \{V_{DD} - V_{tn}\} = - 2.0/10 = -0.2V$$

$$V_Y = 2.3V$$