

Assignment -3

Basic Electronics (BE): ECE113

Winter-2023

Release: 9-May-2023 (7:00 PM)

Submission: 16-May-2023 (7:00 PM)

Instructions

- **Institute Plagiarism Policy Applicable.** This will be subjected to strict plagiarism check.
- This assignment should be attempted individually.
- A maximum point for this assignment is 40. All questions are compulsory.
- **File Submission:** Only a .pdf file are acceptable, which you have to submit on Google Classroom. Use A4 size sheets only (ruled or blank) to solve your assignment and scan it to create a .pdf file. Attempt each question on a different sheet. Do not start a new question at the back of the previous one. Do not forget to mention Page Number (bottom center) clearly on each sheet of the assignment. Submit a .pdf file named *A1_RollNo.pdf* (e.g., *A1_PhD22100.pdf*), which containing the quality scan copy of your solved assignment.
- **Submission Policy:** Turn-in your submission as early as possible to avoid late submissions. In case of multiple submissions, the latest submission will be evaluated. Expect **No Extensions**. Late submissions will not be evaluated and hence will be awarded zero marks strictly.
- **Clarifications:** Symbols have their usual meaning. Assume the missing information & mention it in the report. Use Google Classroom for any queries. In order to keep it fair for all, no email queries will be entertained.
- There could be multiple ways to approach a question. Please justify your answers. Questions without justification will get zero marks.

Question-1: In the given following circuit (Figure-1), the switch is opened initially and it is closed at time $t=0$ sec then find the values of following things- (1) $I_1(0^+)$ (2) $I_2(0^+)$ (3) $I_1(\infty)$ (4) $I_2(\infty)$ (5) $V_C(0^+)$ (6) $[d/dt]I_1(0^+)$ (7) $[d/dt]I_2(0^+)$ (8) $[d^2/dt^2]I_1(0^+)$ (9) $[d^2/dt^2]I_2(0^+)$. [5 Points]

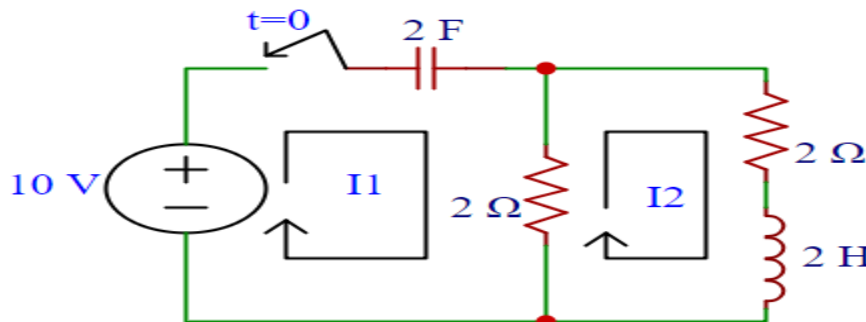


Figure 1

Question-2: In the given following circuit (Figure-2), the initial voltage and current across capacitor and inductor are zero. The switch is closed at time $t=0$ sec and remain with that position then find out the value of following things- (1) $I_C(0^+)$ (2) $V_L(0^+)$ (3) $[d/dt]I_L(0^+)$ (4) $[d/dt]V_C(0^+)$. [5 Points]

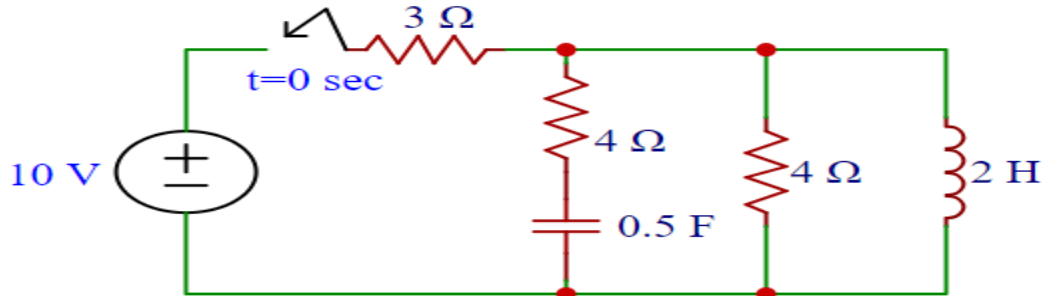


Figure 2

Question-3: In the given following circuit (Figure-3), the input voltage is given by $V_i(t) = [e^{-j200t} + 2e^{-j(500t - \pi/2)} + e^{j200t} - 2e^{j(500t + \pi/2)}]$ volt then find out the value of $V_o(t)$ (in polar form). [5 Points]

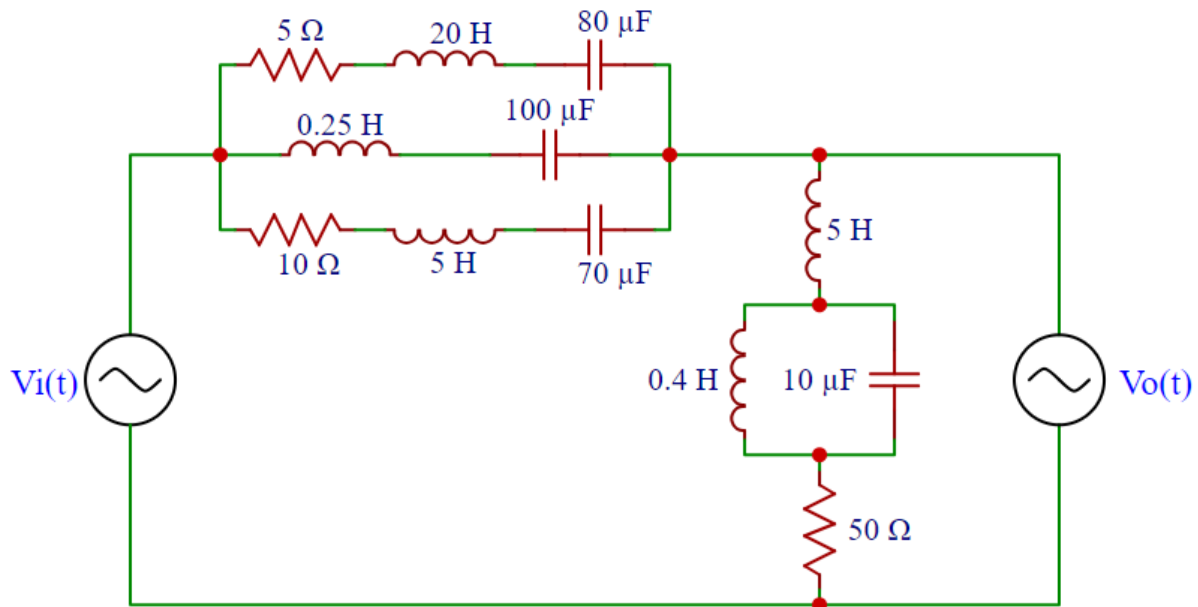


Figure 3

Question-4: In the given following circuit (Figure-4), it is given that the current (I) flowing through 100Ω resistor is zero. Then the find out the value of unknown capacitor ' C ' (in μF), where all the symbol have their usual meaning. [5 Points]

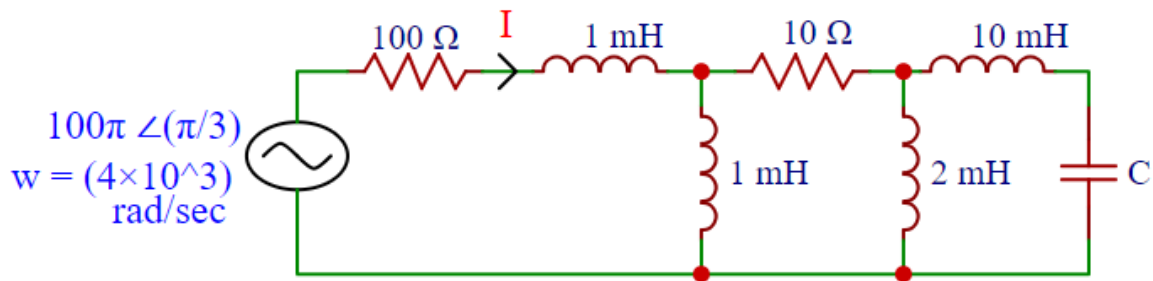


Figure 4

Question-5: In the given following circuit (Figure-5), if the value of source voltage $V_s = 80 \angle 60^\circ$ volt then find out the of Thevenin's equivalent voltage (V_{th}), Norton equivalent current (I_N) and Thevenin's equivalent resistor (R_{th}) as seen by the load inductive reactance $X_0 = 6 \Omega$. [5 Points]

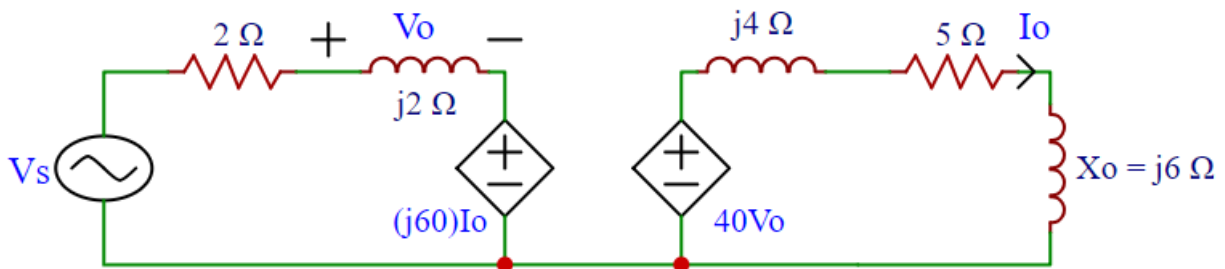


Figure 5

Question-6: In the given following circuit (Figure-6), if value of $V_a = 100 \angle 60^\circ$ volt, $V_b = 80 \angle 40^\circ$ volt and $V_c = 40 \angle 20^\circ$ volt then find the value of load impedance $Z_L (=R_L + jX_L)$, so that maximum power dissipation in the load impedance occurs. [2.5 points]

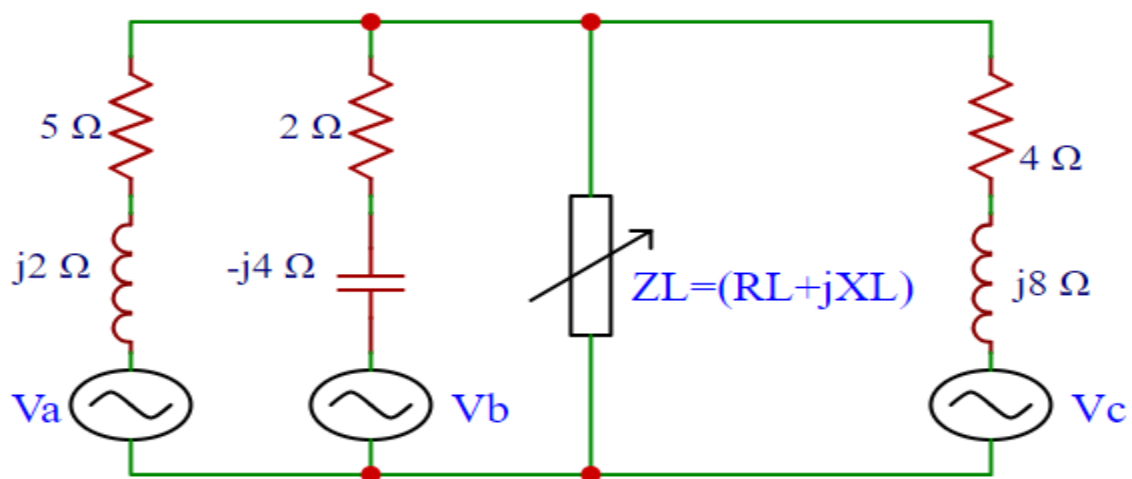


Figure 6

Question-7: In the given following circuit (Figure-7), find the value of resonance frequency (f_0) (in Hz) of the circuit- [5 Points]

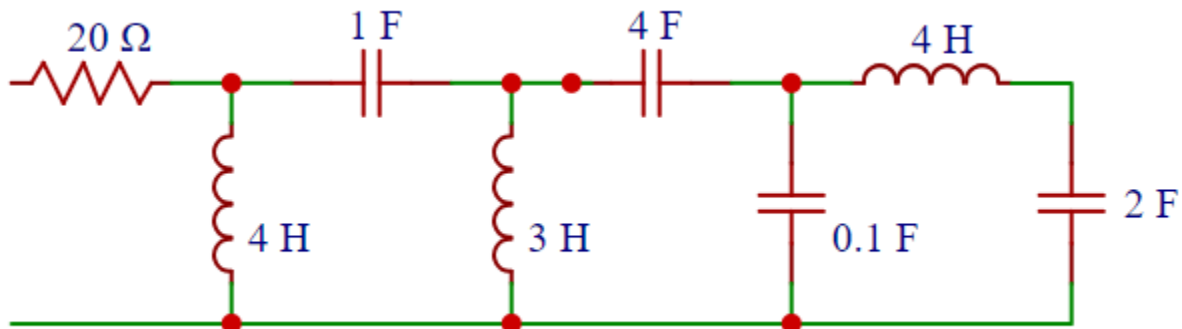


Figure 7

Question-8: In the given following circuit (Figure-8), if $V_c = 40 \sin(1000t + 60^\circ)$ volt and $V_d = 60 \sin(1000t - 40^\circ)$ volt then find out the value of- (a) V_a and V_b by using nodal analysis only (b) I_a , I_b and I_c by using mesh analysis only. Represent the answers in Polar form, Time domain form & rectangular form. [7.5 Points]

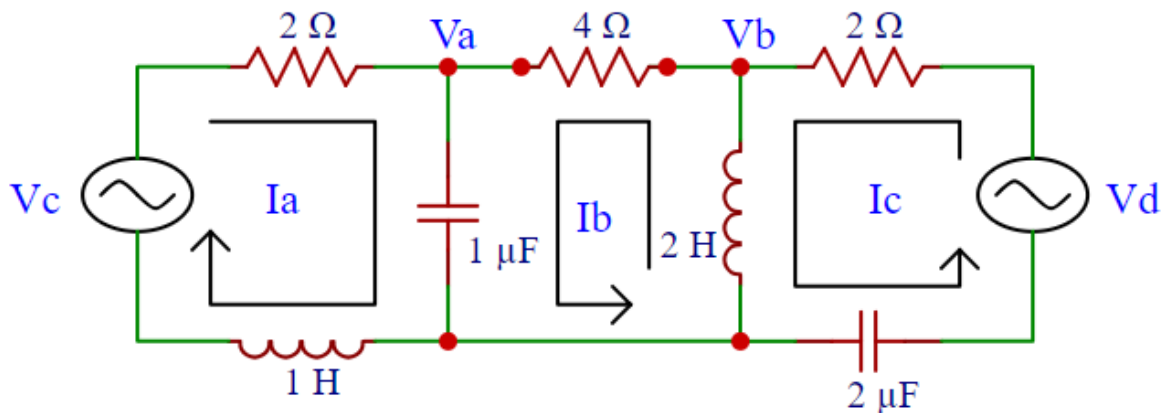


Figure 8