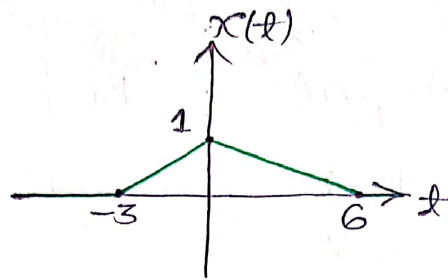



# Re Quiz - 1 Rubric

SOL (1) :-


First we need to draw signal/current,  $i(t) = x(-2t+1)$



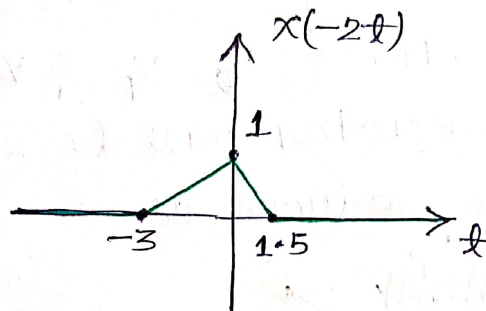Time Scaling  
+  
Time Reversal  
operation



Time Shifting  
operation

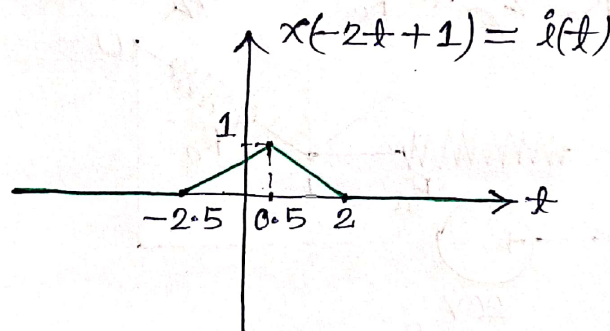

— (2 Marks)

as we know that —  $Q = \int_{-\infty}^{\infty} i(t) \cdot dt$

$$= \int_{-2.5}^2 i(t) \cdot dt$$


= area of  $i(t)$  signal

$$= \frac{1}{2} \times 4.5 \times 1$$

$$= 2.25 \text{ C}$$


— (3 Marks)

# SOL(2) :-

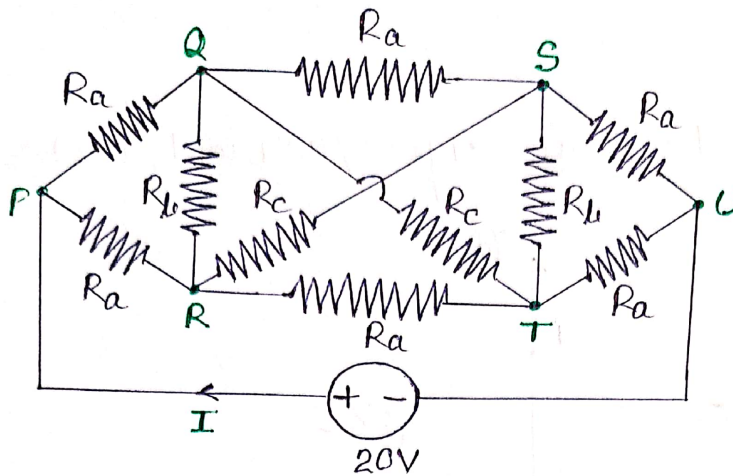

As the given network is symmetric network w.r.t. 20V voltage source. Hence  $V_Q = V_R$  &  $V_S = V_T$ . So current through both  $R_b$  resistors will be zero. -(1 Marks)

Now network can be reduced as -

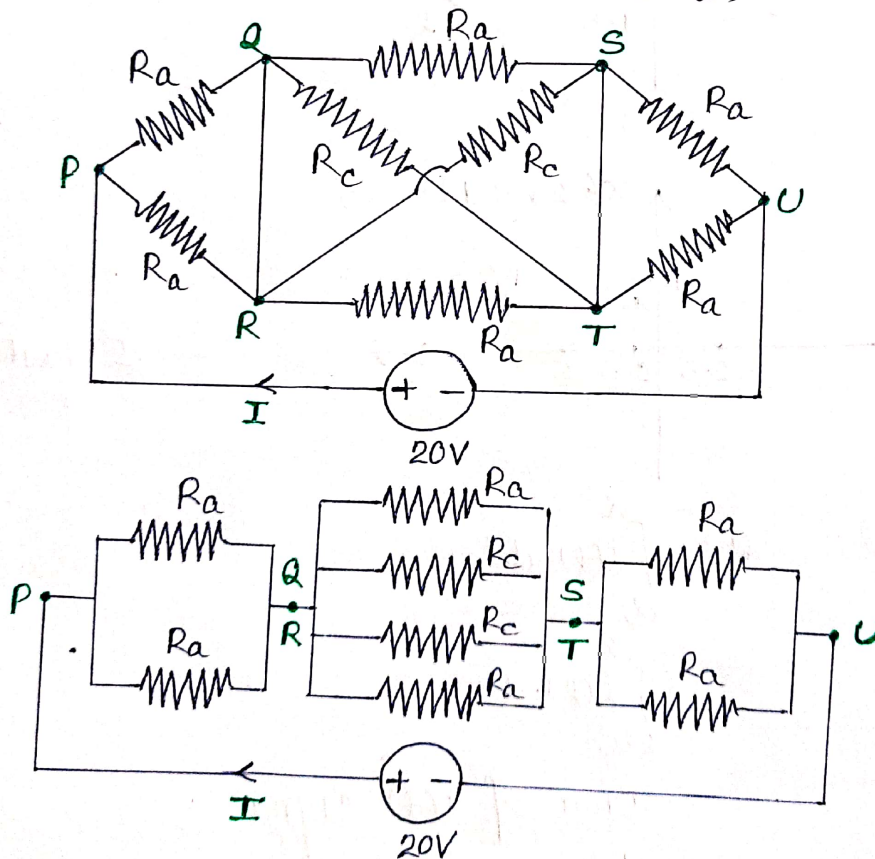

Given -  $R_a = 5\Omega$ ,  $R_c = 10\Omega$

Hence equivalent resistance between 'P' & 'U',

$$\begin{aligned} \therefore R_{eq} &= 2(R_a || R_a) + (R_a || R_c || R_c || R_a) \\ &= R_a + \left( \frac{R_a}{2} || \frac{R_c}{2} \right) = 5 + \left( \frac{10}{2} || \frac{5}{2} \right) = 6.67\Omega \end{aligned}$$


-(2 Marks)

$$\therefore \text{Current through source} = I = \frac{20}{R_{eq}} \approx 3A$$

-(2 Marks)




SOL(3) :-

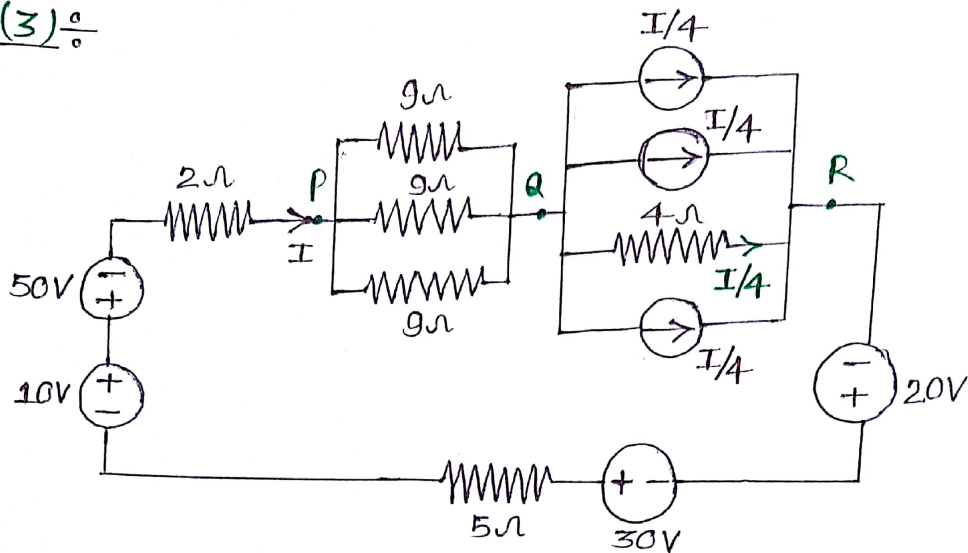


In the given network between point 'Q' & 'R', all branch having equal current ( $I/4$ ) & voltage drop. Hence all parallel branch ~~will~~ have equal resistance ( $4\Omega$ ).

Now network can be reduced as —

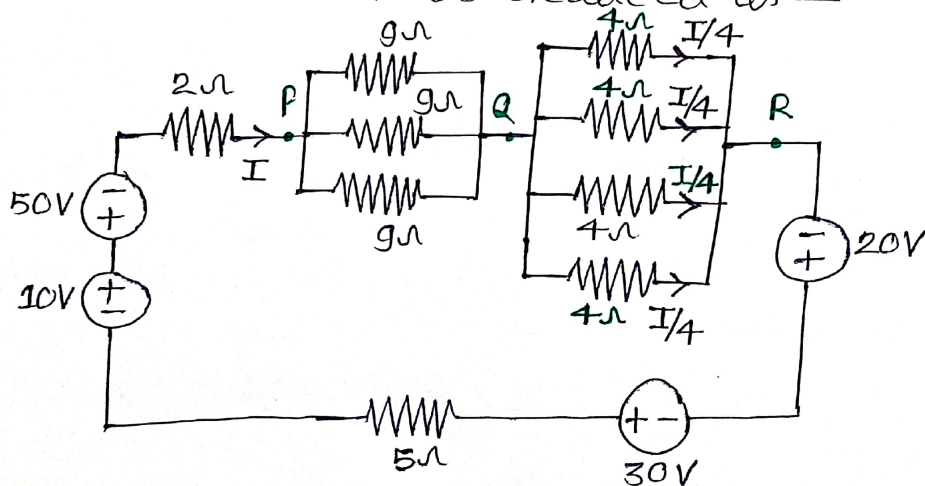

— (1 Marks)

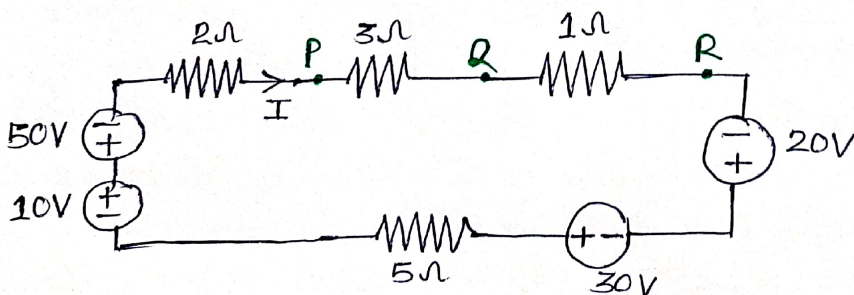

Apply KVL —  $50 + (2+3+1+5)I - 20 - 30 - 10 = 0$

$$11I = 10$$

$$I = (10/11)A = 0.91A$$

∴ Current through ' $4\Omega$ ' resistance =  $(I/4) = 0.23A$

∴ Voltage across ' $4\Omega$ ' resistance =  $4 \times 0.23 = 0.92 \text{ Volt}$

— (2 Marks)