

Basic Electronics (ECE113)

Quiz 3_Solution

Ans 1.

$$V = 100 \text{ V}; \tau = 0.8 \text{ s}, R = 50 \text{ k}\Omega$$

(a) Since time constant $\tau = CR$

$$\Rightarrow C = \tau / R$$

$$\Rightarrow C = \frac{0.8}{50 \times 10^3} = \boxed{16 \mu\text{F}}$$

(b) $V_C = V e^{-t/\tau} \Rightarrow 20 = 100 e^{-t/0.8}$

$$\Rightarrow e^{t/0.8} = 5 \Rightarrow t = 0.8 \ln 5$$

$$= \boxed{1.29 \text{ s}}$$

(c) $i = I e^{-t/\tau}$

The initial current flowing $I = \frac{V}{R} = \frac{100}{50 \times 10^3}$

$$\therefore i = I e^{-t/\tau} = 2 e^{(-0.5/0.8)} = 2 \text{ mA}$$

$$= 2 e^{-0.625} = 2 \times 0.535$$

$$= \boxed{1.07 \text{ mA}}$$


(d) $V_R = V_C = V e^{-t/\tau}$

$$= 100 e^{-1/0.8} = 100 e^{-1.25}$$

$$= 100 \times 0.287 = \boxed{28.7 \text{ V}}$$

Ans 2.

Date: / /

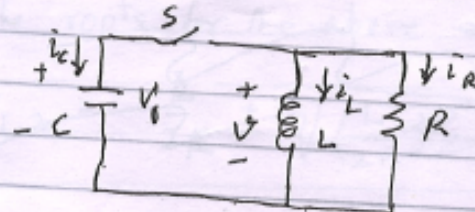


$L = 0.5 \text{ H}$
 $R = 400 \Omega$
 $C = 0.5 \text{ mF}$
 $V_0 = 30 \text{ V}$

At $t < 0$

$i_c(t) = 0 \text{ A}$ $V(t) = 0 \text{ V}$ $i_L(t) = 0 \text{ A}$ $i_R(t) = 0 \text{ A}$

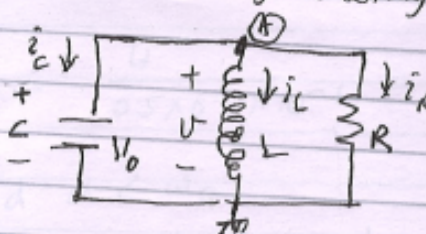At $t = 0_+$, the switch is closed. The equivalent ckt will be seen as following:



Since the capacitor voltage can not change between $t = 0_-$ to $t = 0_+$ (i.e. closing of switch), so voltage across inductor is same as capacitor voltage.

$V(t=0_+) = V_0 = 30 \text{ V}$

The current through R is given as $i_R(t=0_+) = \frac{30}{R}$

$= 75 \text{ mA}$

The current in the inductor can not change instantly, so $i_L(t=0_+) = 0 \text{ mA}$

At junction (A), $i_c + i_L + i_R = 0$

$$\text{So, } i_c = -i_L - i_R = -75 \text{ mA}$$

For $t > 0$, We can obtain the solution from following equation by writing node equation at (A).

$$\frac{1}{L} \int v dt + \frac{v}{R} + C \frac{dv}{dt} = 0$$

differentiating again we get,

$$C \frac{d^2 v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0$$

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$s_{1,2} = -\frac{1}{2RC} \pm \frac{1}{2} \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}$$

$$= -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

damping factor

$$\alpha = \frac{1}{2RC}$$

$$\beta = \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$\beta = \sqrt{\alpha^2 - \omega_n^2}$$

$$\Rightarrow \beta = \omega_n \sqrt{\xi^2 - 1}$$

$$\xi = \frac{\alpha}{\omega_n} = \frac{\frac{1}{2RC}}{\frac{1}{\sqrt{LC}}}$$

$$= \frac{\sqrt{LC}}{2RC} = \frac{1}{2R} \sqrt{\frac{L}{C}}$$

$$= \frac{1}{2 \times 400} \sqrt{\frac{0.5}{0.5 \times 10^{-6}}} = \frac{1}{800} \times 10^3 = 1.25$$

So it is a overdamped system.