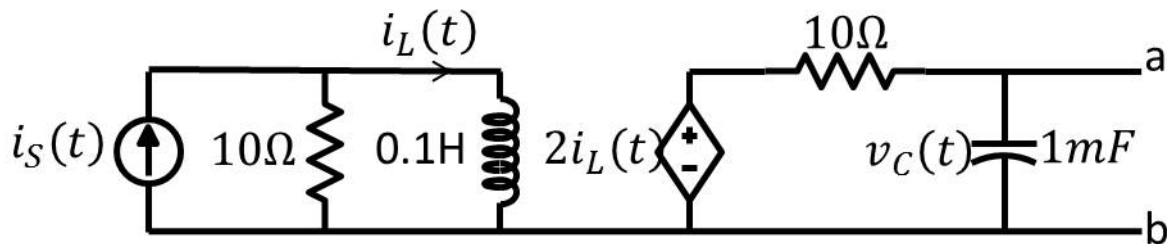


Set 1

Consider the circuit shown below where the excitation is $i_{in}(t) = 10 \cos(50t)A$. Assume that none of the elements carry any energy at initial conditions.


1. Find Thevenin's equivalent across the terminals of the capacitor (exclude the capacitor while calculating the Thevenin's equivalent).
2. Using Thevenin's equivalent model, find the time domain current $i_L(t)$ and $v_C(t)$.



Set-2

Consider the circuit shown below where the excitation is $i_{in}(t) = 2 \sin(30t - 50^\circ)A$. Assume that none of the elements carry any energy at initial conditions.

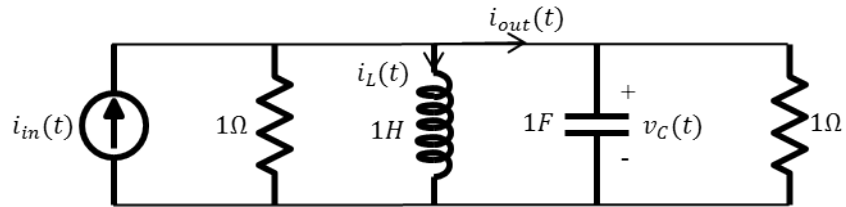1. Find Thevenin's equivalent across the terminals of the rightmost 1Ω resistor (exclude the resistor while calculating the Thevenin's equivalent).
2. Using Thevenin's equivalent model, find the time domain current $i_{out}(t)$ and $v_C(t)$.




QUIZ-1

Set 3


Questions :

Consider the circuit shown below. Assume that none of the elements carry any energy at initial conditions.

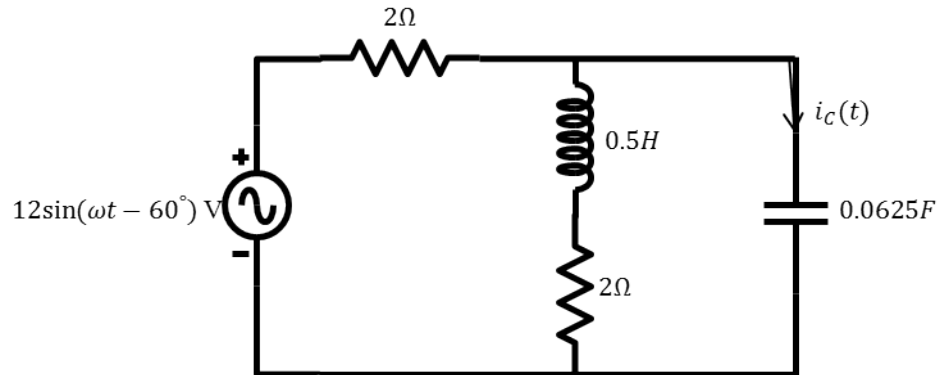1. Find Thevenin's equivalent across the terminals of the capacitor (exclude the capacitor while calculating the Thevenin's equivalent).
2. Using Thevenin's equivalent model, find the time domain current $i_C(t)$ and $v_C(t)$ across the capacitor.




Solutions:

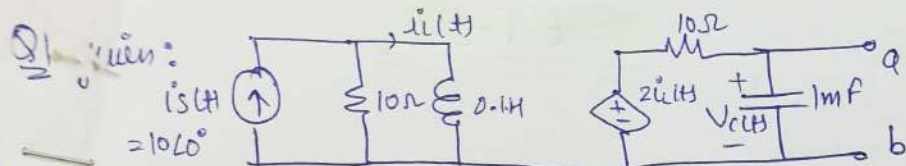

SET-1


(1)

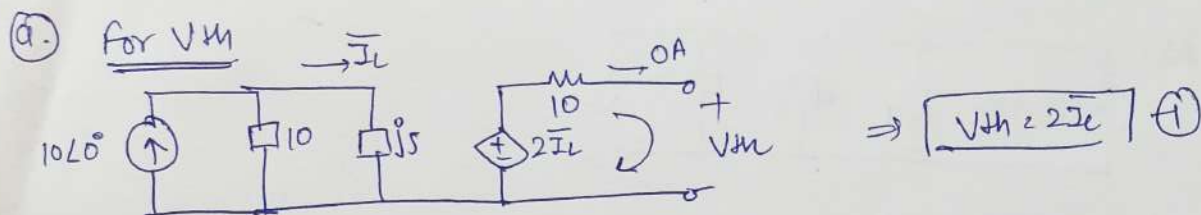


$$\bar{I}_L = 10 \angle 0^\circ \left[\frac{10}{10 + j5} \right] = 8.94 \angle -26.56^\circ \text{ A}$$

\therefore Put value of \bar{I}_L in eq (1): $V_{th} = 2 [8.94 \angle -26.56^\circ] \text{ V}$
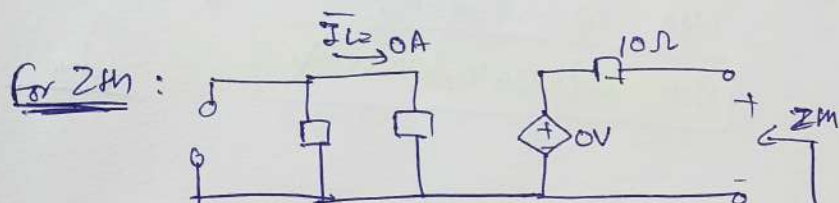
$$V_{th} = 17.88 \angle -26.56^\circ \text{ V}$$



$$Z_{th} = 10 \Omega$$

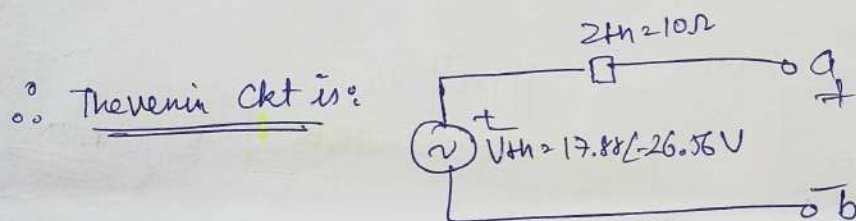


(b) For $i_L(t)$: Use simple current division rule in the ckt:

$$\bar{I}_L = 10 \angle 0^\circ \left[\frac{j5}{10 + j5} \right] = 8.94 \angle -26.56^\circ \text{ A}$$

$$\therefore i_L(t) = 8.94 \cos(50t - 26.56^\circ) \text{ A}$$

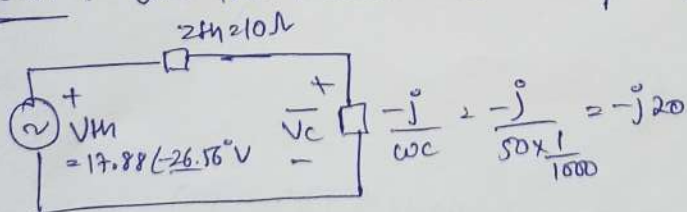For $V_{c(t)}$: Use the thevenin ckt in part (a):




$$\therefore \bar{V}_c = 17.88 \angle -26.56^\circ \left[\frac{-j20}{10 - j20} \right] = 15.99 \angle -53.12^\circ \text{ V}$$

$$\therefore V_{c(t)} = 15.99 \cos(50t - 53.12^\circ) \text{ Volts}$$

Q2. Given:




$$i_{in}(t) = 2 \sin(30t + 50^\circ) A$$

$$= 2 \angle -50^\circ A$$

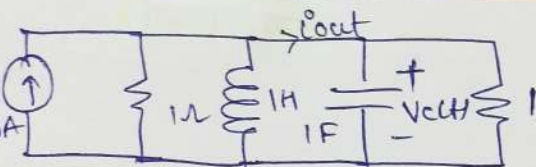

SET-2

(i) For V_{th} & Z_{th} :

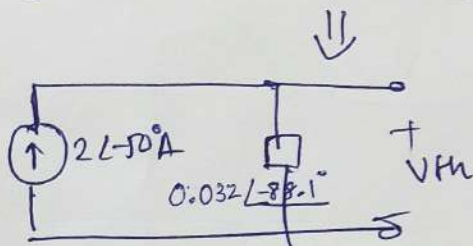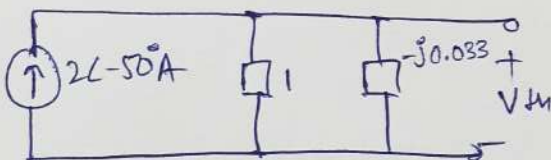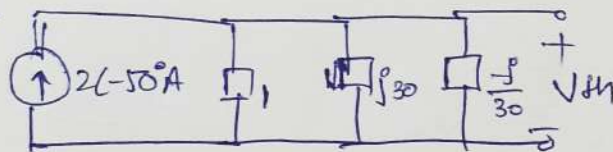


$$\therefore V_{th} = (0.032 \angle -88.1^\circ) (2 \angle -50^\circ) V$$

$$V_{th} = 0.064 \angle -138.1^\circ V$$

Ans

for Z_{th} ,

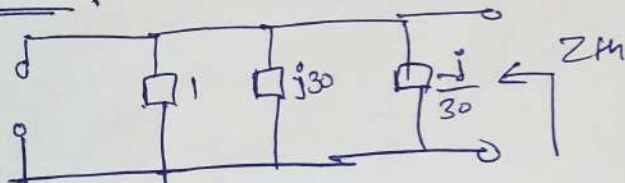


$$Z_{th} = 1 \parallel j30 \parallel -j/30$$


$$Z_{th} = 0.032 \angle -88.01^\circ$$

Ans

(b) Here


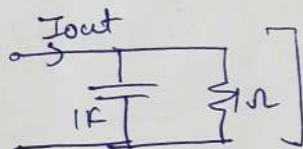


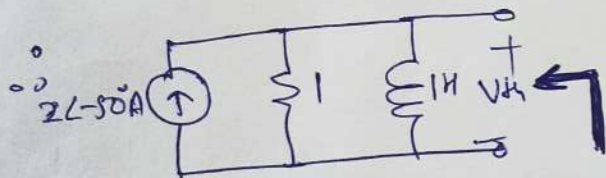Consider this as load & make the theorem's. Ckt across this load.



I need to find V_{th} & Z_{th} of this ckt now.

For V_{th}

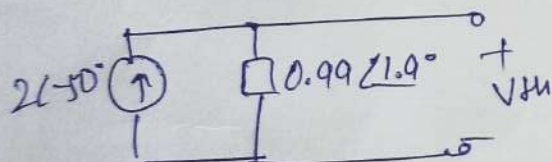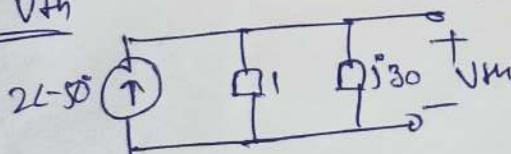


$$V_{th} = (0.99 \angle 1.9^\circ) (2 \angle -50^\circ)$$

$$V_{th} = 1.98 \angle -48.1^\circ \text{ Volts}$$


✓

Z_{th} :


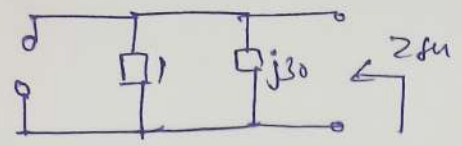


$$Z_{th} = 0.99 \angle 1.9^\circ \Omega$$

Thvenin ckt is:

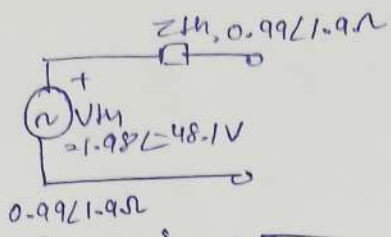

for \vec{I}_{out} :

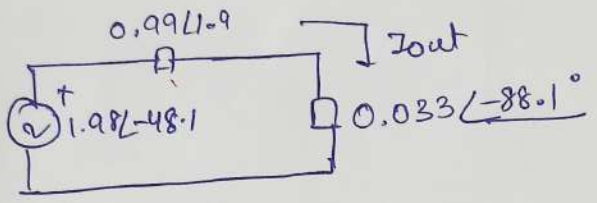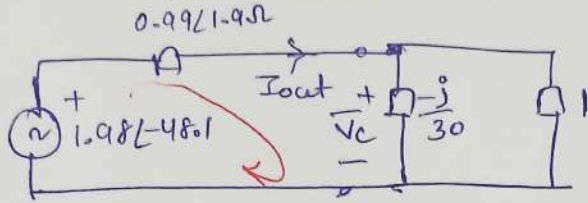

$$I_{out} = \frac{1.98 \angle -48.1}{0.99 \angle 1.9 + 0.033 \angle -88.1}$$

$$\vec{I}_{out} = 1.99 \angle -48.09^\circ A$$

~~$\vec{I}_{out}(t) = 1.99 \sin(30t - 48.09^\circ) A$~~ $\vec{I}_{out} = 1.99 \sin(30t - 48.09^\circ) A$ ✓

Ans

for $\vec{V}_C(t)$:



$$-1.98 \angle -48.1 + (0.99 \angle 1.9) \vec{I}_{out} + \vec{V}_C = 0$$

$$\vec{V}_C = 1.98 \angle -48.1 + (0.99 \angle 1.9)(1.99 \angle -48.09^\circ)$$

$$= 1.98 \angle -48.1 - 1.97 \angle -46.19^\circ$$

$$\vec{V}_C = 0.066 \angle -128.5^\circ V$$

$\therefore \vec{V}_C(t) = 0.066 \sin(30t - 128.5^\circ) \text{ Volts}$ ✓


Ans




Quiz 1

(Set-3)


Q1

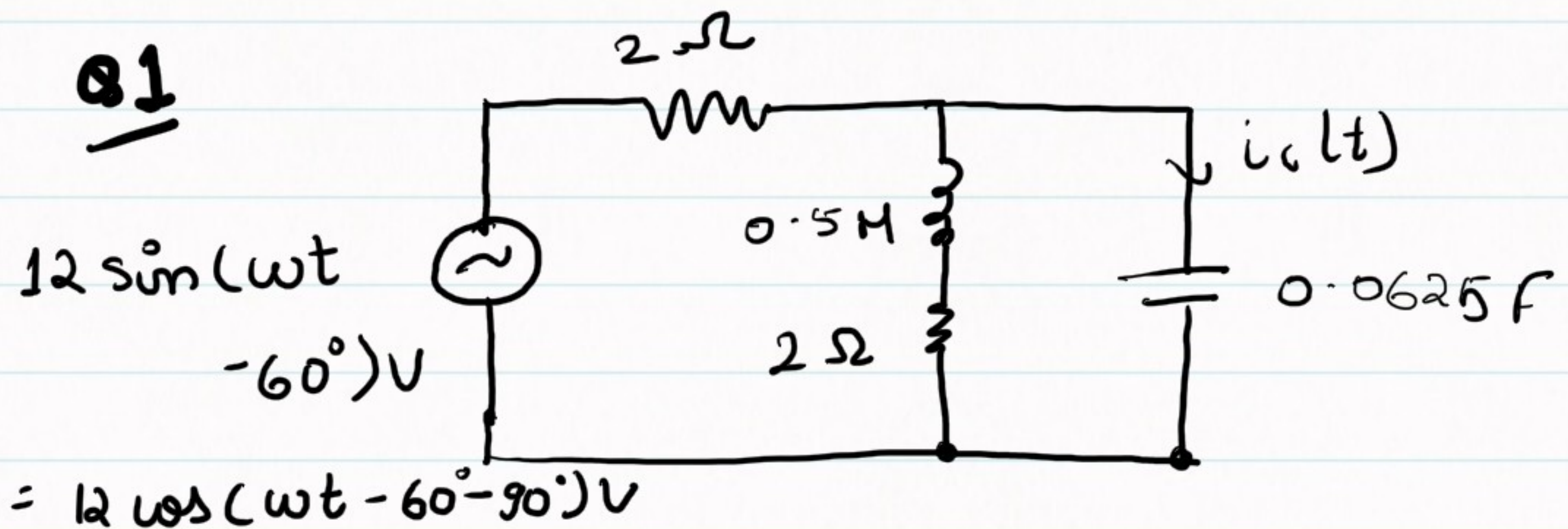

Converting to phasor

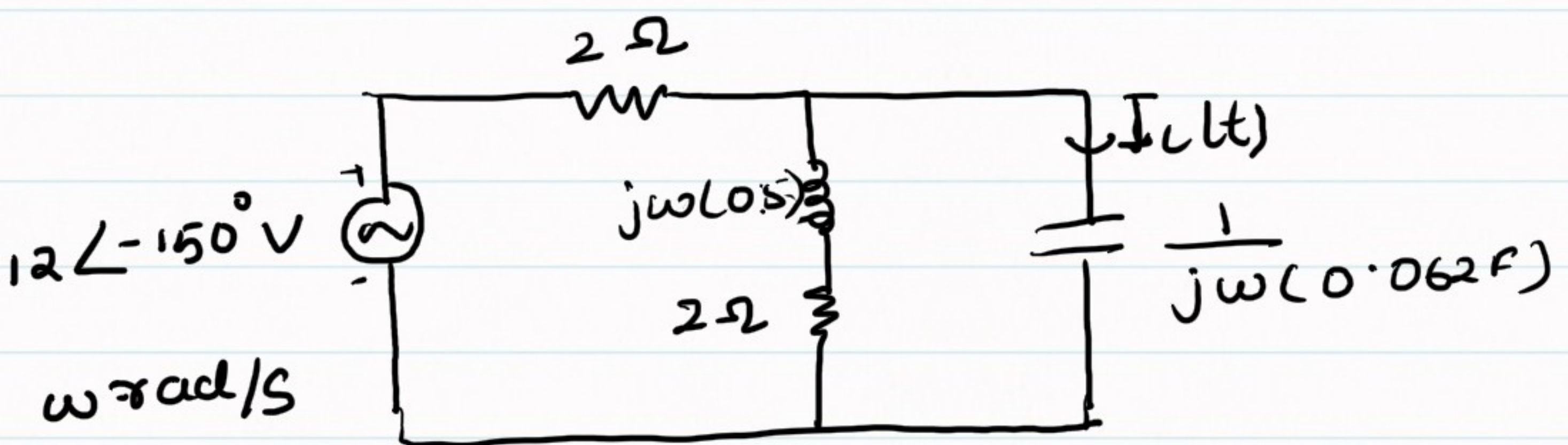

Thevenin equivalent

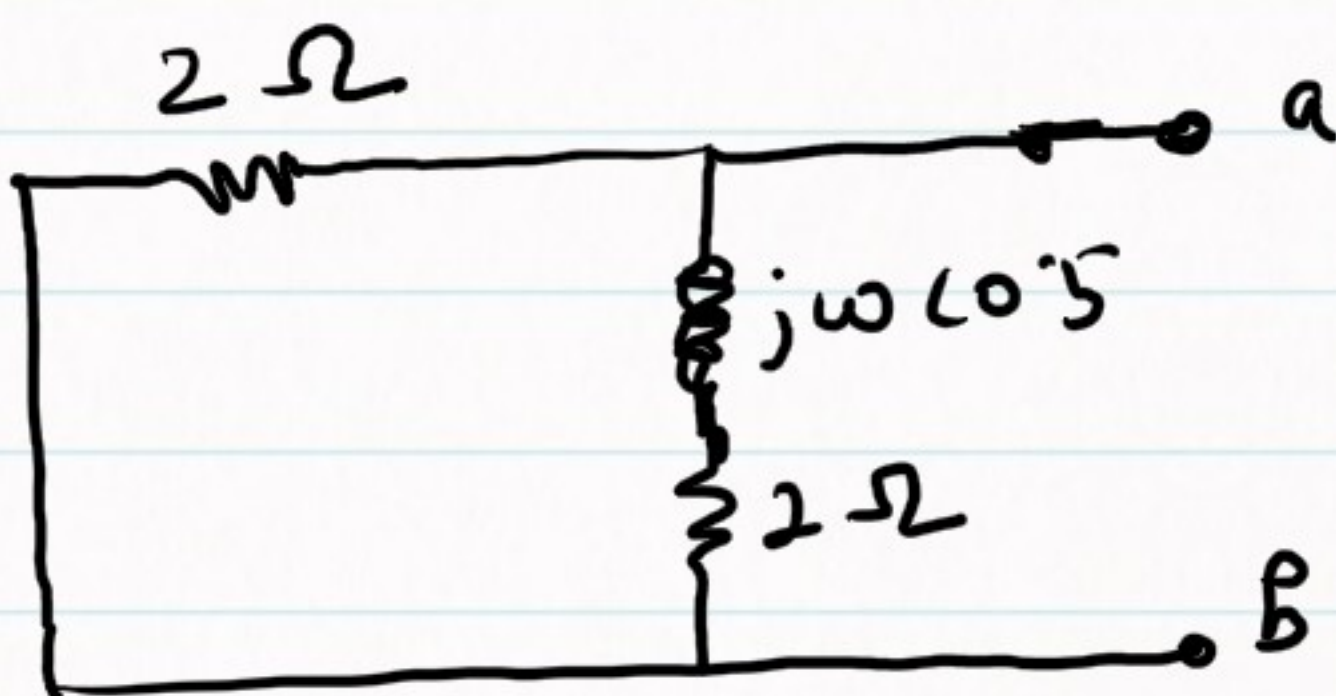

$$Z_{th} = (2 + j\omega(0.5)) \parallel 2.$$

$$\Rightarrow \tilde{Z}_{th} = (2 + j\frac{\omega}{2}) \parallel 2$$

$$= \frac{2 \times (2 + j\frac{\omega}{2})}{2 + 2 + j\frac{\omega}{2}} \rightarrow$$

$$= \frac{8 + 2j\omega}{8 + j\omega}$$

$$= \frac{8 + 2j\omega}{8 + j\omega}$$


$$\text{If } \omega = 1 \text{ rad/s}$$

$$= \frac{8.25 \angle 14.04^\circ}{8.06 \angle 7.13^\circ}$$

$$= 1.02 \angle 6.91^\circ$$

$$\tilde{Z}_{th} = 1.09 + j0.12 \Omega$$

For V_{th}

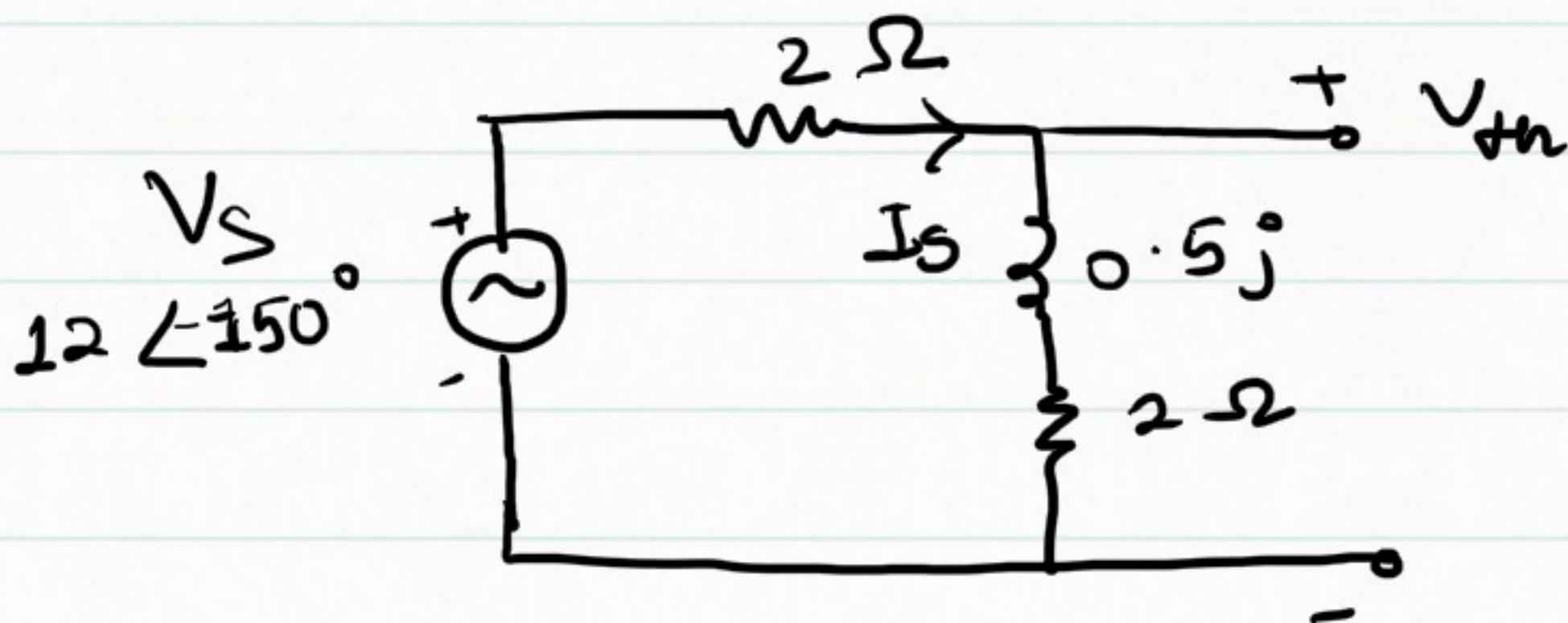

Applying KVL,

$$-V_S + 2I_S + I_S(2 + j\frac{\omega}{2}) = 0$$

$$\Rightarrow V_S = I_S(4 + j\frac{\omega}{2})$$

$$\Rightarrow I_S = \frac{(12 \angle -150^\circ)}{(4 + j\frac{\omega}{2})}$$

$$\Rightarrow I_S = \frac{12 \angle -150^\circ}{4.03 \angle 7.13^\circ} = 3 \angle -157.13^\circ A$$


$$\Rightarrow I_S = -2.7 - 1.16j A.$$

$$\therefore V_{th} = I_S(2 + 0.5j)$$

$$\Rightarrow V_{th} = 3 \angle -157^\circ \times 2.06 \angle 14.04^\circ \\ = 6.18 \angle -142.96^\circ$$

$$V_{th} = -4.99 - 3.72j$$

Now Thevenin ckt will be -

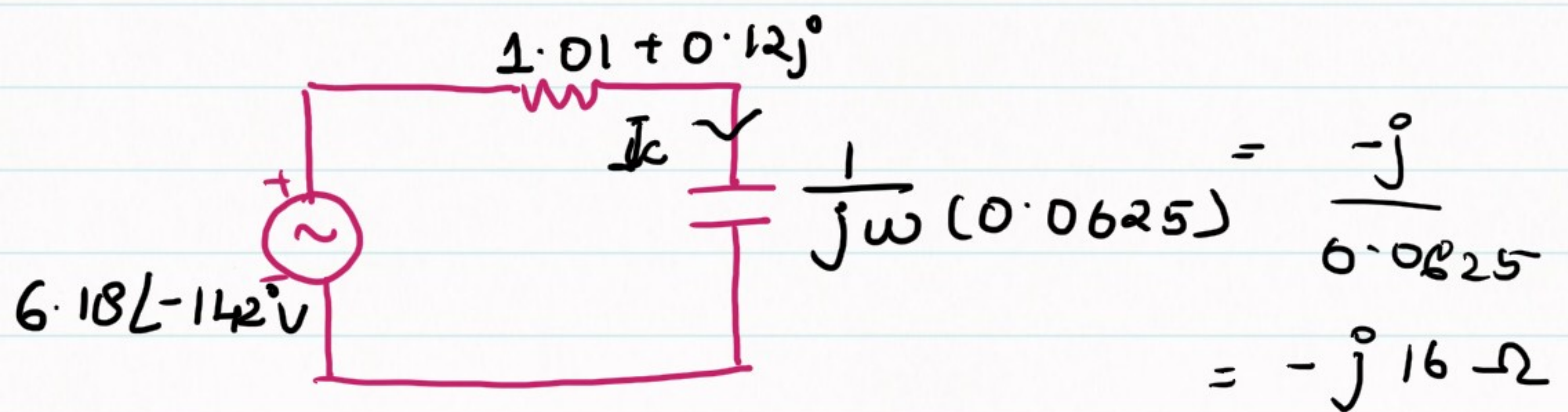

$$I_c = \frac{6.18\angle-142^\circ}{1.01 - 15.88j^\circ}$$

$$= \frac{6.18\angle-142^\circ}{15.91\angle-86.36^\circ}$$

$$I_c = 0.388\angle-55.64^\circ$$

$$\Rightarrow i_c(t) = 0.388 \cos(t - 55.64^\circ) \text{ A}$$

$$\text{Also, } V_c = I_c \times Z_c$$

$$= 0.388\angle-55.64^\circ \times (-j16) \quad \rightarrow 16\angle-90^\circ$$

$$= 6.208\angle-145.46^\circ$$

$$\therefore v_c(t) = 6.208 \cos(t - 145.46^\circ) \text{ V}$$