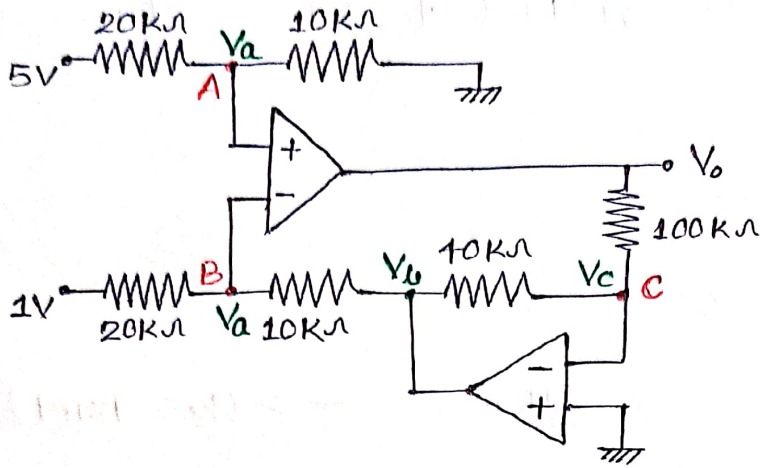


BE QUIZ-5 RUBRIC

SOL (1) :



Node A & B both will be on same potential (let V_a) due to virtual short.

$$\therefore V_a = \left(\frac{10}{10+20} \right) 5 \quad (\text{at Point/Node-A})$$

$$\therefore V_a = \left(\frac{5}{3}\right) V \quad \text{--- (a)} \quad \rightarrow (1 \text{ point})$$

KCL at node B —

$$\frac{V_a - 1}{20} + \frac{V_a - V_b}{10} = 0$$

$\therefore V_L = 2V$ — (6) \rightarrow (2 Point)


KCL at node c —

$$\frac{0 - V_L}{40} + \frac{0 - V_o}{100} = 0$$

$\therefore V_c = 0V$ (virtual short)

$\therefore V_0 = (-5) \text{ Volt} \quad \text{--- (c) } \rightarrow (2 \text{ Point})$

SOL(2):

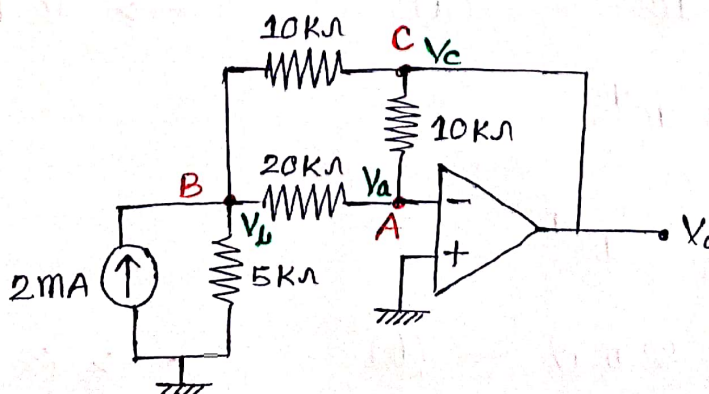

At Point/Node-C, $V_c = V_o$ — (a)

At Node-A, $V_a = 0V$ (virtual short) — (b)

KCL at node A —

$$\frac{V_a - V_b}{20} + \frac{V_a - V_c}{10} = 0$$

$$\frac{0 - V_b}{20} + \frac{0 - V_o}{10} = 0$$

$$\therefore V_b = -2V_o \quad \text{— (c)} \quad \rightarrow (2.5 \text{ Point})$$

KCL at node B —

$$\frac{V_b - V_a}{20} + \frac{V_b - V_c}{10} + \frac{V_b}{5} = 2$$

$$\frac{-2V_o - 0}{20} + \frac{-2V_o - V_o}{10} + \frac{-2V_o}{5} = 2$$

$$V_o = -\frac{40}{16}$$

$$\therefore V_o = -2.5 \text{ Volt} \quad \text{— (d)} \quad \rightarrow (2.5 \text{ Point})$$

SOL(3) :

$$\text{Power gain} = \frac{\text{Output Power}}{\text{Input Power}}$$

$$A_p = \frac{P_o}{P_{in}}$$

$$A_p = 40 \text{ dB (Given)}$$

$$10 \log_{10}(A_p) = 40$$

$$\therefore A_p = 10^4 \quad \text{— (a)} \quad \rightarrow (2 \text{ Point})$$

$$\frac{P_o}{P_{in}} = 10^4$$

$$\frac{P_o}{2 \times 10^{-6}} = 10^4$$

$$\therefore P_o = 20 \text{ mW} \quad \text{— (b)} \quad \rightarrow (3 \text{ Point})$$