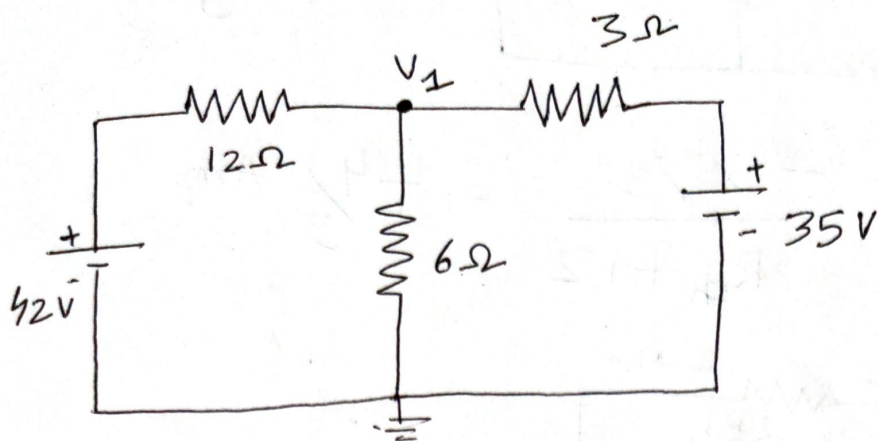


# Quiz 2 Solutions

Q1



Soln  $\Rightarrow$  (a)  $\frac{V_1 - 42}{12} + \frac{V_1}{6} + \frac{V_1 - 35}{3} = 0$

$$\frac{V_1}{12} + \frac{V_1}{6} + \frac{V_1}{3} = \frac{42}{12} + \frac{35}{3}$$

$$V_1 \left[ \frac{1+2+4}{12} \right] = \frac{42+140}{12} = \frac{182}{12}$$


$$V_1 = \frac{182}{7} = 26 \text{ Volt}$$

Current in  $12\Omega = \frac{V_1 - 42}{12}$   ~~$\frac{182}{12} - \frac{42}{12}$~~

$$= \frac{26 - 42}{12} = \frac{-16}{12} = -\frac{4}{3} \text{ Amp.}$$

(OR)

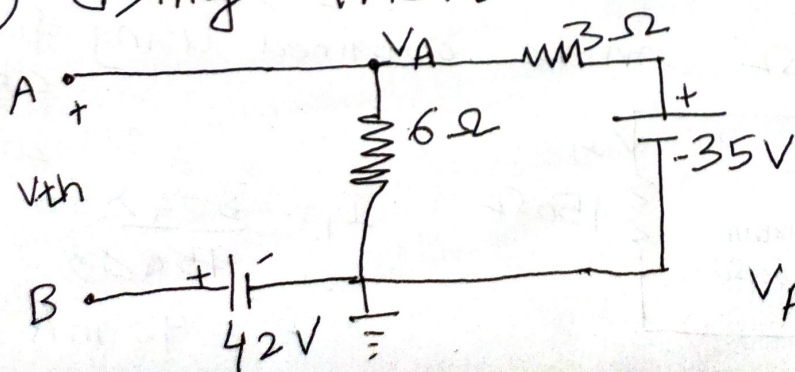(b) Using Thevenin's Theorem for  $12\Omega$  resistor




$$V_A = \frac{6}{3} \times 35 \text{ V}$$

$$= \frac{70}{3} \text{ Volt}$$


$$V_A - V_B = V_{th} = \frac{70}{3} - 42 = \frac{-56}{3}$$

$$R_{th} =$$

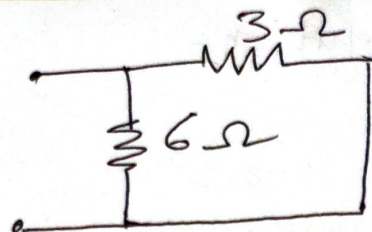


$$R_{th} = \frac{18}{9} = 2 \Omega$$
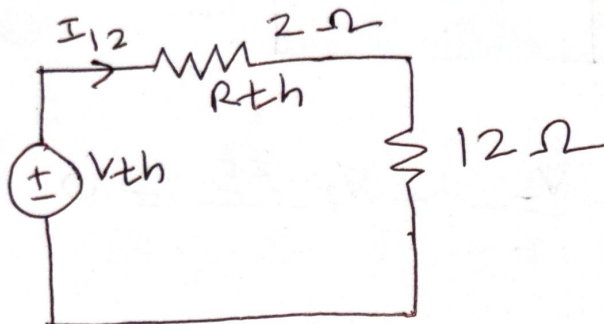
$$I_{12} = \frac{-56/3}{R_{th} + 12} = -\frac{4}{3} \text{ Amp}$$




Q(2)

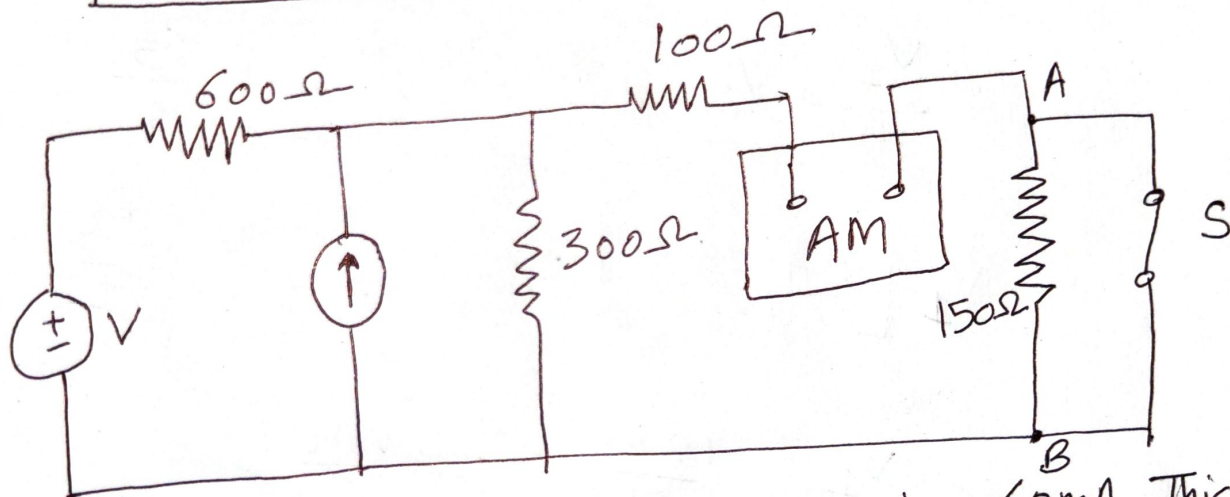


With switch 'S' closed, ammeter current = 60mA. This is the short circuit current across AB.

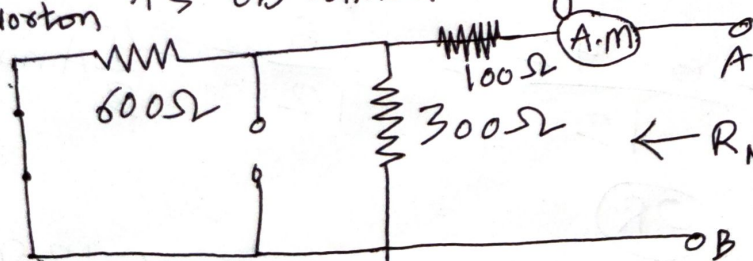The  $R_{Norton}$  is obtained using following circuit



$$R_{Norton} = \frac{100 \times 600}{900} + 100 = 200 + 100 = 300 \Omega$$

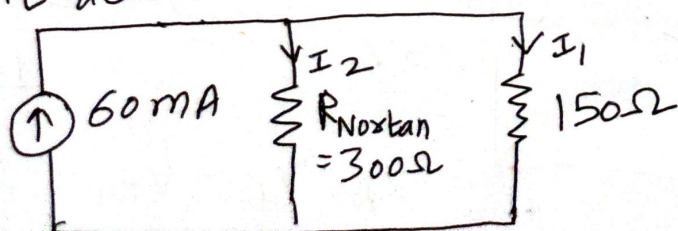Current across 150 ohm can be obtained using following ckt.



$$I_1 = \frac{6 \times 20}{450.83} = 40 \text{ mA}$$