

ECE113: Basic Electronics Mid Semester Exam-2023

Date: **15/04/2023**

Duration: **1Hours**

Total Points: **40 Points**

Q1: The **V-I** characteristic of two elements is shown in Fig. 1. Comments about Active/Passive, Linear/Non-linear & Unilateral/Bilateral parameters in both cases. **(2*1 Points)**

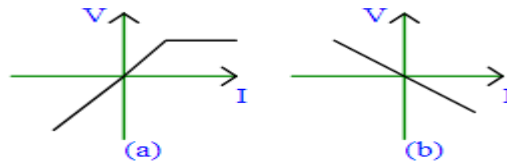


Figure 1

Q2: In Fig. 2, switch (S_1) was initially closed for sufficient time. At time $t = t_0$ sec, the switch (S_1) is opened & after time $t = (t_0 + \Delta t_0)$ sec, the switch (S_2) is closed. What will happen in the circuit at time $t = (t_0 + \Delta t_0)$ sec ? **(2 Points)**

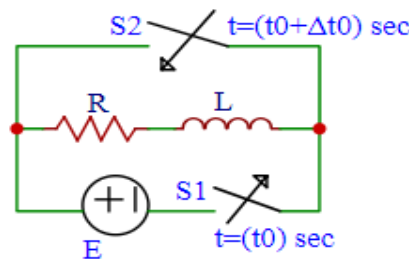


Figure 2

Q3: In Fig. 3, for $C=2F$, $R=4\ \Omega$ & $L=2H$, the current $I=1A$. When $C=1F$, $R=2\ \Omega$ & $L=1H$, the current " I " would be- **(3 Points)**

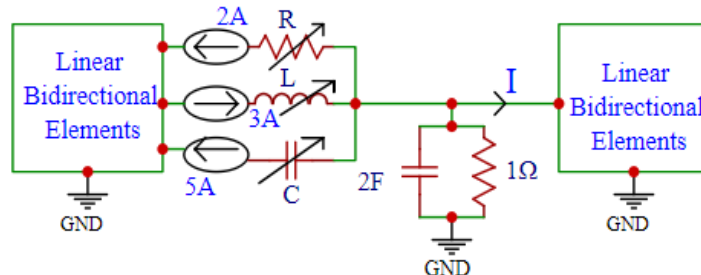


Figure 3

Q4: How many $5\ \mu F$, $100V$ capacitors are needed to make a capacitor of $50\ \mu F$, $500V$? Explain with connection diagram as well. **(3 Points)**

Q5: Find V_{AB} in the circuit in Fig. 4 with a proper circuit diagram having all useful notation. **(6 Points)**



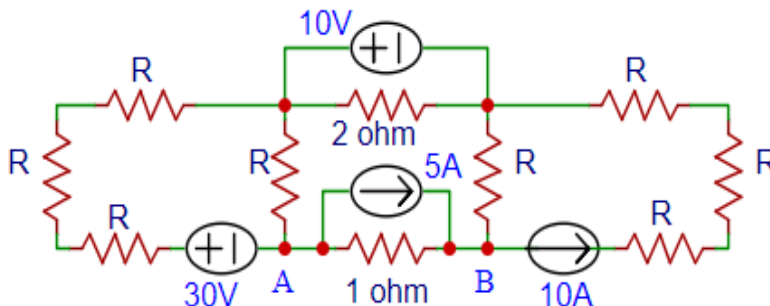


Figure 4

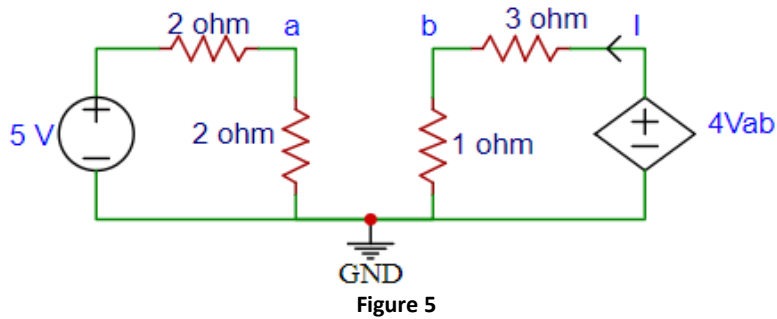
Q6: In the given following circuit, find out the value of current ' I ' and voltage across points 'a' & 'b' (V_{ab}) using mesh analysis, with a proper circuit diagram. **(6 Points)**



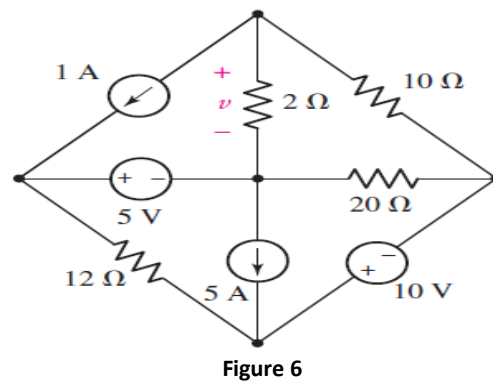Q7: In the given following circuit, find out the value of voltage (v) across $2\ \Omega$ resistance by using super node analysis, with a proper circuit diagram. **(6 Points)**



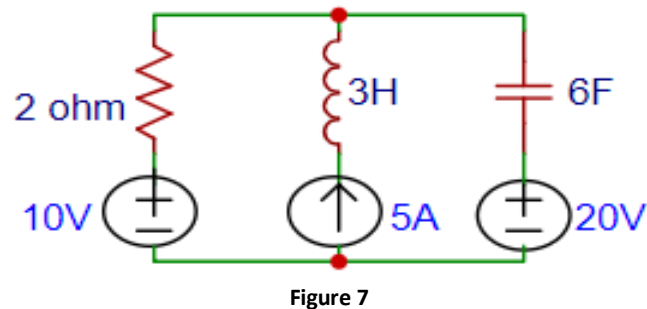Q8: Develop a dual network of the network shown in Fig. 7, with proper explanation. **(6 Points)**



Q9: Find out the value of current across the inductor at $t=5\text{ sec}$, in the given following circuit in Fig. 8.

(6 Points)

