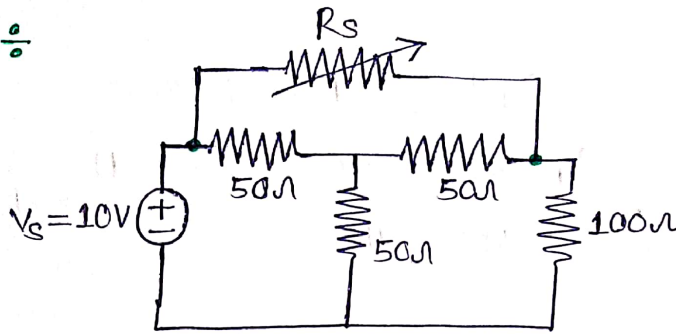


BE Quiz-3 Rubric

SOL(1):




Here for maximum power transfer from the 10V source to the 100Ω load is possible, when the value of variable resistor ' R_s ' should be minimum. \rightarrow (2.5 Point)

\therefore Minimum possible value of $R_s = 0\Omega$ \rightarrow (2.5 Point)

SOL(2):

Case(I):

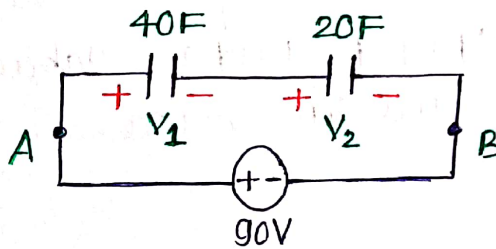

$$(Q = CV)$$

at steady state (after long time),

$$V_1 = \left(\frac{20}{40+20}\right) 90 = 30 \text{ Volt}$$


$$V_2 = \left(\frac{40}{40+20}\right) 90 = 60 \text{ Volt}$$

$$Q_1 (\text{charge at } 40F) = 40 \times 30 = 1200C \quad \text{--- (1)}$$

$$Q_2 (\text{charge at } 20F) = 20 \times 60 = 1200C \quad \text{--- (2)}$$

\rightarrow (2x0.5 Point)

Case(II):

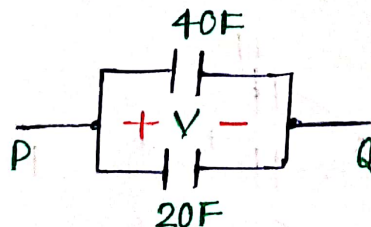

at steady state (after long time),

$$V = \frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

$$\frac{Q_1}{Q_2} = \frac{C_1}{C_2} = \frac{40}{20} = 2 \quad \text{--- (3)} \quad \rightarrow (1 \text{ Point})$$

By eqⁿ (1) & (2), we get — $Q_1 + Q_2 = 1200 + 1200$

$$Q_1 + Q_2 = 2400 \quad \text{--- (4)} \quad \rightarrow (1 \text{ Point})$$

By eqⁿ (3) & (4), we get (for case-II)

$$Q_1 = 1600 \text{ C}$$

$$Q_2 = 800 \text{ C}$$

$\rightarrow (2 \times 0.5 \text{ Point})$



\therefore Voltage across each capacitor in parallel combination,

$$V = \frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

$$= \frac{1600}{40} = \frac{800}{20} = 40 \text{ Volt}$$


$\rightarrow (1 \text{ Point})$

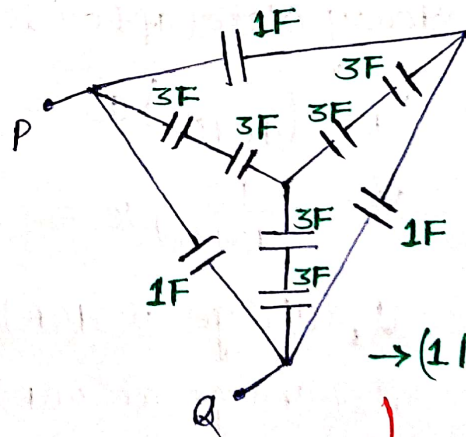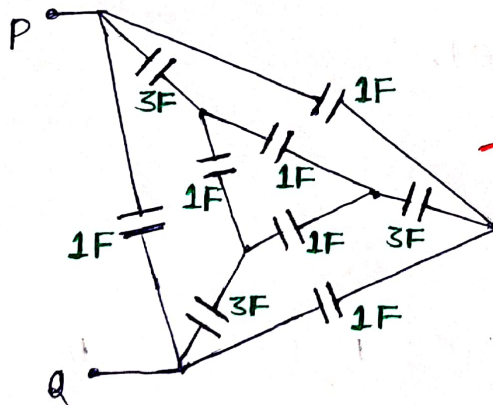SOL(3) \div As we know that — Capacitors of equal values transformed from Star to Delta, capacitance decrease by 3 times and vice versa.



$\rightarrow (1 \text{ Point})$

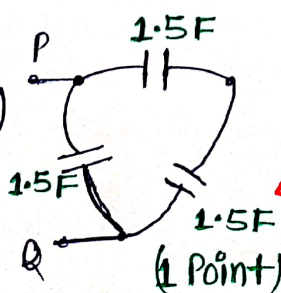
$$\therefore C_{eq} = (1.5) \parallel (0.75)$$




(1 Point)

$$\therefore C_{eq} = 2.25 \text{ F}$$

$\rightarrow (1 \text{ Point})$

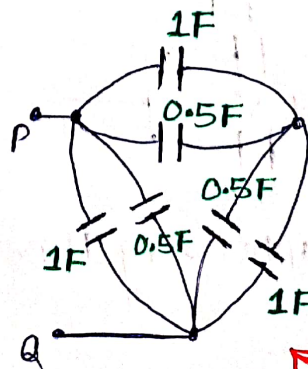

(1 Point)

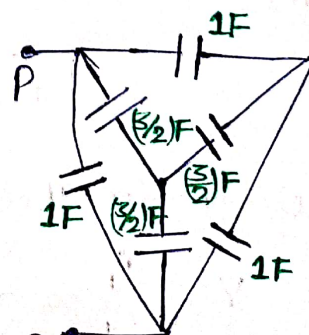

(1 Point)