

Quiz 3  
Basic Electronics - ECE113  
Duration: 30 mins  
Marks: 10  
Date: 4/07/2022    Time: 4.45 - 5.15 pm

1. A capacitor is charged to 100 V and then discharged through a 50 k $\Omega$  resistor. If the time constant of the circuit is 0.8 s, determine: (a) the value of the capacitor, (b) the time for the capacitor voltage to fall to 20 V, (c) the current flowing when the capacitor has been discharging for 0.5 s, and (d) the voltage drop across the resistor when the capacitor has been discharging for one second.

**[1+1+1+1 = 4 Marks]**

2. In the circuit of Fig. 1,  $L = 0.5$  H,  $R = 400$  ohm and  $C = 0.5$   $\mu$ F. The capacitor has an initial voltage of  $V_0 = 30$  V, and the switch is closed at  $t = 0$ .

- (a) Determine the numerical values of  $v$ ,  $i_R$ ,  $i_L$  and  $i_C$  just after the switch is closed, i.e. at  $t = 0^+$ .
- (b) For this system, write the governing equation in terms of  $v$ .
- (c) Will the response be under, over or critically damped?

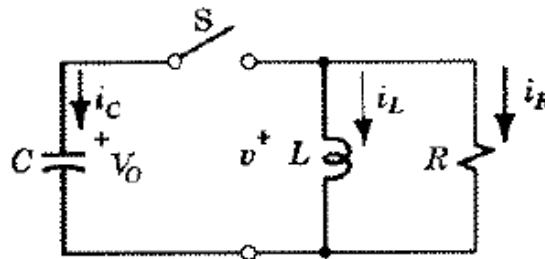


Figure 1

**[2+3+1 = 6 Marks]**