

## QUIZ 5

Basic Electronics - ECE113

Duration: 30 mins

Marks: 10

Date: 25/07/2022 Time: 4.15-4.45 pm

- Consider the op amp circuit shown in Fig. 1 where  $Z$  is a resistor  $R$  in parallel with a capacitor  $C$  and  $Z'$  consisting of a resistance  $R'$ . The input is a sweep voltage  $v = at$ . Show that the output voltage  $v_o$  is equal to  $-a RC - a (R'/R) t$ . Assume infinite open loop gain.

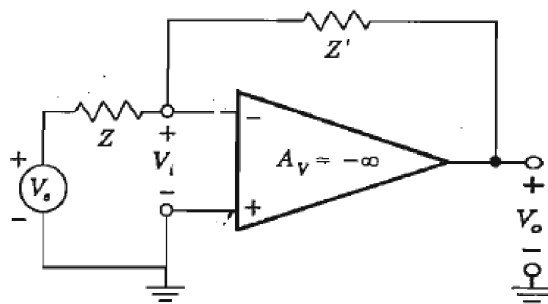


Figure 1

[5 Marks]

- For the circuit shown in Fig. 2, show that input impedance  $Z_i = \frac{v_i}{I_i} = \frac{R_1 R_2}{Z}$ . What will be  $Z_i$ , if  $Z$  is a capacitor. Comment on your result.

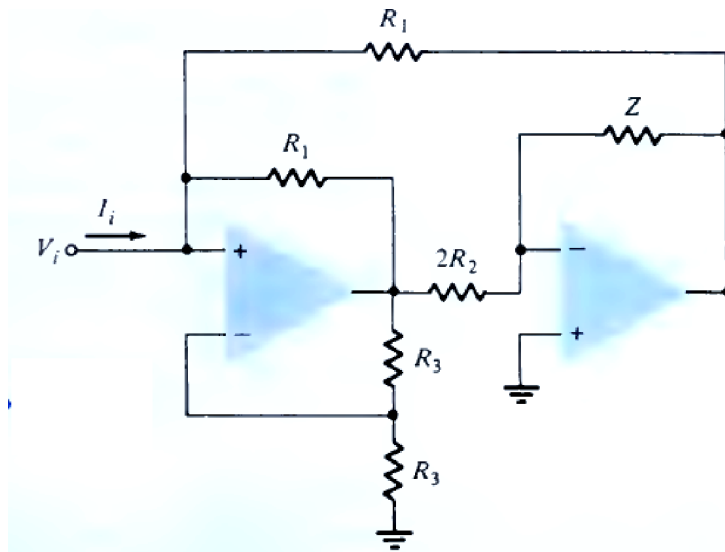


Figure 2

[5 Marks]