

Assignment -4

Basic Electronics (BE): ECE113

Winter-2023

Release: 26-May-2023 (3:00 PM)

Submission: 2-June-2023 (3:00 PM)

Instructions

- **Institute Plagiarism Policy Applicable.** This will be subjected to strict plagiarism check.
- This assignment should be attempted individually.
- A maximum point for this assignment is 40. All questions are compulsory.
- **File Submission:** Only a .pdf file are acceptable, which you have to submit on Google Classroom. Use A4 size sheets only (ruled or blank) to solve your assignment and scan it to create a .pdf file. Attempt each question on a different sheet. Do not start a new question at the back of the previous one. Do not forget to mention Page Number (bottom center) clearly on each sheet of the assignment. Submit a .pdf file named *A1_RollNo.pdf* (e.g., *A1_PhD22100.pdf*), which containing the quality scan copy of your solved assignment.
- **Submission Policy:** Turn-in your submission as early as possible to avoid late submissions. In case of multiple submissions, the latest submission will be evaluated. Expect **No Extensions**. Late submissions will not be evaluated and hence will be awarded zero marks strictly.
- **Clarifications:** Symbols have their usual meaning. Assume the missing information & mention it in the report. Use Google Classroom for any queries. In order to keep it fair for all, no email queries will be entertained.
- There could be multiple ways to approach a question. Please justify your answers. Questions without justification will get zero marks.

Q1: In Fig.-1, find out the value of output voltage (V_o).

[8 Points]

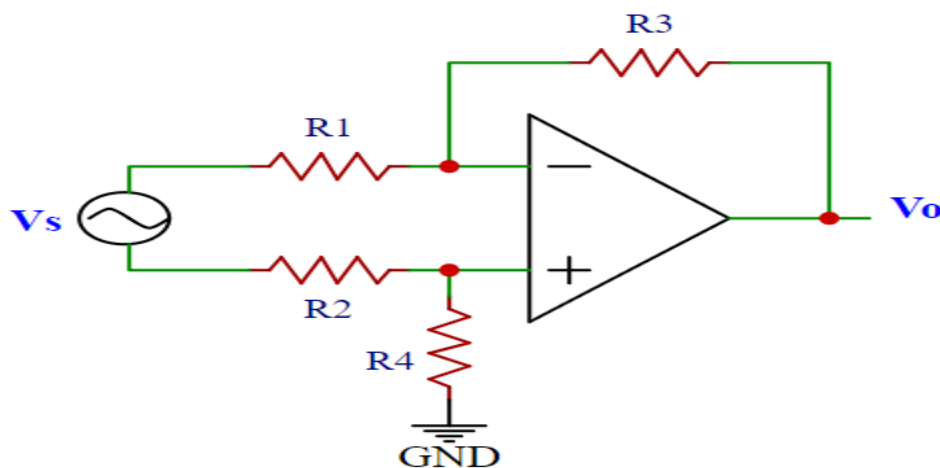


Figure 1

Q2: In Fig.-2, the switch was initially opened for long time. At time $t=0$ sec, the switch is closed. Find voltage across capacitor (V_c), current through capacitor (I_c) & output voltage (V_o) at time $t=1$ msec.

[8 Points]

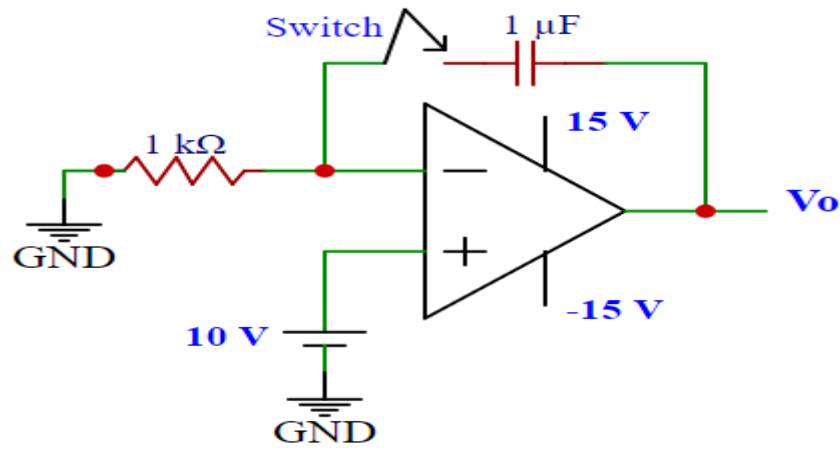


Figure 2

Q3: In Fig.-3, If $V_i(t) = 4 \sin(t)$ then find out value of $V_o(t)$, with proper explanation. Define the nature of the circuit and draw the transfer characteristics & $V_o(t)$ of the circuit.

[8 Points]

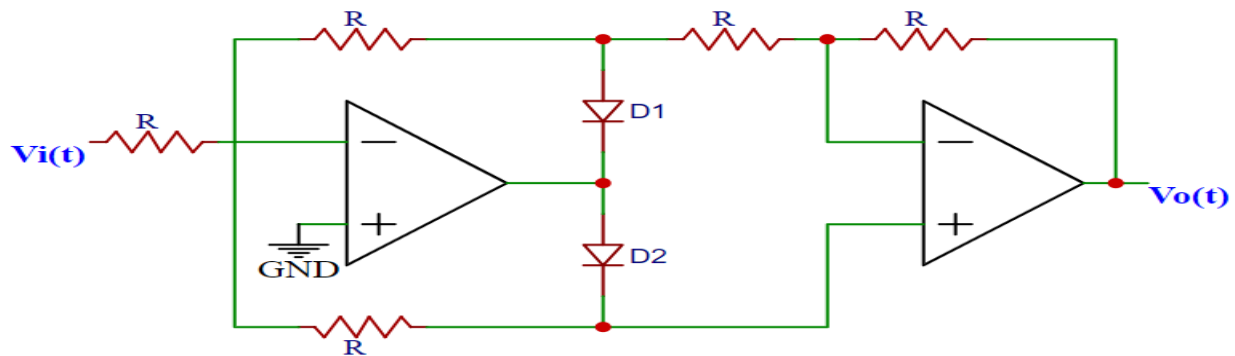


Figure 3

Q4: In Fig.-4, $V_Z=10V$, $I_L=10mA-85mA$ & $I_{Zmin}=15mA$ (symbol have their usual meaning). Find R. [8 Points]

[8 Points]

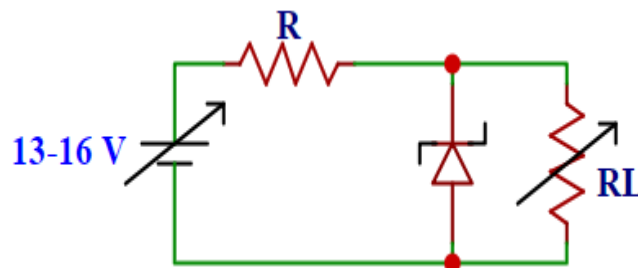


Figure 4

Q5: In Fig.-5, if $V_i(t) = 5 \sin(\omega t)$ then draw the curve for capacitor voltage [$V_c(t)$] & output voltage [$V_o(t)$] with explanation. Define the nature of circuit.

[8 Points]

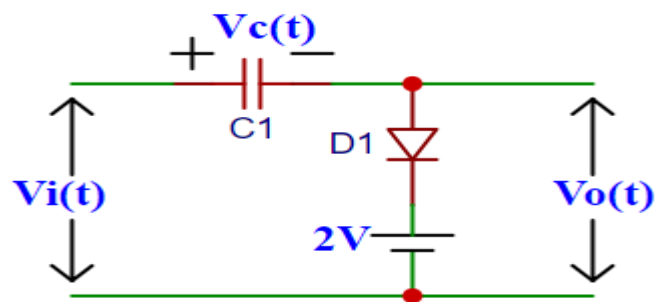


Figure 5